

# EE2019 Analog Systems and Lab: Problem Set 7

## Problem-1

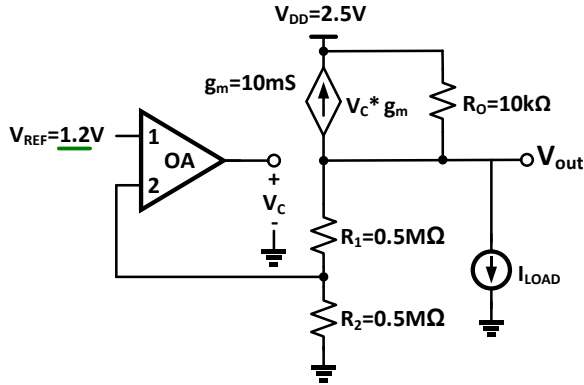


Figure 1: Circuit for Problem-1

Figure 1 shows a linear regulator. Assuming op-amp OA is ideal:

- Determine the polarity of input terminals 1 & 2 of the op-amp for negative feedback operation.
- Find the output voltage  $V_{out}$ .
- Find the minimum and maximum value of  $V_C$  if  $I_{LOAD}$  varies from 1mA to 10mA.
- Find the error in output voltage if OA is replaced with an op-amp of gain = 100 and  $R_{LOAD}$  =

## Problem-2

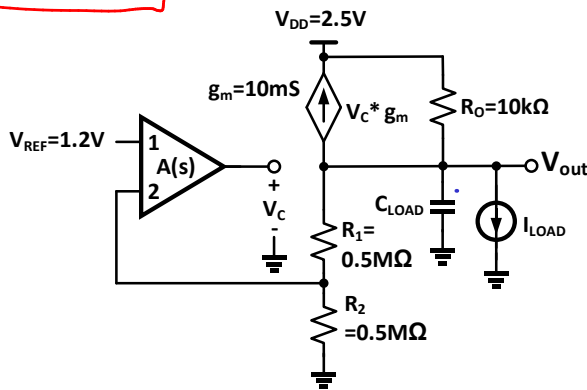


Figure 2: Circuit for Problem-2

Figure 2 shows the linear regulator of Figure 1 with a real 2-stage compensated op-amp having transfer function:

$$A(s) = \frac{100}{(1+5 \times 10^{-6}s)(1+5 \times 10^{-8}s)}$$

- Assuming op-amp pole as dominant, find the maximum value of the load capacitor,  $C_{LOAD}$  to maintain the phase margin  $> 45^\circ$ . Support your answer with bode magnitude and phase plot.
- Is it possible to use  $C_{LOAD}$  larger than the value found in (a) and still achieve a phase margin  $> 45^\circ$ ? Support your answer with bode magnitude and phase plot.
- Determine the value of  $C_{LOAD}$  for which phase margin becomes  $0^\circ$ .

## Problem-3

Simulate the circuit of Figure 2 on LTSpice and compare the result of problem-2 with your simulated results. Comment on differences, if there are any.

## Problem-4

In class, we saw that the response of a “slow” linear time-invariant system to a rapidly varying input like  $v_i$  in Figure 4 is approximately the same as that due to  $\hat{v}_i$ . In this problem, we will convince ourselves of this by working a specific example on LTSpice simulation.

Assume that  $v_i$  has a frequency of 1 MHz, and a duty cycle of 10%.  $RC = 1$  ms. On the same graph, plot  $v_o(t)$  when the input is  $v_i(t)$ , and when it is  $\hat{v}_i(t)$ .

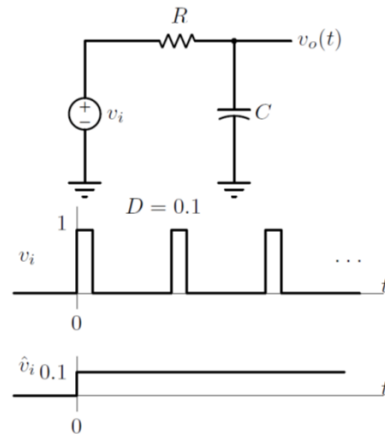


Figure 4: Circuit for Problem-4

## Problem-5

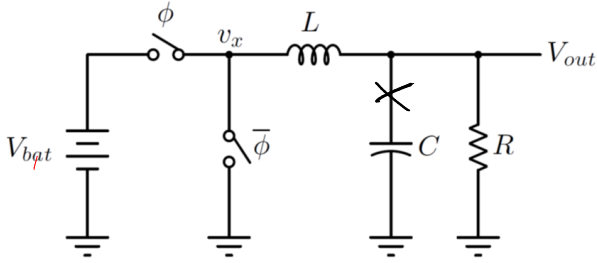


Figure 5: Circuit for Problem-5

Figure 5 shows a buck converter. The battery voltage  $V_{bat}$  is 5V.  $\phi$  and  $\bar{\phi}$  are complementary switch drive signals. The duty cycle of  $\phi$  is denoted by  $D$ . The switching frequency is 1.5 MHz.  $L = 2.2 \mu\text{H}$  and  $C = 22 \mu\text{F}$ . The load resistor  $R = 10\Omega$ .

- Determine  $D$  needed to achieve  $V_{out} = 3.3\text{V}$ .
- Determine the transfer function from  $v_x$  to  $V_{out}$ .
- Using the observation that the pole frequency of the LC filter is much lower than the switching frequency, determine the ripple in the inductor current and output voltage.
- Sketch the current waveforms in the inductor and capacitor in steady state.
- Sketch the voltage waveform  $V_{out}$  in steady state.

## Problem-6

As usual, the switching period  $T_s$  is much smaller than the time-constant of the LC network. S1 and S2 are controlled by complementary waveforms, and the waveform controlling S1 is shown in the figure. Determine the average output voltage  $v_o$ , and the average current drawn from the source. Draw the steady state current and voltage waveforms through/across the inductor and capacitor.

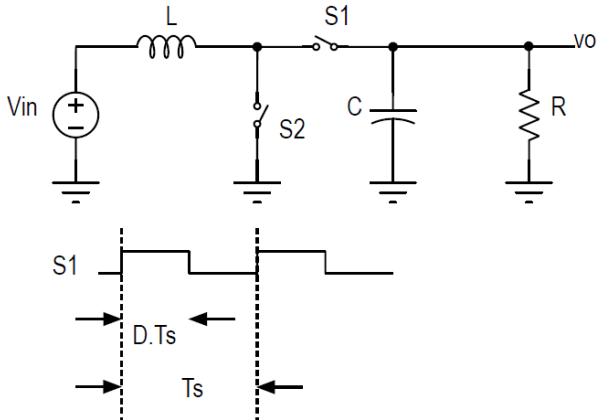


Figure 6: Circuit for Problem-6

## Problem-7

Figure 7 shows the circuit diagram of a type-I (integral) compensated buck converter with output voltage,  $V_{out}$  regulated at 2.5V for input supply,  $V_{DD}=5\text{V}$  and load current,  $I_{LOAD}=1\text{A}$ . Assuming switches  $S_P$  and  $S_N$  are ideal.

- Model the buck converter in continuous time domain and find the small signal loop gain transfer function.
- Determine the value of capacitor  $C_1$  to achieve the gain margin of  $> 20\text{dB}$  and draw the bode magnitude and phase plot.
- Find the value of control voltage,  $V_{CTRL}$  and duty cycle,  $D$  to regulate the output voltage at 2.5V.
- Find the value of peak to peak inductor ripple current and peak-to-peak output ripple voltage.
- Draw the steady state waveforms for PWM voltage ( $V_{PWM}$ ), switch currents ( $I_P$  and  $I_N$ ), inductor current ( $I_L$ ) and output voltage ( $V_{out}$ ).

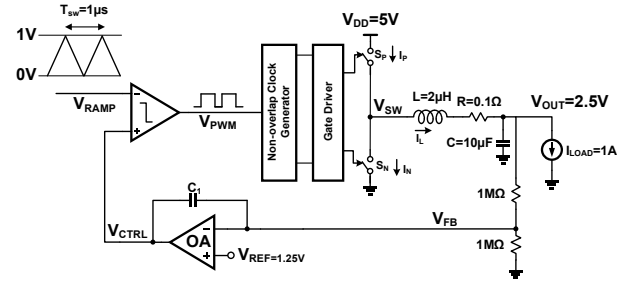


Figure 7: Circuit for Problem-7

## Problem-8

Design the buck converter circuit shown in Figure 7 and its continuous time model in LTSpice.

- Perform AC analysis and plot the loop gain magnitude and phase response of the continuous time model and verify your results found in Problem-7 (b). Observe and comment on the effect of varying capacitor ( $C_1$ ) value on unity gain frequency ( $\omega_u$ ) and gain margin. Use enough points per decade in your AC simulation to get the correct value of  $Q_O$  due to LC resonance.
- Perform transient analysis and plot waveforms  $V_{CTRL}$  and  $V_{OUT}$  of buck converter and corresponding signals in its continuous time mode on the same graph. Verify that  $V_{CTRL}$  and  $V_{OUT}$  of the buck converter have the average value as of its continuous time model. Comment on the difference if observed any. Use initial condition  $V_{OUT}=0$  in your transient simulation. Verify your results found in Problem 7 (c), (d) and (e).

## Problem-1

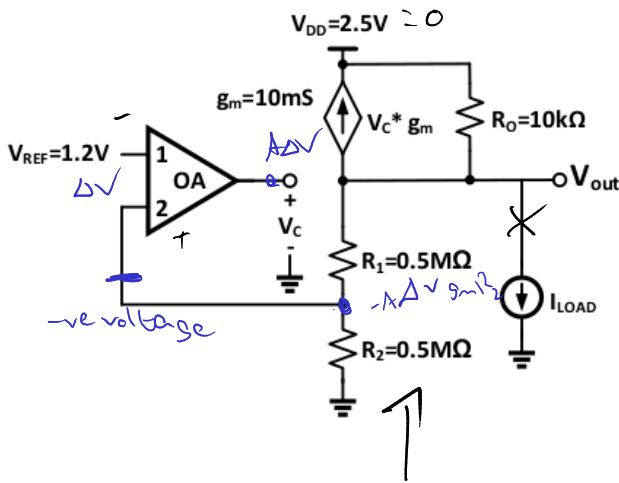



Figure 1: Circuit for Problem-1

Figure 1 shows a linear regulator. Assuming op-amp OA is ideal:

- Determine the polarity of input terminals 1 & 2 of the op-amp for negative feedback operation.
- Find the output voltage  $V_{out}$ .
- Find the minimum and maximum value of  $V_C$  if  $I_{LOAD}$  varies from 1mA to 10mA.
- Find the error in output voltage if OA is replaced with an op-amp of gain = 100 and  $R_{LOAD} =$


a) since for best voltage, terminal 2 vt is -ve, 1 is +ve

1 is -ve, 2 is +ve

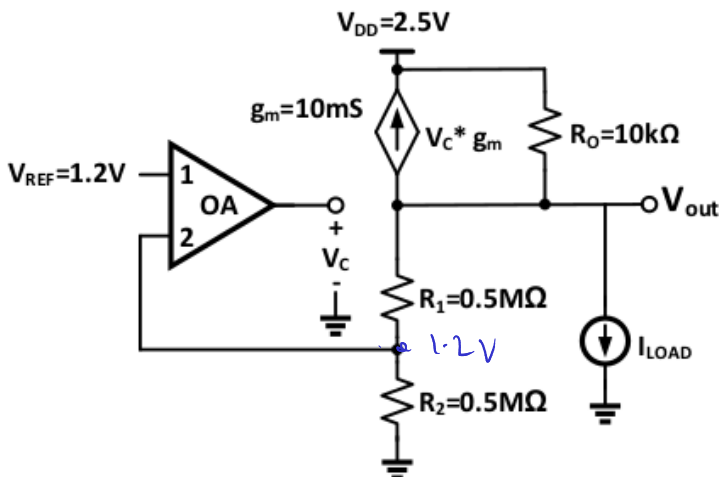

2.4V

$V_{min}$

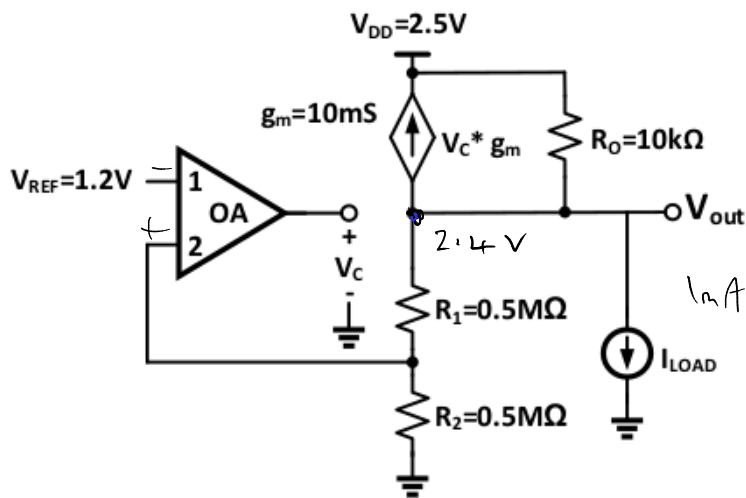

Doing KCL,

$$\frac{2.4}{10k} + 1mA + \frac{(2.4 - 2.5)}{10k} + gmV_c = 0$$

$$1mA - \frac{0.1}{10^4} + gmV_c = 0$$

$$99 \times 10^{-5} = -gmV_c$$

$$V_c = \frac{-99 \times 10^{-5}}{10^{-3}}$$

$$= -99 \times 10^{-2} = -0.99V$$

Max

$$(10mA - \frac{0.1}{10^4}) + gmV_c = 0 \quad V_c = (-0.999V)$$

d) Find the error in output voltage if OA is replaced with an op-amp of gain = 100 and  $R_{LOAD} = \infty$

$$V_c = \left( \frac{V_{out}}{2} - 1.2 \right) 100 \quad V_c gm + \frac{V_{out} - 2.5}{R_o} + 0 + \cancel{I_{load}} = 0$$

$$\frac{V_{out}}{2} - 1.2 + \frac{V_{out} - 2.5}{10k} + \cancel{I_{load}} = 0$$

$$V_{out} \left[ \frac{1}{2} + \frac{1}{10k} \right] = 1.2$$

$$\Delta V = 2.4 - \frac{1.2}{\frac{1}{2} + \frac{1}{10k}} = (0.00047V)$$

## Problem-2

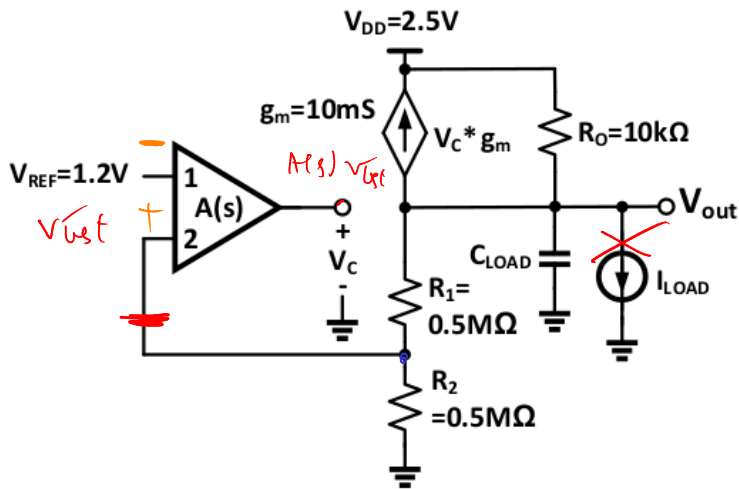


Figure 2: Circuit for Problem-2

Figure 2 shows the linear regulator of Figure 1 with a real 2-stage compensated op-amp having transfer function:

$$A(s) = \frac{100}{(1 + 5 \times 10^{-6}s)(1 + 5 \times 10^{-8}s)}$$

- Assuming op-amp pole as dominant, find the maximum value of the load capacitor,  $C_{LOAD}$  to maintain the phase margin  $> 45^\circ$ . Support your answer with bode magnitude and phase plot.
- Is it possible to use  $C_{LOAD}$  larger than the value found in (a) and still achieve a phase margin  $> 45^\circ$ ? Support your answer with bode magnitude and phase plot.
- Determine the value of  $C_{LOAD}$  for which phase margin becomes  $0^\circ$ .

$$V_c = A(s) V_{test}$$

$$R = 14 \Omega$$

$$V_{out} \Delta C_{load} + \frac{V_{out} - 0}{R_O}$$

$$+ \frac{V_{out}}{14 \Omega} + V_c g_m = 0$$

$$V_{out} \left[ s C_{load} + \frac{1}{R} + \frac{1}{R_O} \right] = -g_m A(s) V_{test}$$

$$LL(s) = \frac{V_{out}}{V_{test}} = \frac{1}{2} \frac{-g_m A(s)}{\left( s C_{load} + \frac{1}{R} + \frac{1}{R_O} \right)}$$

$$= \frac{-g_m 100 R_O A(s)}{2 \left( s C_{load} R_O + 1 \right)}$$

$$= \frac{-1 \times 10^3 \times 10^4 \times 10^4}{2 \left( 1 + \frac{s}{2 \times 10^5} \right) \left( \frac{s}{10^6} + 1 \right) \left( 1 + \frac{s}{2 \times 10^7} \right)}$$

$$= 5 \times 10^3$$

$$\left( 1 + \frac{s}{2 \times 10^5} \right) \left( 1 + \frac{s}{10^6} \right) \left( 1 + \frac{s}{2 \times 10^7} \right)$$

non pole

$$\omega_{cg} \approx p_0$$


$$\omega_{cg} = 10^9 \text{ rad/s}^{-1}$$

$$\text{Now, } P.M. = 45^\circ = 180 - \underbrace{\tan^{-1} \frac{\omega_{re}}{2 \times 10^5}}_{\approx 90^\circ} - \underbrace{\tan^{-1} \frac{\omega_{re}}{2 \times 10^7}}_{\approx 90^\circ} - \underbrace{\tan^{-1} \frac{\omega_{re}}{p_0}}_{\approx 90^\circ}$$

$$\Rightarrow \tan^{-1} \frac{\omega_{ng}}{p_0} \approx -45^\circ$$

$$C_{load} = -5 \times 10^{-16} F$$

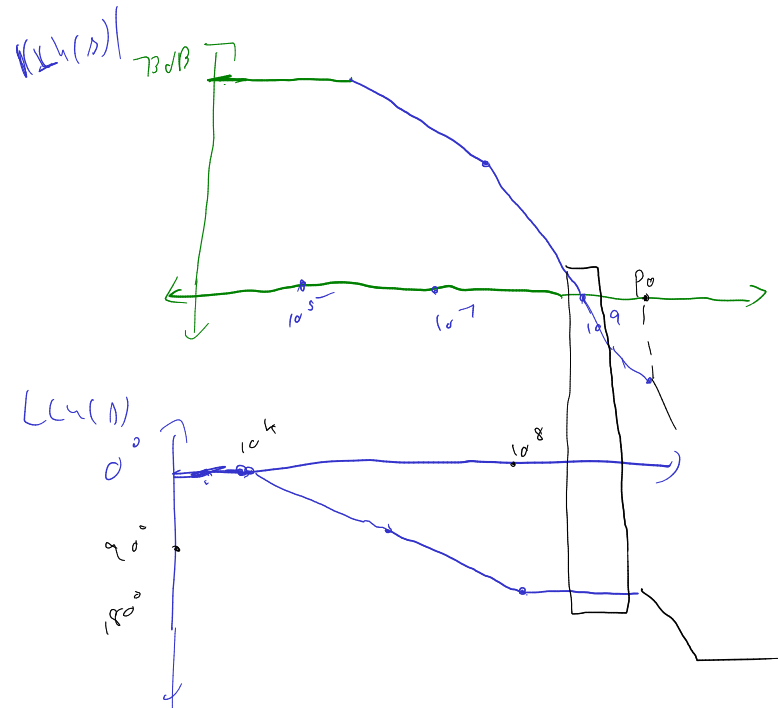$\Rightarrow C$  is -ve, so assumption is wrong



At  $\omega_{ng}$ , phase is  $180^\circ$ , so extra pole cannot bring phase to  $135^\circ$

Answer with bode magnitude and phase plot.

- b) Is it possible to use  $C_{LOAD}$  larger than the value found in (a) and still achieve a phase margin  $> 45^\circ$ ? Support your answer with bode magnitude and phase plot.

If  $\omega_c$  pole is dominant pole, then  $P.M. > 45^\circ$  is achievable

If  $\omega_c$  is dominant pole, then  $\omega_{ng} = p_1 = \boxed{2 \times 10^5 \text{ rad/s}}$

$$C_{load} = 5 \times 10^{-3}$$

$$\left(1 + \frac{s}{2 \times 10^5}\right) \left(1 + \frac{s}{p_0}\right) \left(1 + \frac{s}{2 \times 10^7}\right)$$

$$\frac{5 \times 10^3}{(\sqrt{2})(1) \frac{2 \times 10^5}{P_o}} = 1$$

$$5 \times 10^3 = \sqrt{2} \times \frac{2 \times 10^5}{P_o}$$


$$P_o = \frac{\sqrt{2} \times 2 \times 10^5}{5 \times 10^3} = \frac{\sqrt{2} \times 2 \times 20}{1} = 40\sqrt{2} \text{ W} \approx 113.1 \text{ W}$$

$$\cos \phi = \frac{1}{C_{load} \times R_o} = \frac{1}{C_{load} \times 10^4}$$

$$C_{load} = \frac{1}{40\sqrt{2} \times 10^4}$$

$$1.76 \mu\text{F}$$

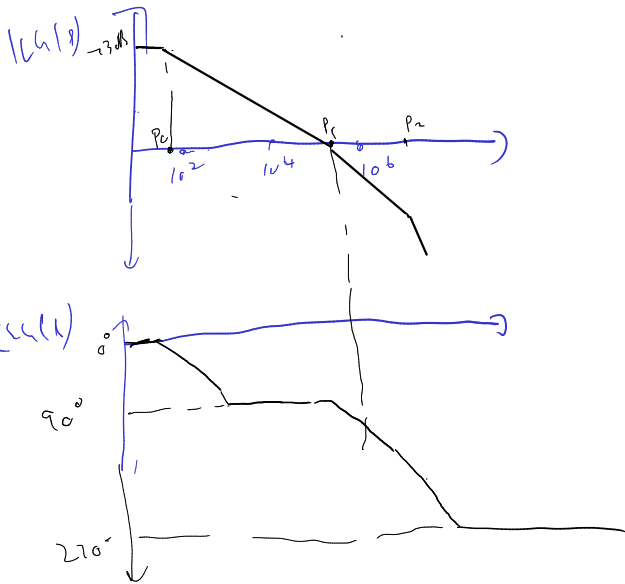For  $C_{load} = 1.76 \mu\text{F}$ ;  $\phi = 45^\circ$



c) Determine the value of  $C_{LOAD}$  for which phase margin becomes  $0^\circ$ .

$$p_1 = 0^\circ \quad z = \quad \omega_{wg} = 10 p_1 \quad \boxed{2 \times 10^6 \text{ rad s}^{-1}}$$

$$L_h(s) = \frac{5 \times 10^3}{\left(1 + \frac{s}{2 \times 10^5}\right) \left(1 + \frac{s}{p_0}\right) \left(1 + \frac{s}{2 \times 10^7}\right)}$$

$$= \frac{5 \times 10^3}{10 \times \frac{2 \times 10^6}{p_0}}$$

$$\frac{2 \times 10^7}{p_0} \sim 5 \times 10^3$$

$$p_0 = \frac{2 \times 10^7}{5 \times 10^3} = 4 \times 10^3$$

$$\boxed{4 \times 10^3 \text{ rad s}^{-1}}$$

$$= \frac{1}{10^4} C_{LOAD}$$

$$C_{LOAD} = \frac{1}{10^4} \times 4 \times 10^3$$

$$= \frac{4 \times 10^3}{10^4}$$

$$= 2.5 \times 10^{-8}$$

$$\boxed{25 \text{ nF}}$$



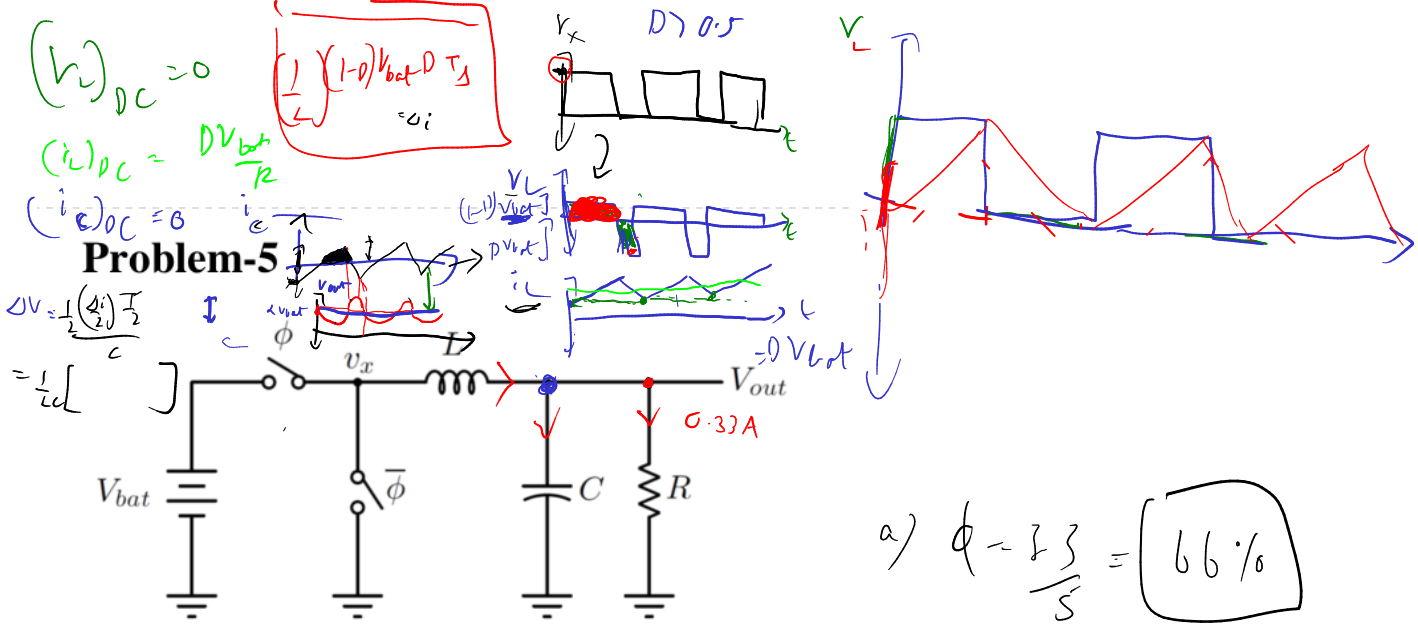


Figure 5: Circuit for Problem-5

Figure 5 shows a buck converter. The battery voltage  $V_{bat}$  is 5V.  $\phi$  and  $\bar{\phi}$  are complementary switch drive signals. The duty cycle of  $\phi$  is denoted by  $D$ . The switching frequency is 1.5 MHz.  $L = 2.2 \mu\text{H}$  and  $C = 22 \mu\text{F}$ . The load resistor  $R = 10 \Omega$ .

- Determine  $D$  needed to achieve  $V_{out} = 3.3\text{V}$ .
- Determine the transfer function from  $v_x$  to  $V_{out}$ .
- Using the observation that the pole frequency of the LC filter is much lower than the switching frequency, determine the ripple in the inductor current and output voltage.
- Sketch the current waveforms in the inductor and capacitor in steady state.
- Sketch the voltage waveform  $V_{out}$  in steady state.

Handwritten derivation of the transfer function:

$$V_{out} = \frac{R \parallel \frac{1}{sC}}{R \parallel \frac{1}{sC} + sL}$$

$$= \frac{R}{R + s^2 LC + sL}$$


$$= \frac{1}{s^2 LC + sL + 1}$$

Handwritten calculation of the natural frequency:


$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{22 \times 2.2 \times 10^{-6}}} = 0.14 \times 10^6 = 1.4 \times 10^5 \text{ rad/s}$$

Handwritten calculation of the ripple current:

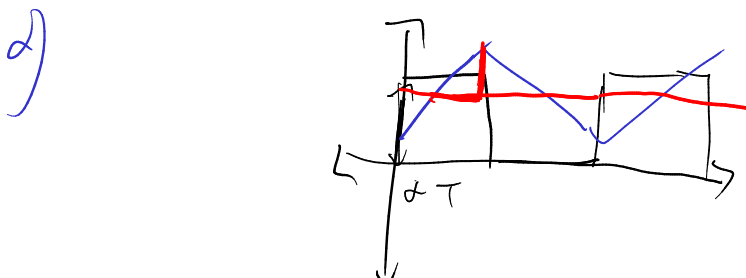
$$i_{\text{ripple}} = \frac{1}{L} \int_0^{T_{on}} (V_s - V_o) dt = \frac{1}{L} (V_s - V_o) T_{on}$$



Rough



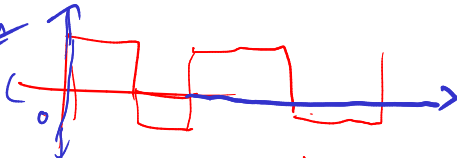

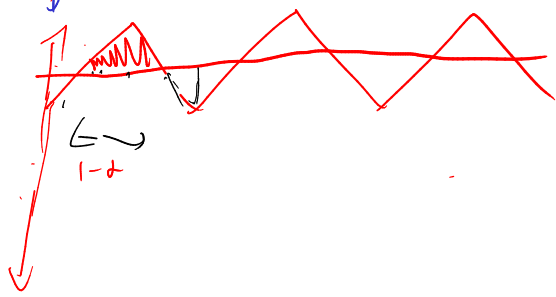
$$= \frac{1}{L} (1-d) V_{bat} dT \quad \boxed{0.33A}$$




$$V_C = \frac{1}{C} \int i_C dt$$
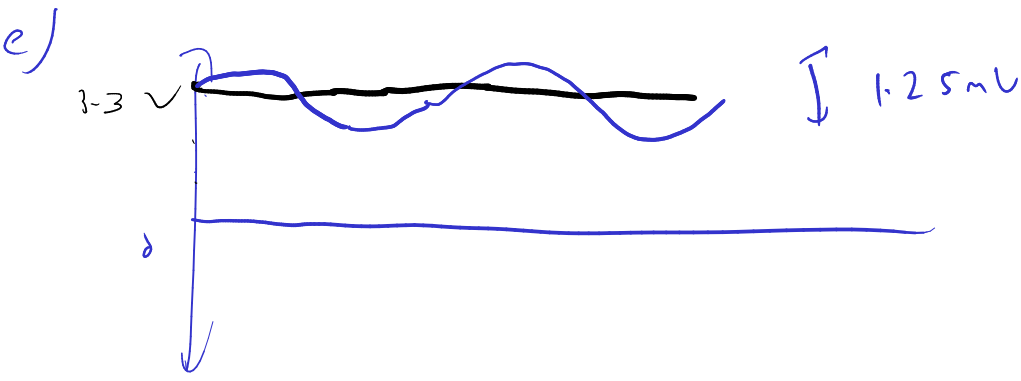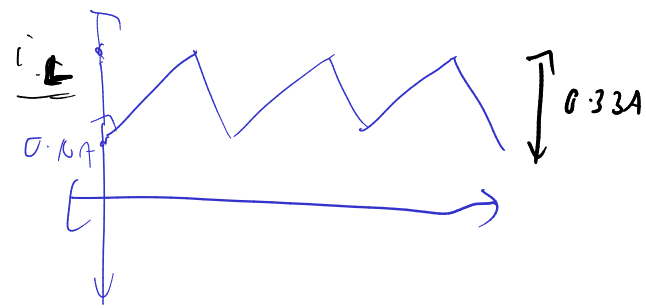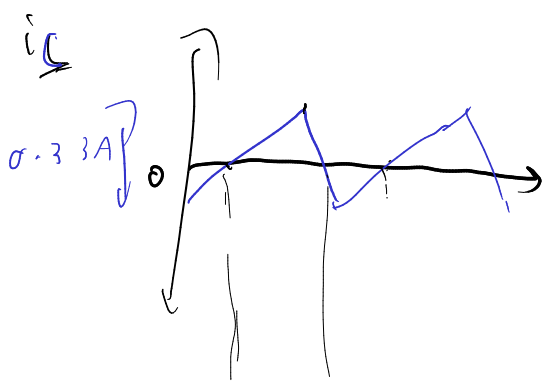
$$= \frac{1}{C} \left( \frac{1}{2} \right) \frac{\Delta i}{2} (1.25 \mu V)$$


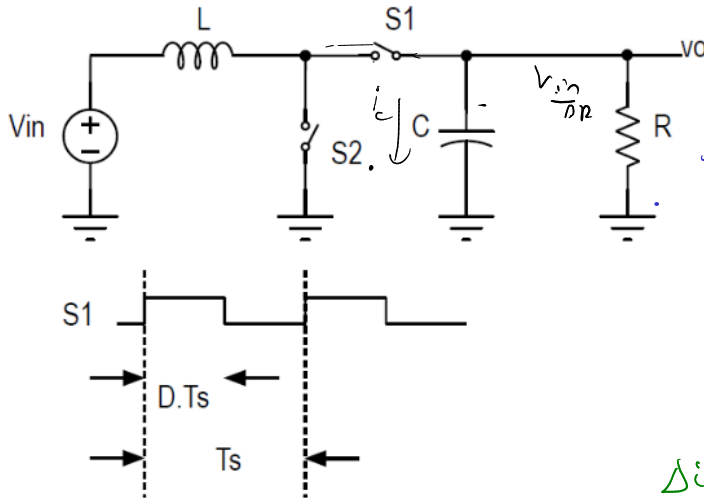
## Problem-6

As usual, the switching period  $T_s$  is much smaller than the time-constant of the LC network. S1 and S2 are controlled by complementary waveforms, and the waveform controlling S1 is shown in the figure. Determine the average output voltage  $v_o$ , and the average current drawn from the source. Draw the steady state current and voltage waveforms through/across the inductor and capacitor.



$$(V_{in} - v_o) D T_s = -V_{in} (1-D) T_s$$

$$-v_o D = -V_{in}$$


$$v_o = \frac{V_{in}}{D}$$

$$\Delta i = \frac{V_{in} (1-D) T_s}{L}$$

$$(i_{avg}) D = \frac{V_{in} (1-D)}{D \cdot R}$$

$$i_{avg} = \frac{V_{in} (1-D)}{D^2 R}$$
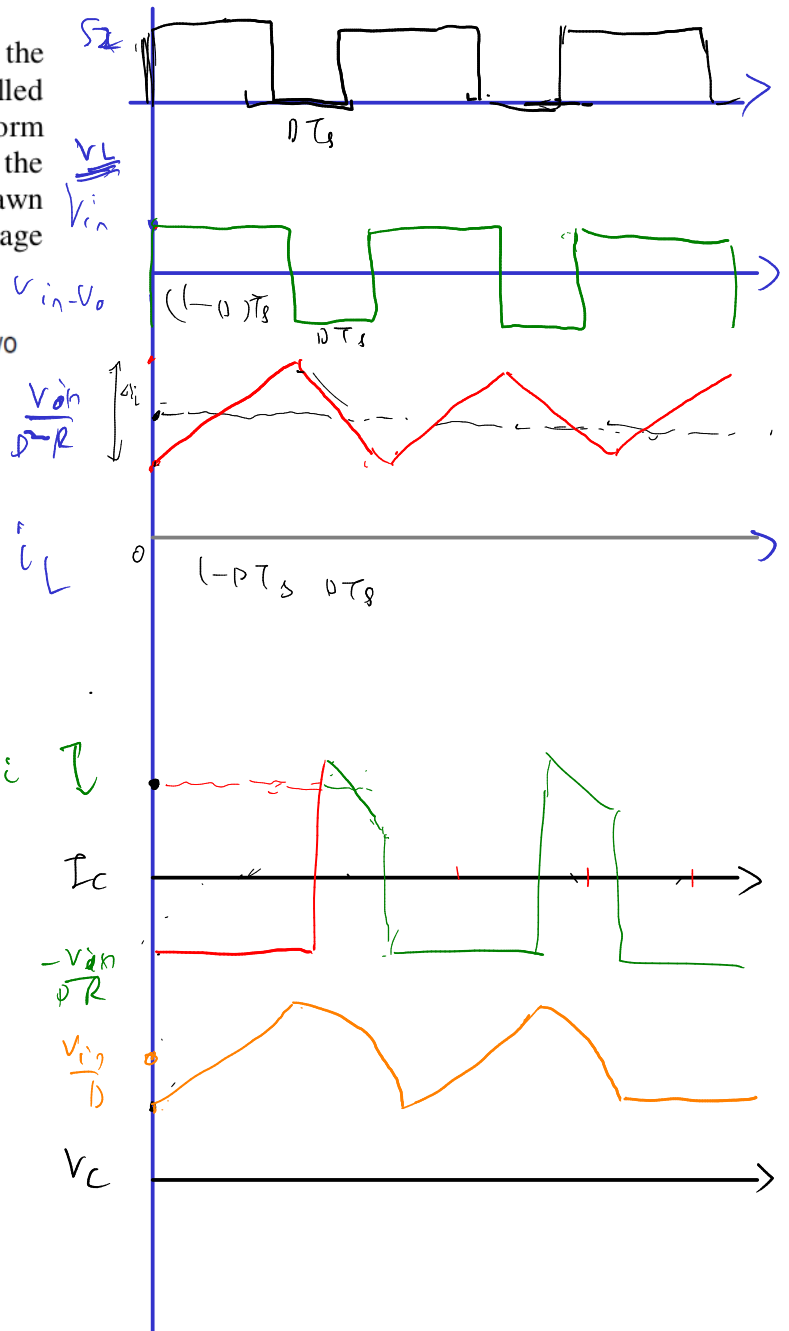
$$\Delta v_{out} = \frac{-V_{in} (1-D) T_s}{D \cdot R \cdot C}$$



### Problem-7

Figure 7 shows the circuit diagram of a type-I (integral) compensated buck converter with output voltage,  $V_{out}$  regulated at 2.5V for input supply,  $V_{DD}=5V$  and load current,  $I_{LOAD}=1A$ . Assuming switches  $S_P$  and  $S_N$  are ideal.

- Model the buck converter in continuous time domain and find the small signal loop gain transfer function.
- Determine the value of capacitor  $C_1$  to achieve the gain margin of  $> 20\text{dB}$  and draw the bode magnitude and phase plot.
- Find the value of control voltage,  $V_{\text{CTRL}}$  and duty cycle,  $D$  to regulate the output voltage at  $2.5\text{V}$ .
- Find the value of peak to peak inductor ripple current and peak-to-peak output ripple voltage.
- Draw the steady state waveforms for PWM voltage ( $V_{\text{PWM}}$ ), switch currents ( $I_P$  and  $I_N$ ), inductor current ( $I_L$ ) and output voltage ( $V_{\text{out}}$ ).

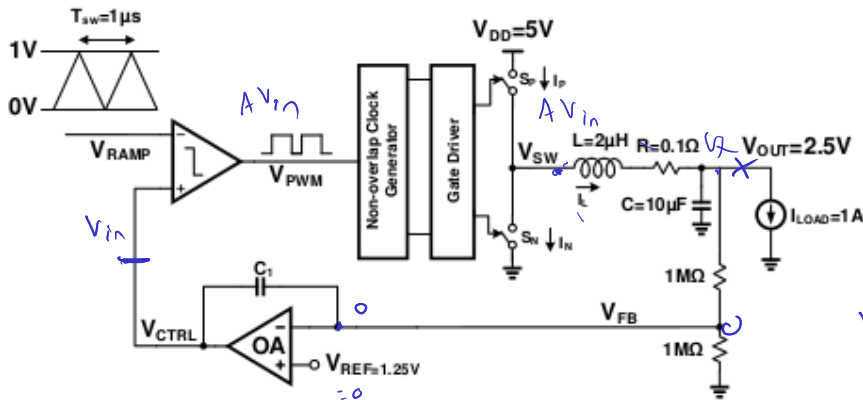


Figure 7: Circuit for Problem-7

$$L_L(s) = \frac{V_{RB} = -1.5}{s \left( \frac{R_1 R C_1}{1} \right) (1 + s^2 LC + R_2 C_2)}$$

1-5

$$(2R, C, ) (1 + 82.2 \times 10^{-11} + 8 \times 10^{-6})$$

$$LH(s) = -90 - \left( (1 - \omega^2) \times 10^{-11} + j\omega 10^{-6} \right)$$

- 180

$$\omega_2 = \frac{1}{2 \times 10^{-11}},$$

$$\omega = 2.2 \times 10^5 \text{ rad s}^{-1}$$

$$u.A = |u(u_{-100})| =$$

$$2.2 \times 10^5 \times 10^{-6} (C) \quad 2.2 \times 10^5 \times 10^{-6}$$

$$10^{-1} C$$

$$F \times 10^{10}$$

$$C = 10^{-9} = 1 \text{ nF}$$

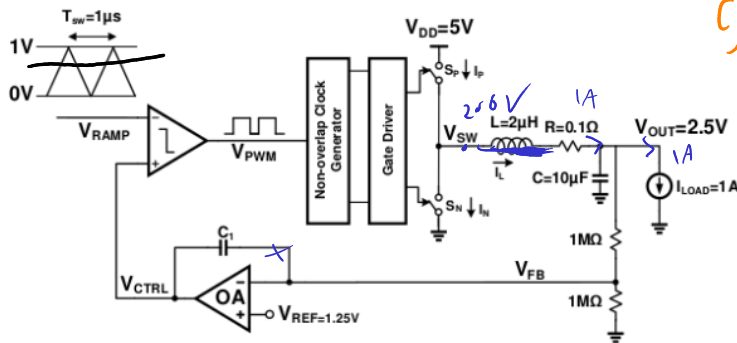


Figure 7: Circuit for Problem-7

$$c) \quad S_D = 2.6$$

$$D = 52\%$$

$$V_{CTRL} = 0.52 \text{ V}$$

- d) Find the value of peak to peak inductor ripple current and peak-to-peak output ripple voltage.




$$\frac{(1-D) V_S (D T_S)}{L}$$

$$= \frac{0.52 \times 0.48 \times 5 \times 10^{-6}}{2 \times 10^{-6}}$$


$$= 0.624 \text{ A}$$

$$\frac{\Delta i_L T_S}{8C} = 7.8 \text{ mV}$$

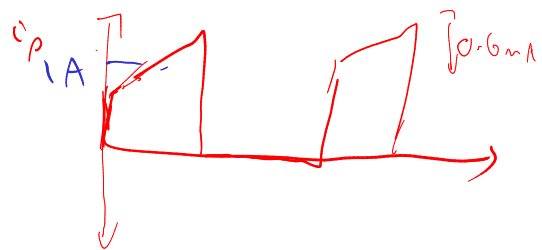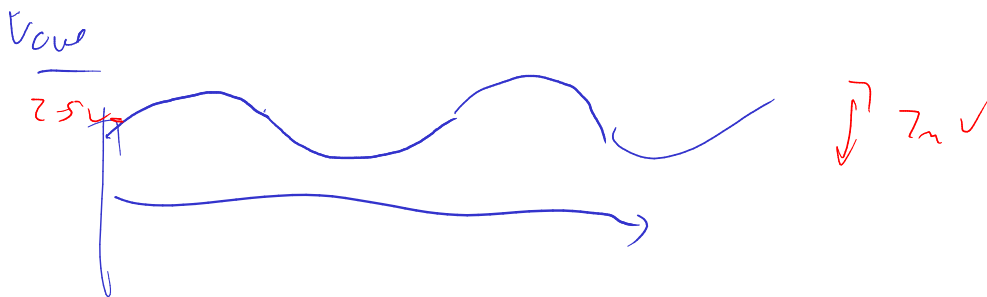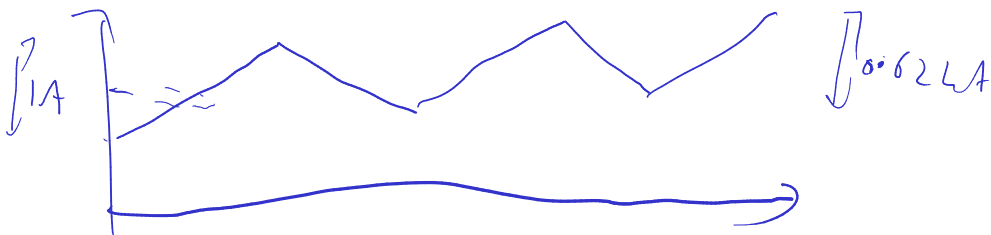- e) Draw the steady state waveforms for PWM voltage ( $V_{PWM}$ ), switch currents ( $I_P$  and  $I_N$ ), inductor current ( $I_L$ ) and output voltage ( $V_{out}$ ).




$\sigma 0.62L_A$

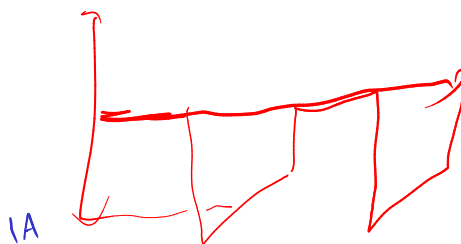

### Problem 3

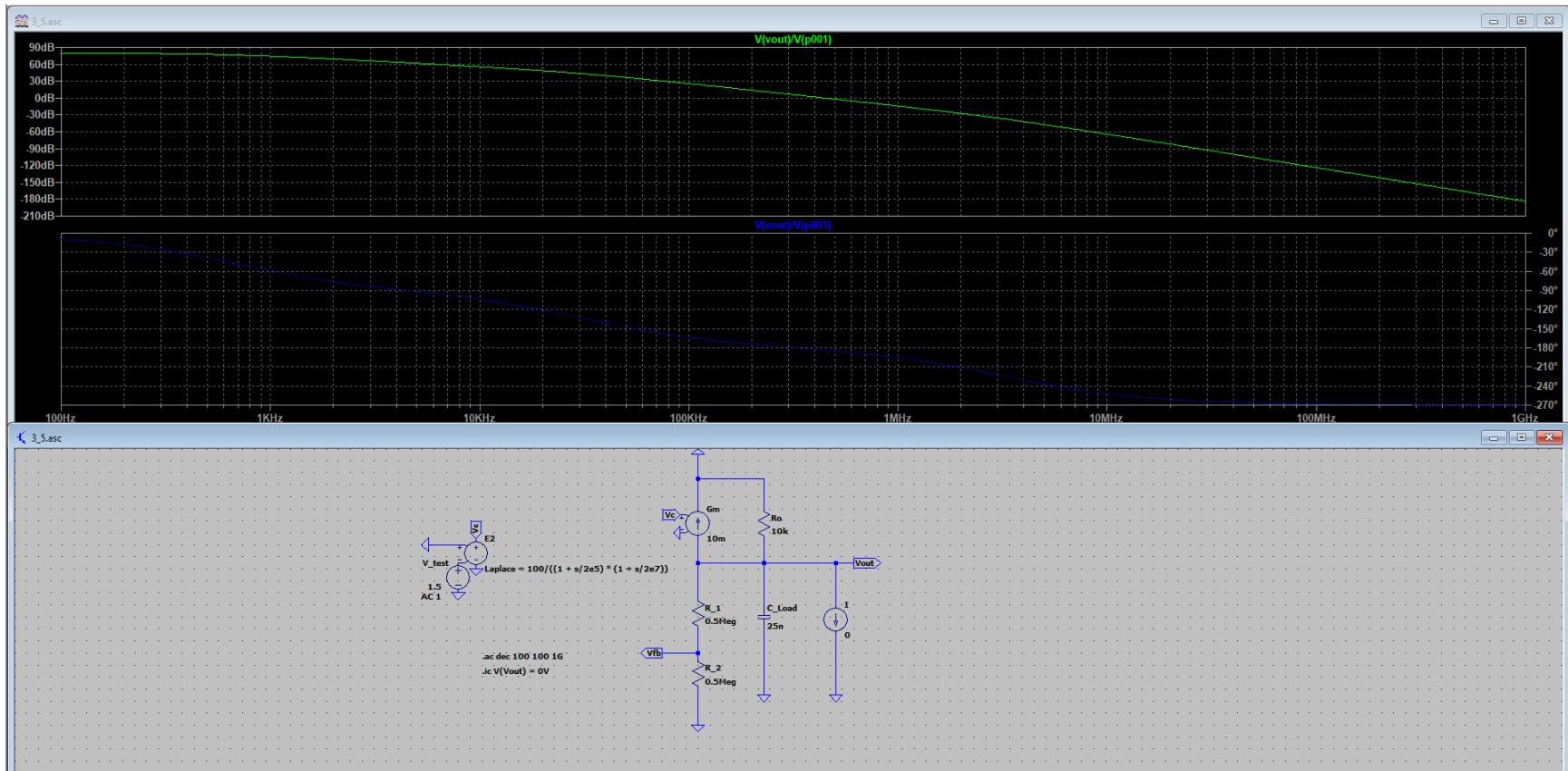Problem 2 circuit is simulated below. Below simulation is for the loop gain. As calculated theoretically, 2.5 nF yields a phase margin of 0, so simulation matches theoretical prediction.




## Problem 4

Vout1 is the output when input is  $v_i$

Vout2 is the output when input is  $v_i'$

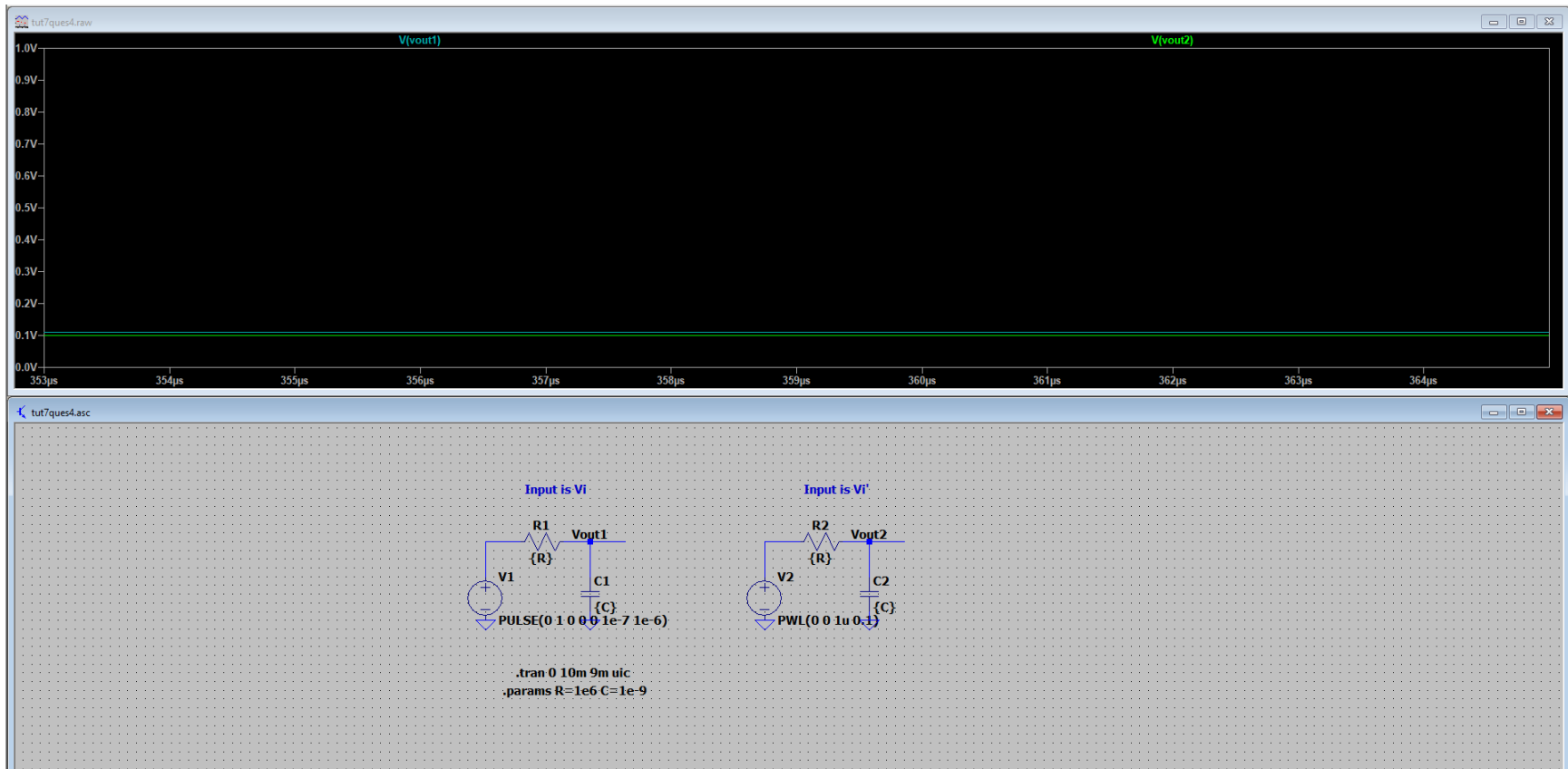
Response of slow LTI system to  $v_i$  is similar to  $v_i'$ . Clearly, it is close to 0.1V in both cases.





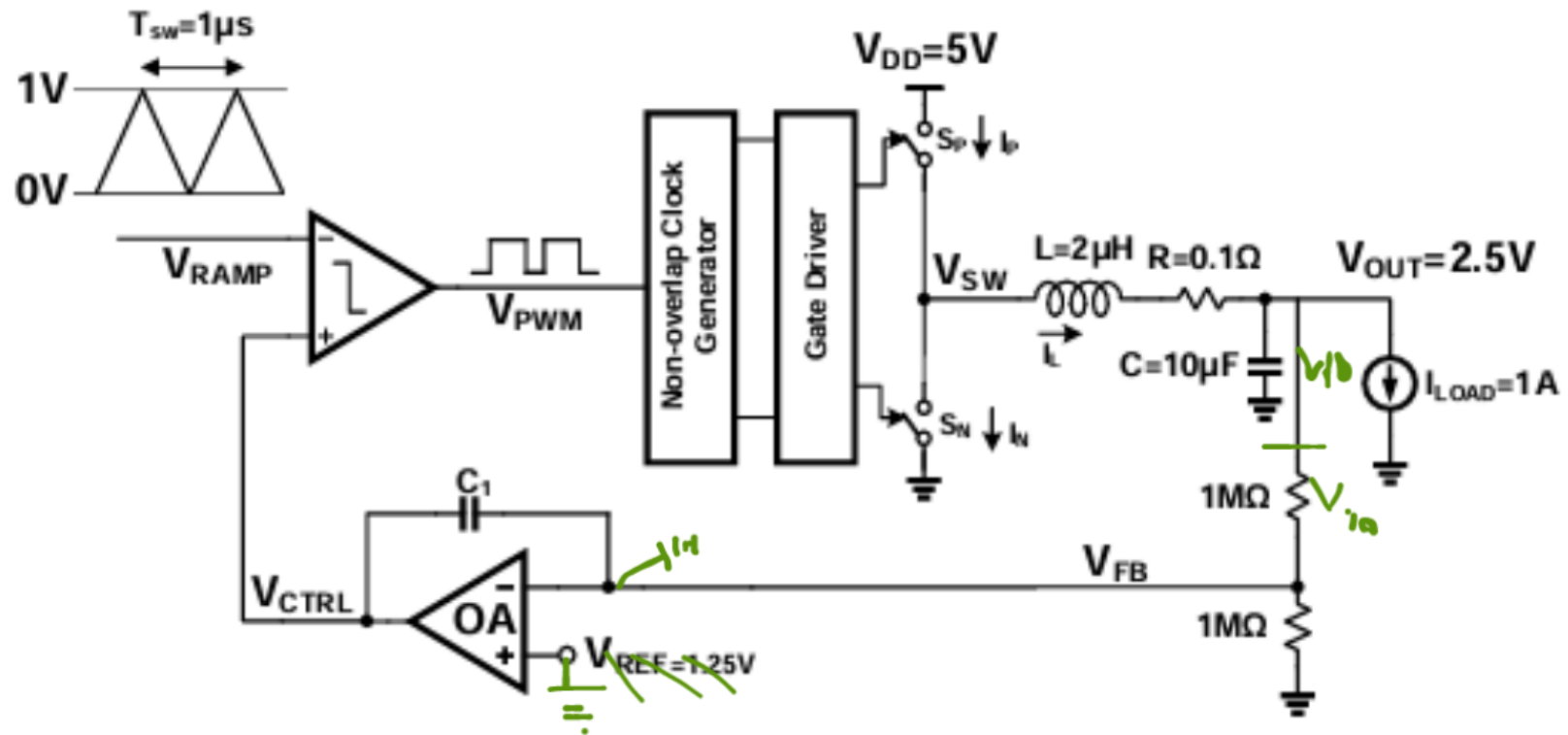
### Problem 8

Below is the loop gain equation, where  $V_{DD} = 0$ ,  $V_{ref} = 0$ ,  $I_{load} = 0$ .



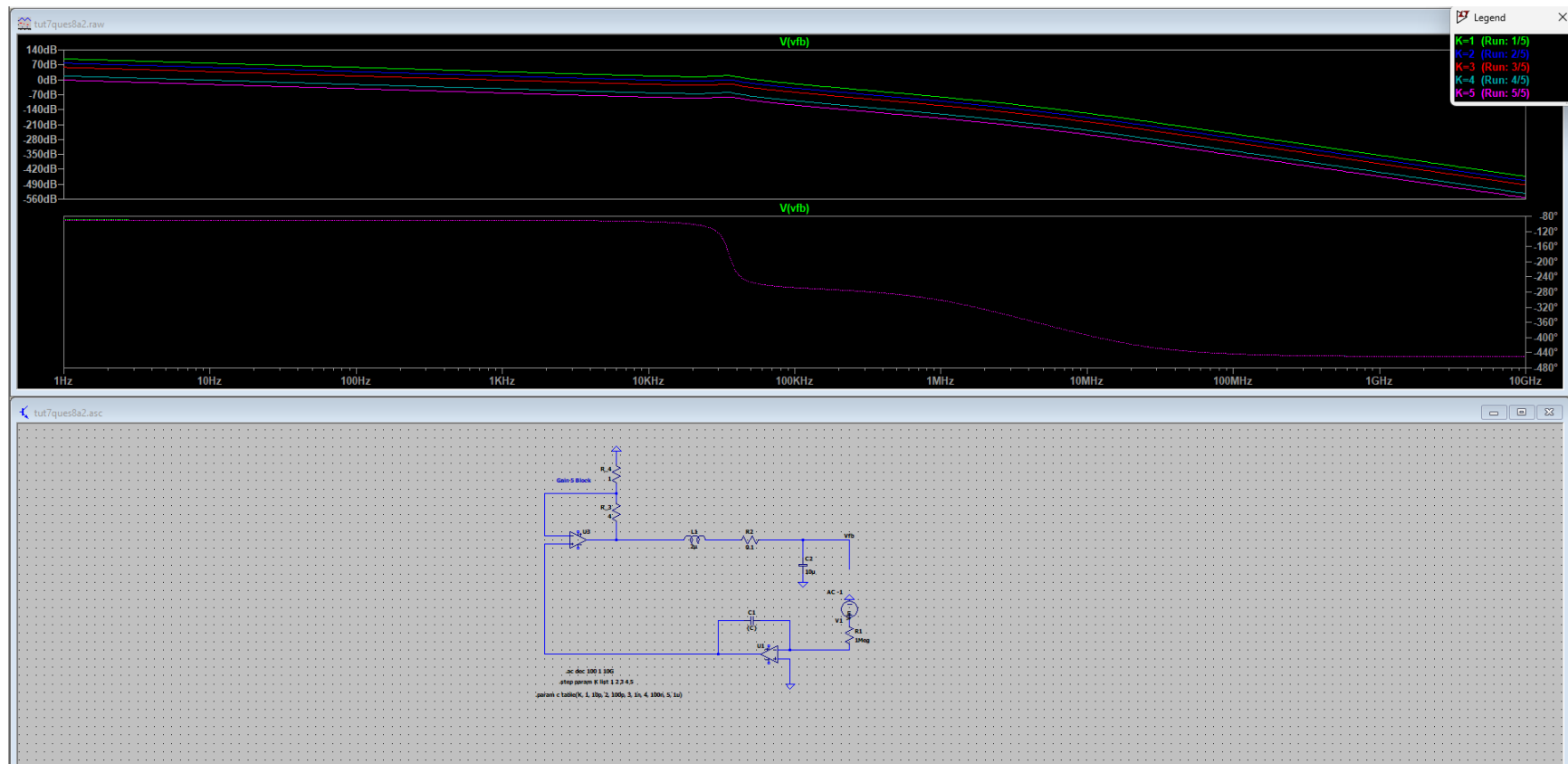
## Problem 8 a)

Below is AC analysis for a range of Capacitor Values, 10p, 100p, 1n, 100n, 1u



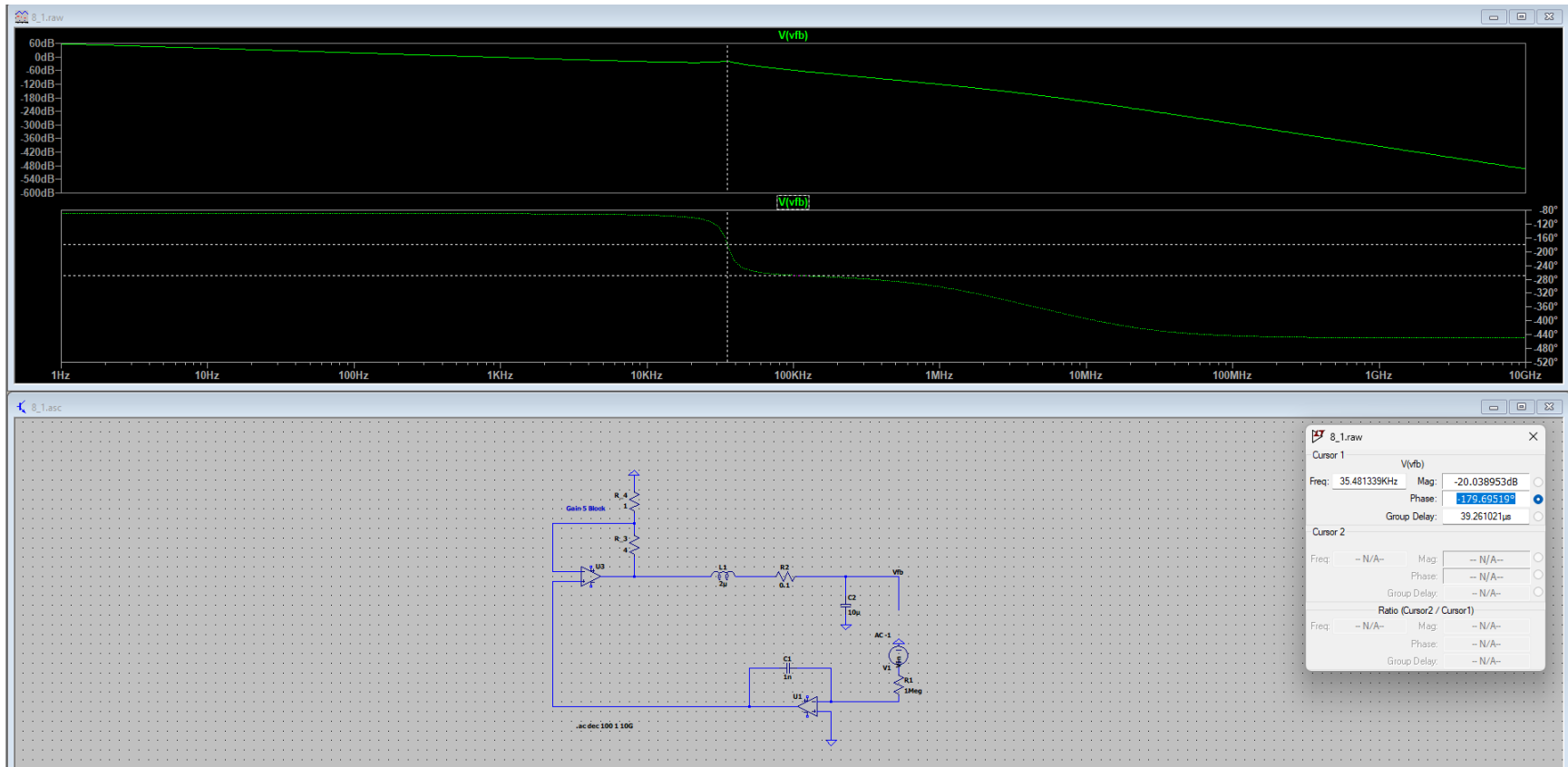**Below is AC analysis at 1n, which achieves gain margin 20dB.**




## Calculation of Q

$\omega_n$  is natural frequency.

Consider the Transfer function of just the RLC circuit. There, the Gain is approximately 13dB. Now, Gain at  $\omega = \omega_n$  is Q.


So,  $20 * \log_{10}(Q) = 13$ .

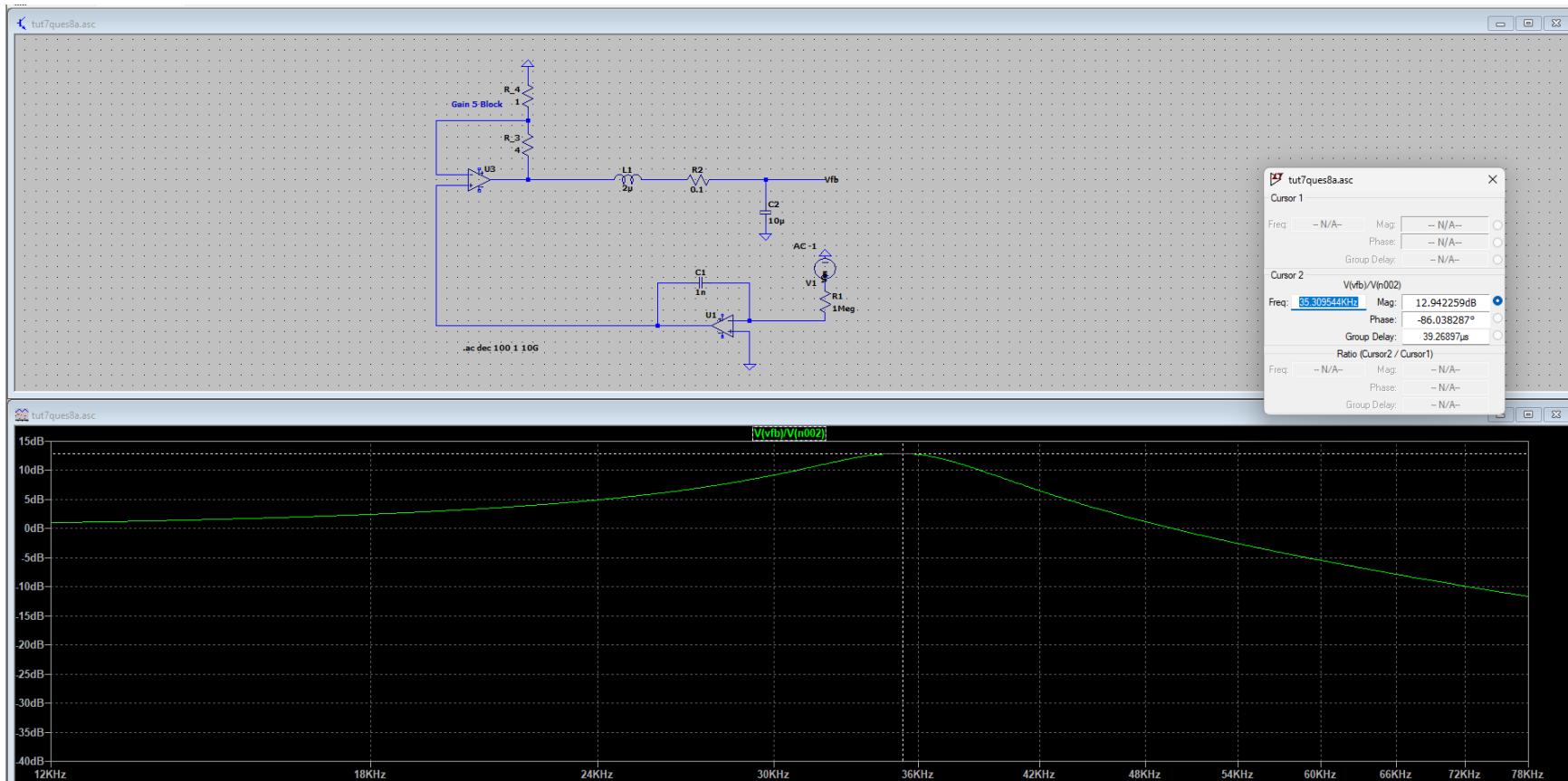Therefore, **Q = 4.46**, which matches with theoretical calculations.




## Problem 8 b)

Vout

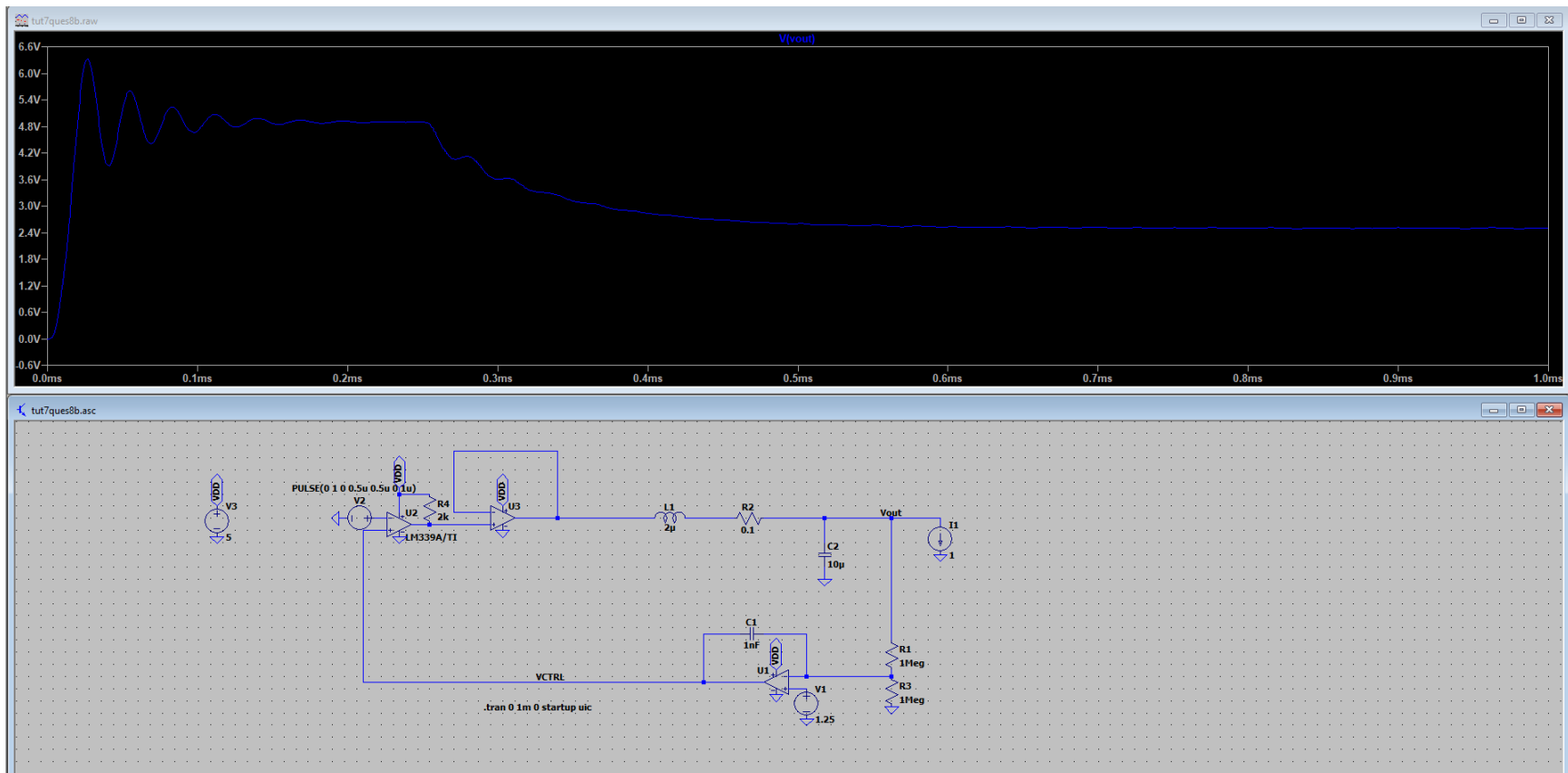

We can observe that  $V_{out}$  has some initial condition, but finally settles down to 2.5 V as expected.


## VCTRL

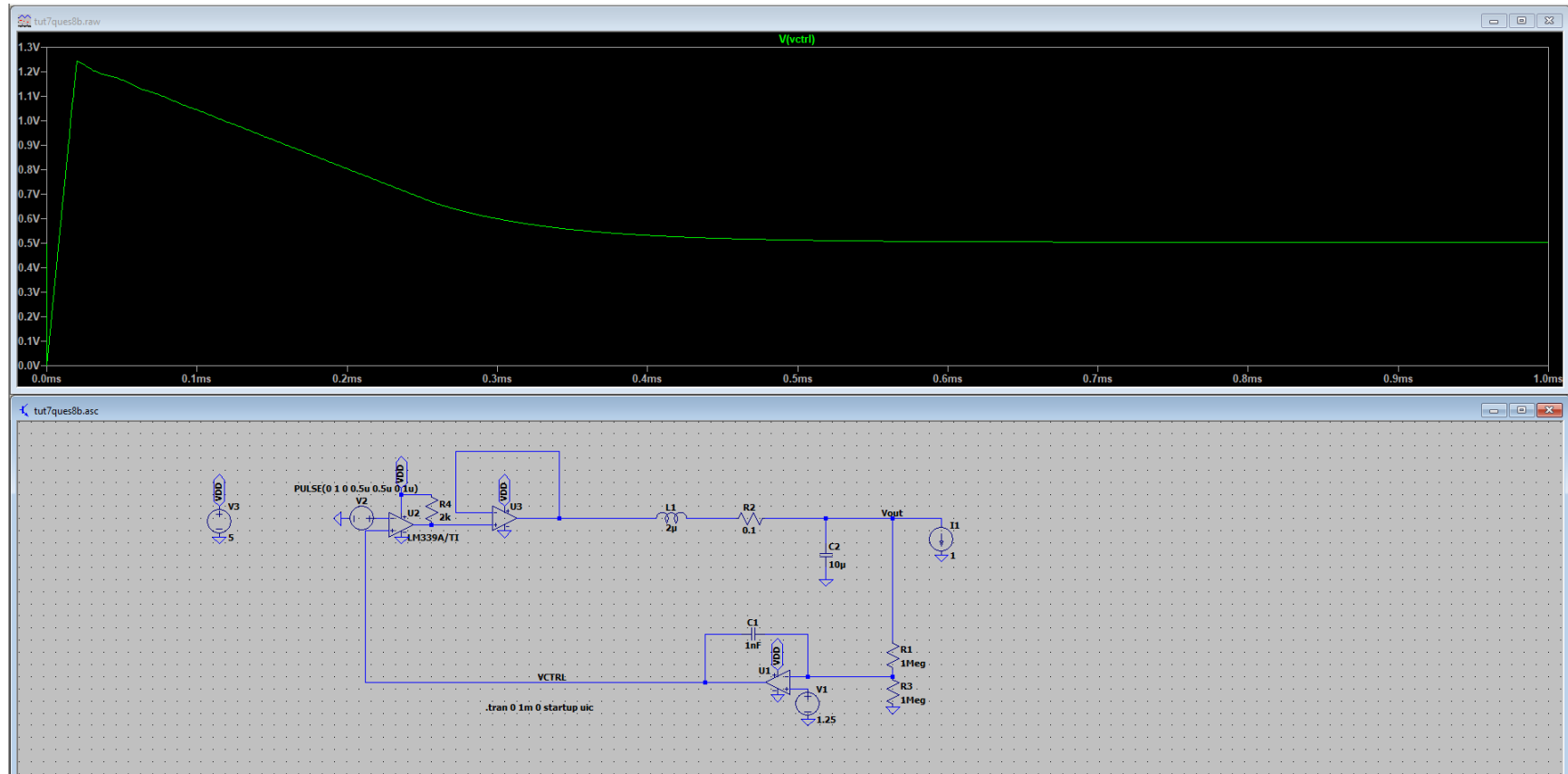

VCTRL also has some initial values, but settles down to 0.52V, as expected by theoretical calculation.


Explanation: c) As calculated theoretically,  $V_{ctrl} = 0.52\text{ V}$ , Duty cycle is 0.52

d) Peak to Peak inductor ripple

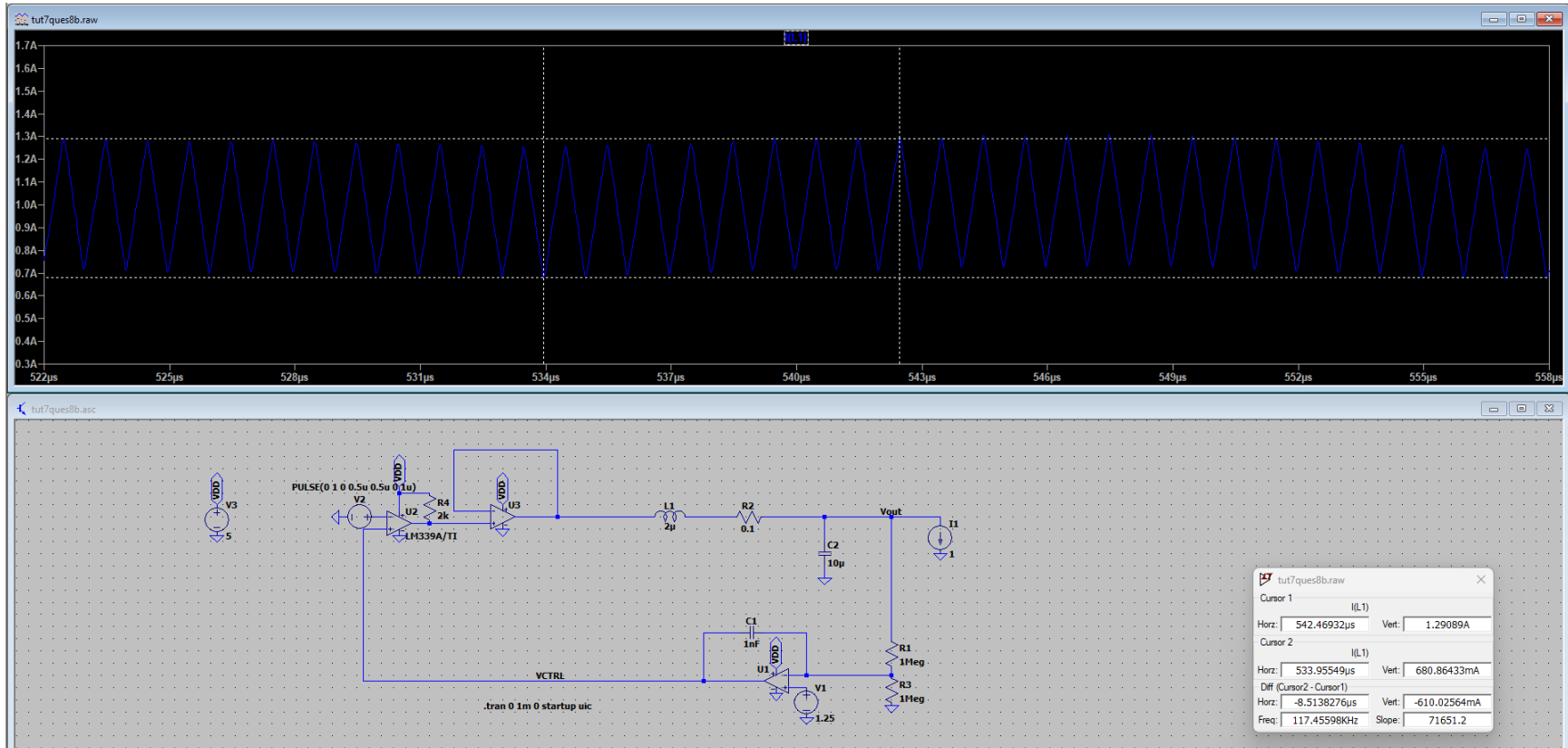

Ripple current is found to be  $1.29\text{ A} - 0.68\text{ A} = 0.6\text{ A}$ , which is similar to theoretical value

e)

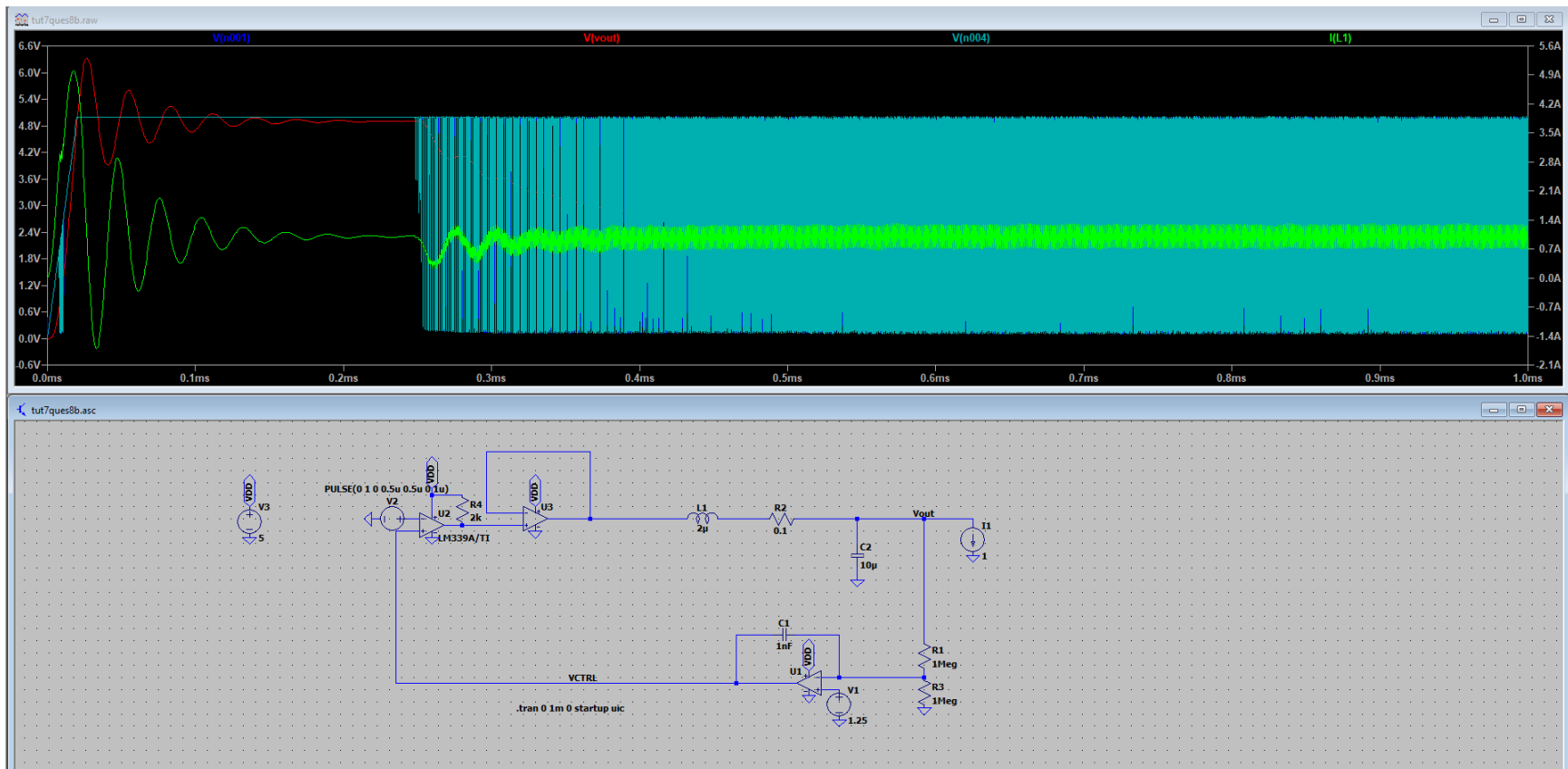

Theoretical predictions match with simulated values