

# ANALOG SYSTEMS : PROBLEM SET 3

IN ALL PROBLEMS IN THIS TUTORIAL, THE OPAMP IS NONIDEAL IN THE SENSE THAT IT HAS FINITE BANDWIDTH. The transfer function of the opamp is given by  $A(s) = \frac{\omega_u}{s}$

## Problem 1

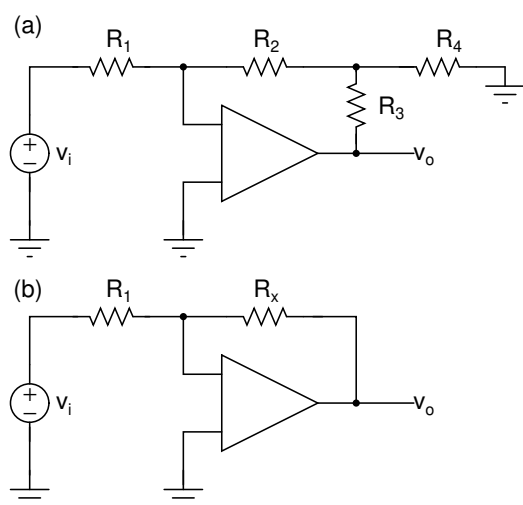


Figure 1: Circuits for Problem 1.

In the circuits above, determine the signs on the opamps for negative feedback operation, and determine the transfer function  $v_o/v_i$ . Consider the case where  $R_x = 100 R_1$ ,  $R_2 = R_1 = R_3$ . Determine  $R_4$  so that both circuits have the same gain. Compare the 3-dB bandwidths achieved for both circuits.

## Problem 2

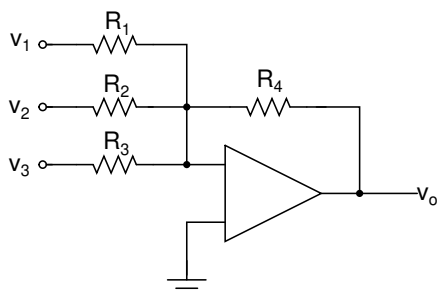


Figure 2: Circuit for Problem 2.

Determine the transfer functions from  $v_1$ ,  $v_2$  and  $v_3$  to  $v_o$ . What is the 3-dB bandwidth of each of these transfer functions?

## Problem 3

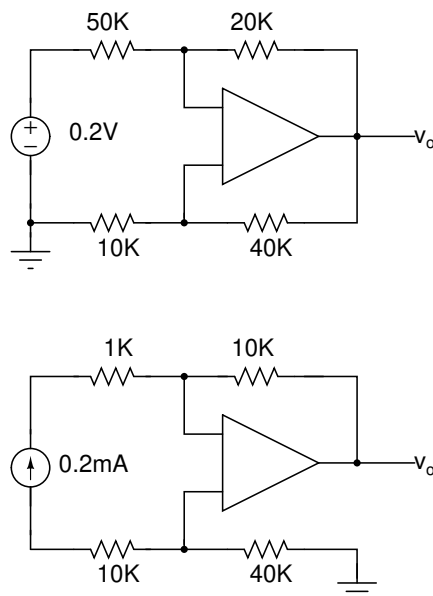


Figure 3: Circuits for Problem 3.

In the circuits above, mark the signs on the opamp for negative feedback operation, and determine the transfer functions from the input sources to  $v_o$ .

## Problem 4

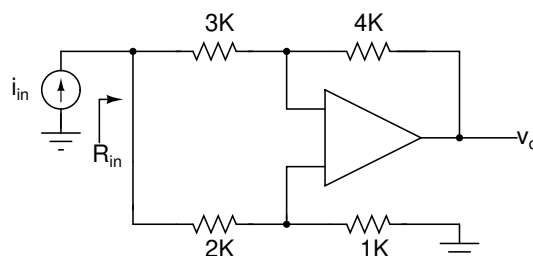


Figure 4: Circuits for Problem 4.

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the transfer function from  $i_{in}$  to  $v_o$ . Determine the input impedance (as a function of frequency) looking in, as denoted by  $R_{in}$ .

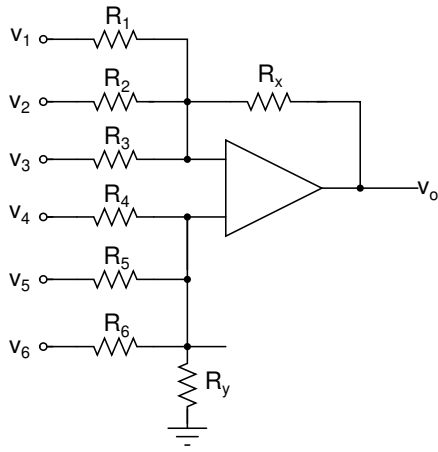


Figure 5: Circuit for Problem 5.

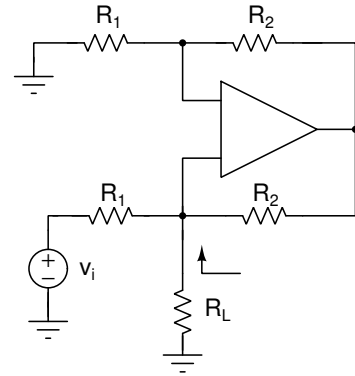


Figure 7: Circuit for Problem 7.

## Problem 5

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the transfer functions to  $v_o$  from  $v_1, \dots, v_6$ .

## Problem 6

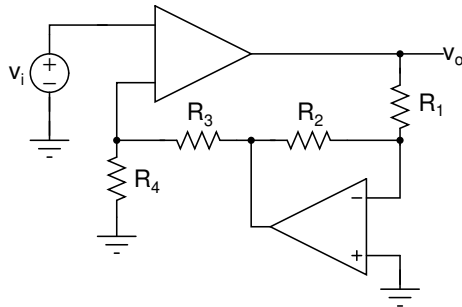


Figure 6: Circuit for Problem 6.

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine  $V_o(s)/V_i(s)$ .

## Problem 7

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the Norton equivalent for the circuit looking across the load resistor  $R_L$ . Remember, that the Norton equivalent will be frequency dependent.

## Problem 8

The figure above shows three different ways of achieving an amplifier with a gain of  $n^2$ , where  $n^2 \gg 1$ . If  $v_{off,1,2} = 0$  and the opamps have infinite gain, all three are equivalent.

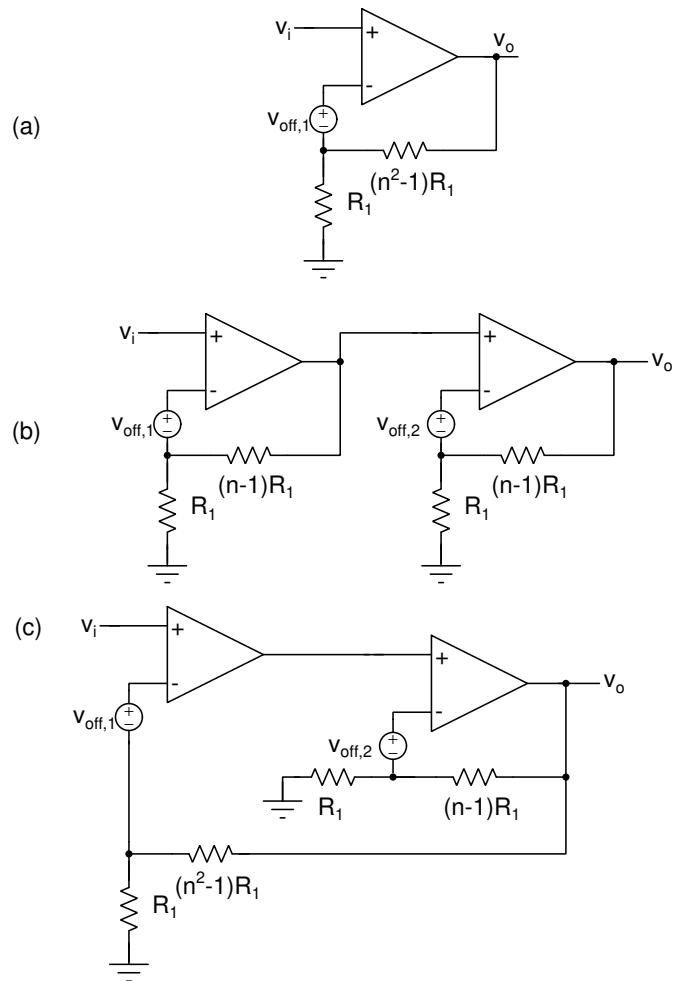


Figure 8: Circuit for Problem 8.

Determine the transfer functions of each of these amplifiers. Assume that the offset voltages are all zero. Which of them has the highest bandwidth?

# Problem 1

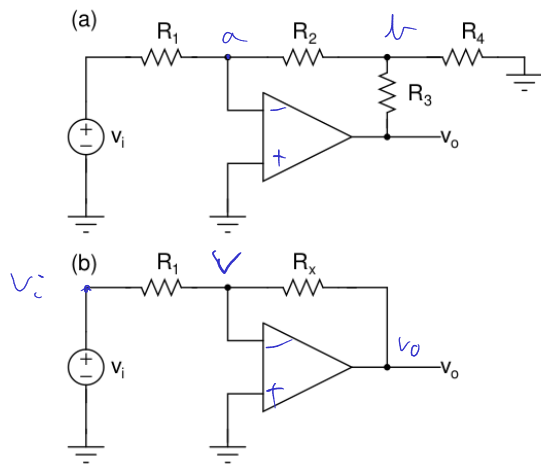


Figure 1: Circuits for Problem 1.

In the circuits above, determine the signs on the opamps for negative feedback operation, and determine the transfer function  $v_o/v_i$ . Consider the case where  $R_x = 100 R_1$ ,  $R_2 = R_1 = R_3$ . Determine  $R_4$  so that both circuits have the same gain. Compare the 3-dB bandwidths achieved for both circuits.

a) To find sign convention, give  $\Delta v$  as input. As potential at point a  $\uparrow$ , a is -ve terminal

b) To find sign convention, give  $\Delta v$  as input. As potential at point  $\checkmark \uparrow$ ,  $\checkmark$  is -ve terminal

$$v_i - a + \frac{b-a}{R_2} = 0$$

$$b - a + \frac{b-v_o}{R_3} + \frac{b}{R_4} = 0$$

$$b = \frac{a}{R_2} + \frac{v_o}{R_3}$$

$$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{b-a}{R_2} = \frac{1}{R_2} \left[ \frac{\frac{v_o}{R_3} - \frac{a}{R_3} - \frac{a}{R_4}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right]$$

$$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \left( \frac{v_i}{R_1} + \frac{1}{R_2} \left[ \frac{\frac{v_o}{R_3} - \frac{a}{R_3} - \frac{a}{R_4}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right] \right) = \frac{a}{R_2} \left( \frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{a}{R_1} \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$\left( \frac{v_i}{R_1} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{v_o}{R_2 R_3} \right) \frac{1}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_1} \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)} = a$$

$$v_o = -\omega_y a = -\omega_y \left( \frac{v_i}{R_1} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{v_o}{R_2 R_3} \right) \frac{1}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_1} \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)}$$

$$\frac{v_o}{\left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_1} \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) \right) \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{R_2 R_3}} = \frac{v_i}{R_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$-\omega_y \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right) + \omega_y \left( \frac{1}{R_2 R_3} + \frac{1}{R_3} + \frac{1}{R_1 R_2} \right)$$

$$T1 \quad R_1 = R_2 = R_3$$

$$A(s) = \frac{-1 - \frac{1}{3} + \frac{2R_1}{R_4}}{\frac{2}{\omega_u} + \frac{1}{R_1} \left( \frac{2}{R_1} + \frac{1}{R_4} \right)}$$

$$b) \quad V_o = \frac{\omega_u}{s} (-V)$$

$$V_o = -\frac{\omega_u}{s} \left[ \frac{V_i + V_o}{\frac{1}{R_1} + \frac{1}{R_x}} \right] \quad \left( \frac{1}{R_1} + \frac{1}{R_x} \right)$$

$$\left( \frac{1}{R_1} + \frac{1}{R_x} \right) \frac{\omega_u}{s} V_o - \frac{V_o}{R_x} = \frac{V_i}{R_1}$$

$$\frac{V_o}{V_i} = -\frac{1}{R_1} \frac{1}{\left( \left( \frac{\omega_u}{s} \right) \left( \frac{1}{R_1} + \frac{1}{R_x} \right) + \frac{1}{R_x} \right)}$$

$$I) \quad R_x = 100R_1$$

$$\frac{R_1}{R_x} = 98$$

$$a) \quad \omega_{-3dB} = \frac{\omega_u}{199} \rightarrow \text{Smaller}$$

$$b) \quad \omega_{-3dB} = \frac{\omega_u}{101} \rightarrow \text{bigger}$$

## Problem 2

Sign conventions are taken for ensure -ve feedback.

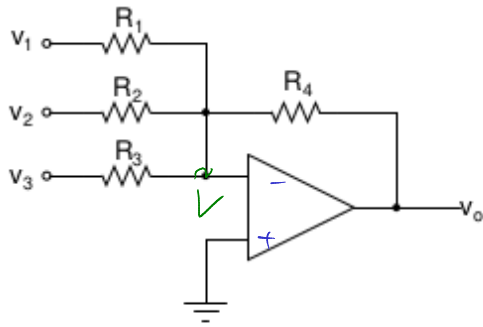


Figure 2: Circuit for Problem 2.

Determine the transfer functions from  $v_1$ ,  $v_2$  and  $v_3$  to  $v_o$ . What is the 3-dB bandwidth of each of these transfer functions?

$$\frac{v_1 - v}{R_1} + \frac{v_2 - v}{R_2} + \frac{v_3 - v}{R_3} + \frac{v_4 - v}{R_4} = 0$$

$$\frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3} + \frac{v}{R_4} = v$$

$$v_o = -\omega_c v \left( \frac{\frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right) (-\omega_c)$$

$$-\frac{1}{\omega_c} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] v_o = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3} + \frac{v}{R_4}$$

$$v_o \left[ -\frac{1}{\omega_c} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_4} \right] = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$

$$\frac{V_o}{V_i} = \frac{-\frac{1}{R_1}}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{1}{R_4}}$$

$V_2 = 0$   
 $V_3 = 0$

$\omega_{3dB}$

$$\omega_{3dB} = \frac{1}{R_4} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

By symmetry,

$$\omega_{3dB}(A) = \omega_{3dB}(B) = \omega_{3dB}(C)$$

### Problem 3

Consider  $\Delta v_{\text{input}} - A \Delta v$  is caused at the output: As potential at pt a  $\uparrow$ , it is at higher potential

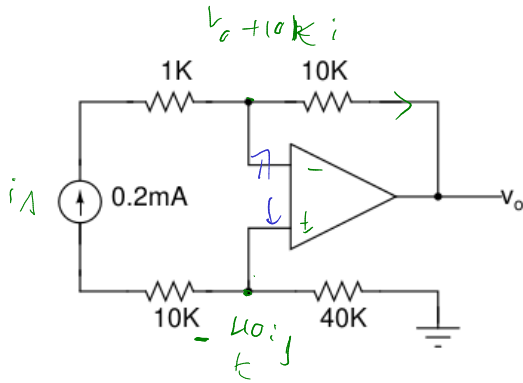
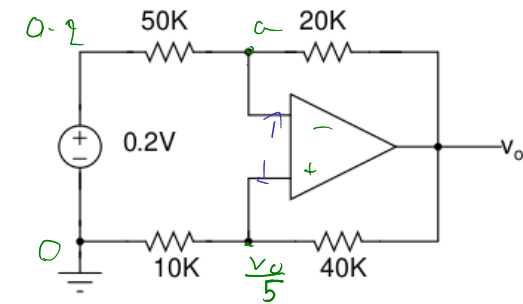


Figure 3: Circuits for Problem 3.

In the circuits above, mark the signs on the opamp for negative feedback operation, and determine the transfer functions from the input sources to  $v_o$ .

$$\frac{a - 0.2}{5} + \frac{a - v_o}{2} = 0$$

$$v_o = + \frac{w_u}{s} \left[ \frac{v_o}{5} - a \right]$$

$$v_o = \frac{w_u}{3} \left[ \frac{v_o}{5} - \left( \frac{v_i}{\frac{1}{5}} + \frac{v_o}{2} \right) \right]$$

$$v_o \left[ \frac{7}{10} \frac{s}{w_u} \right] = \frac{v_o}{5} \left[ \frac{3}{10} \right] + \left( \frac{v_i}{7} + \frac{v_o}{2} \right)$$

$$v_o \left[ \frac{7}{10} \frac{s}{w_u} \right] = v_o \left[ \frac{-3}{10} \right] - \frac{v_i}{5}$$

$$v_o \left[ \frac{7}{10} \frac{s}{w_u} + \frac{3}{10} \right] = -\frac{v_i}{5}$$

$$= \boxed{\frac{+10 w_u}{3s + 18w_u}}$$

$$v_o = \frac{w_u}{s} \left[ -40K i_s - (v_o + 10K i_s) \right]$$

$$\frac{8v_o}{w_u} = i_s \left[ -50K \right]$$

$$v_o \left[ \frac{s}{w_u} + 1 \right] = i_s (-50K)$$

$$\frac{v_o}{i_s} = \boxed{\frac{-50K w_u}{s + w_u}}$$



## Problem 4

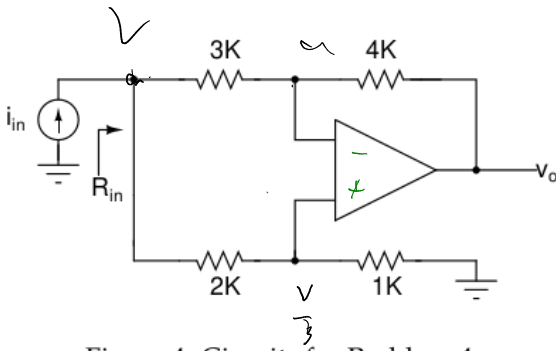


Figure 4: Circuits for Problem 4.

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the transfer function from  $i_{in}$  to  $v_o$ . Determine the input impedance (as a function of frequency) looking in, as denoted by  $R_{in}$ .

To find sign convention,

assume  $i_{in} = 0$ , so potential at point a  $\uparrow$ , so a is -ve terminal

$$a - \frac{v_o}{4} + a - \frac{v}{3} = 0$$

$$v_o = A \left[ \frac{v}{3} - a \right] = A \left[ \frac{v}{3} - \left( \frac{v_o}{4} + \frac{v}{3} \right) \right]$$

$$= A \left( \frac{v}{3} - \frac{(3v_o + 4v)}{12} \right)$$

$$v_o = A \left[ \frac{7v - 3v_o - 4v}{12} \right] = A \left[ \frac{-5v - 3v_o}{12} \right]$$

$$i_{in} = \frac{v}{3k} + \frac{v - v_o}{7k}$$

$$T_i(s) = \frac{v_o}{i_{in}} = \frac{-78 \text{ k}}{\frac{6}{7k} + \frac{1}{A}}$$

$$A = \frac{\omega_c}{s}$$

$$R_{in} = \frac{v}{i_{in}} = \frac{1638 \text{ k} + \frac{2}{s}}{71.5} T_i(s)$$

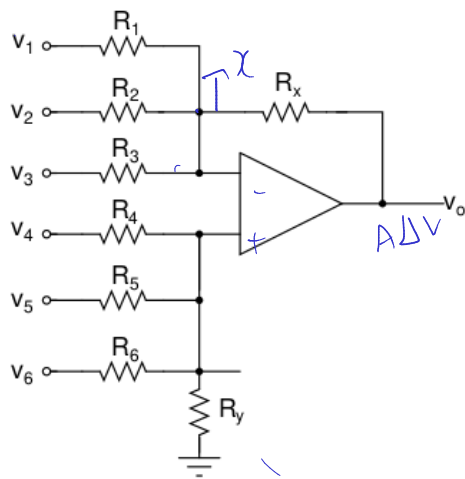


Figure 5: Circuit for Problem 5.

## Problem 5

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the transfer functions to  $v_o$  from  $v_1, \dots, v_6$ .

Assume  $\Delta V$  input.  $v_o = A\Delta V$ ,  
 so potential at pt.  $x$  is  $\Delta V$ ,  
 so  $x$  has to be -ve terminal

$$\frac{x - v_1}{R_1} + \frac{x}{R_2} + \frac{x}{R_3} + \frac{x - v_o}{R_x} = 0$$

$$x = \frac{v_1}{R_1} + \frac{v_o}{R_x}$$

---


$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x}$$

$$v_o = -Ax$$

$$v_o = -A \left( \frac{\frac{v_1}{R_1} + \frac{v_o}{R_x}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x}} \right)$$


$$V_0 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} \right] = -A \left( \frac{V_{i1}}{R_1} + \frac{V_0}{R_x} \right)$$

$$V_0 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} + A \right] = -A \frac{V_{i1}}{R_1}$$

$$\frac{V_0}{V_{i1}} = \frac{-A}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} + A}$$

$$\frac{V_0}{V_{i2}} = \frac{-A}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} + A}$$
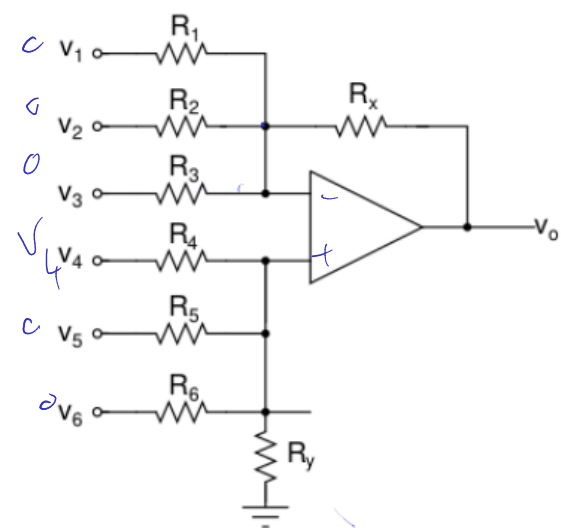
$$\frac{V_0}{V_{i3}} = \frac{-A}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} + A}$$



$$R_{11} = R_5 \parallel R_6 \parallel R_y$$

$$R' = R_1 \parallel R_2 \parallel R_3$$

$$V_+ = V_4 \frac{R_{11}}{R_{11} + R_4}$$

$$V_- = \frac{V_o R_x}{R' + R_x}$$

$$\frac{V_o}{A} = \left[ \frac{V_4 R_{11}}{R_{11} + R_4} - \frac{V_o R_x}{R' + R_x} \right]$$

$$V_4 \left[ \frac{1}{A} + \frac{R_x}{R' + R_x} \right] = \frac{V_4 R_{11}}{R_{11} + R_4}$$

$$\frac{V_o}{V_4} = \frac{\frac{R_{11}}{R_{11} + R_4}}{\frac{1}{A} + \frac{R_x}{R' + R_x}}$$

$$R' = R_1 \parallel R_2 \parallel R_3$$

$$R_{11} = R_5 \parallel R_6 \parallel R_y$$

$$\frac{V_o}{V_5} = \frac{\frac{R_{11}}{R_{11} + R_5}}{\frac{1}{A} + \frac{R_x}{R' + R_x}}$$

$$R' = R_1 \parallel R_2 \parallel R_3$$

$$R_{11} = R_4 \parallel R_6 \parallel R_y$$

$$\frac{V_o}{V_6} = \frac{\frac{R_{11}}{R_{11} + R_6}}{\frac{1}{A} + \frac{R_x}{R' + R_x}}$$

$$R' = R_1 \parallel R_2 \parallel R_3$$

$$R_{11} = R_4 \parallel R_5 \parallel R_y$$

## Problem 6

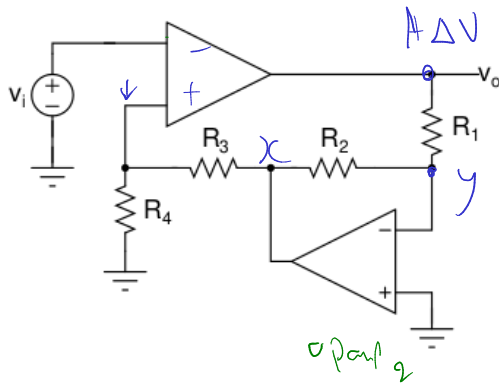


Figure 6: Circuit for Problem 6.

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine  $V_o(s)/V_i(s)$ .

To find sign, assume ideality.  
Give  $\Delta V$  input. As opamp 2 is inverting, potential at pt. x ↓, so  $V_+ \downarrow$ , so  $V_x$  is the terminal.

$$\frac{y - v_o}{R_1} + \frac{y - x}{R_2} = 0$$

$$x = +A(-y) = -(A_0 y)$$

$$-x = +A \left[ \frac{v_o}{R_1} + \frac{x}{R_2} \right]$$

$$-\frac{x}{A} \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{v_o}{R_1} + \frac{x}{R_2}$$

$$-x \left[ \frac{1}{A} \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] + \frac{1}{R_2} \right] R_1 = v_o$$

$$v_o = -A \left[ v_i - \frac{R_1 x}{R_3 + R_4} \right]$$

$$v_o = - \left[ A v_i + \left( \frac{R_4}{R_3 + R_4} \right) \frac{v_o}{\frac{1}{A} \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] + \frac{1}{R_2}} \right]$$


$$-\frac{v_o}{A} = v_i + \left( \frac{R_4}{R_3 + R_4} \right) v_o \frac{1}{R_1 + \frac{1}{A} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{R_2}}$$

$$-v_o \left[ \frac{1}{A} + \left( \frac{R_4}{R_3 + R_4} \right) \frac{1}{R_1} \frac{1}{\left( \frac{1}{A} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{R_2} \right)} \right] = v_i$$

$$\frac{v_o}{v_i} = - \frac{1}{\left[ \frac{1}{A} + \left( \frac{R_4}{R_3 + R_4} \right) \frac{1}{R_1} \frac{1}{\left( \frac{1}{A} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{R_2} \right)} \right]}$$
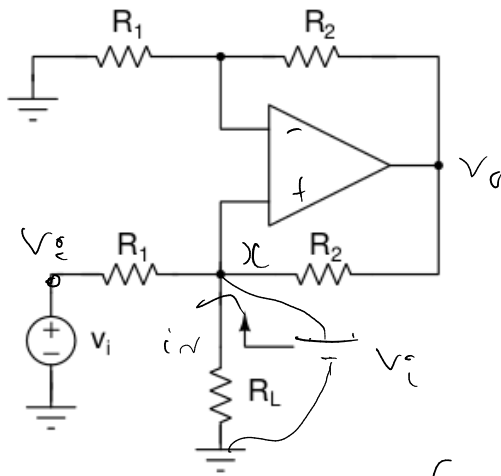
## Problem 7

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the Norton equivalent for the circuit looking across the load resistor  $R_L$ . Remember, that the Norton equivalent will be frequency dependent.



$$\frac{x - V_i}{R_1} + x \frac{1}{R_2} + \frac{x}{R_L} = 0$$

$$V_o = A \left[ x - \frac{R_1}{R_1 + R_2} V_o \right]$$

$$V_o \left[ \frac{1}{A} + \frac{R_1}{R_1 + R_2} \right] = x$$

$$x \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right] = \frac{V_i}{R_1} + \frac{V_o}{R_2}$$


$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right) x = \frac{V_i}{R_1} + \frac{1}{R_2} \left( \frac{x}{\frac{1}{A} + \frac{R_1}{R_1 + R_2}} \right)$$

$$x \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} - \frac{1}{R_2} \left( \frac{1}{\frac{1}{A} + \frac{R_1}{R_1 + R_2}} \right) \right] = \frac{V_i}{R_1}$$

$$\frac{x}{R_L} = \frac{V_i}{R_1 R_L} \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} - \frac{1}{R_2} \left( \frac{1}{\frac{1}{A} + \frac{R_1}{R_1 + R_2}} \right)}$$

$$R_L \rightarrow 0$$

$$I_N = \boxed{\frac{V_i}{R_1}}$$

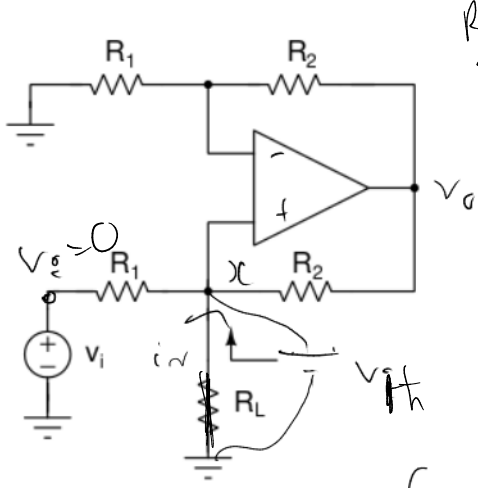

$$V_0 = A \left[ V_{th} - \frac{R_1}{R_1 + R_2} V_0 \right]$$

$$V_0 \left[ 1 + \frac{R_1}{R_1 + R_2} \right] = V_{th}$$

$$i_N + \frac{V_{th} - V_0}{R_2} + \frac{V_{th}}{R_1} = 0$$

$$i_N = \frac{V_{th} - V_0}{R_2} + \frac{V_{th}}{R_1}$$

$$i_N = V_{th} \left[ \frac{1}{R_2} - \frac{1}{R_2} \left[ \frac{1}{1 + \frac{R_1}{R_1 + R_2}} \right] + \frac{1}{R_1} \right]$$

$$R_{th} =$$

$$\frac{1}{\frac{1}{R_2} - \frac{1}{R_2} \left[ \frac{1}{1 + \frac{R_1}{R_1 + R_2}} \right] + \frac{1}{R_1}}$$




## Problem 8

The figure above shows three different ways of achieving an amplifier with a gain of  $n^2$ , where  $n^2 \gg 1$ . If  $v_{off,1,2} = 0$  and the opamps have infinite gain, all three are equivalent.

2

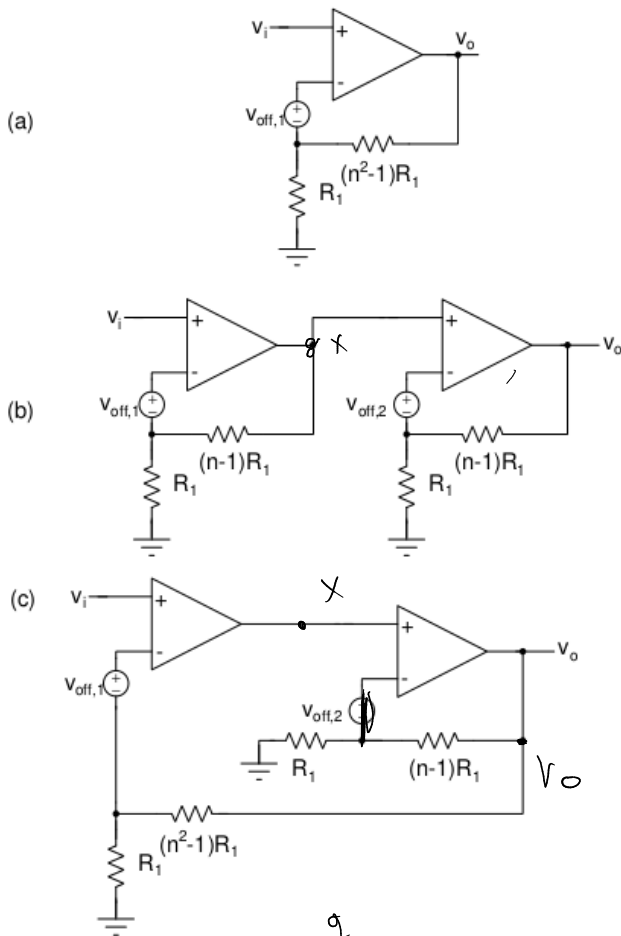Determine the transfer functions of each of these amplifiers. Assume that the offset voltages are all zero. Which of them has the highest bandwidth?



$$v_o = A \left[ v_i - \frac{v_o}{n^2} \right]$$

$$v_o \left[ \frac{1}{A} + \frac{1}{n^2} \right] = v_i$$

$$\frac{v_o}{v_i} = \frac{1}{\frac{1}{A} + \frac{1}{n^2}} \quad \boxed{\omega = \omega_u \frac{1}{n^2}}$$

$$x = v_i / \left[ \frac{1}{A} + \frac{1}{n} \right]$$

$$v_o = x / \left[ \frac{1}{A} + \frac{1}{n} \right]$$

$$v_o = v_i \quad \boxed{\omega = \omega_u (\sqrt{2}-1)^{1/n}}$$

$$\frac{v_o}{v_i} = \frac{1}{\left( \frac{1}{A} + \frac{1}{n} \right)^2}$$

$$v_o = A \left[ x - \frac{v_o}{n} \right]$$

$$x = A \left[ v_i - \frac{v_o}{n^2} \right]$$

$$v_o = A \left[ \left( v_i - \frac{v_o}{n^2} \right) - \frac{v_o}{nA} \right]$$

$$v_o \left[ \frac{1}{A^2} + \frac{1}{n^2} + \frac{1}{nA} \right] = v_i$$

$$\frac{v_o}{v_i} = \frac{1}{A^2 + n^2 + nA}$$

$$\omega_u^2 \frac{1}{8n^2} \cdot \frac{1}{A^2 + n^2 + nA} = 0$$

$$\omega_c^2 + 8L n^2 + 8\omega_c n = 0$$

$$\omega_c^2 - \omega_n^2 + j\omega_c \omega_n = 0$$

$$- \omega_c \omega_n = \omega_c^2 - \omega_n^2$$

$$\omega_n^2 - \omega_c \omega_n - \omega_c^2 = 0$$

$$\omega = \frac{\omega_c \pm \sqrt{\omega_c^2 + 4\omega_c^2}}{2}$$

$$\omega = \frac{\omega_c}{n} \left[ \frac{-1 \pm \sqrt{5}}{2} \right]$$

Assume large value of  $n$ , so  $\omega_1, \omega_2, \omega_3$

(3) Has highest 3dB bandwidth