

ANALOG SYSTEMS : PROBLEM SET 9

Problem 1

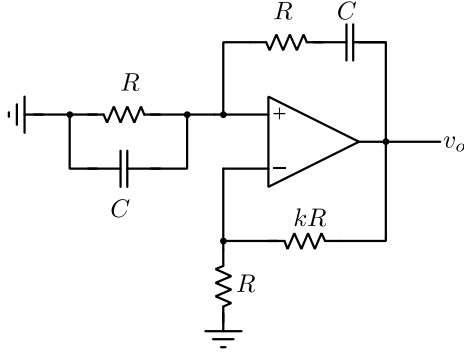


Figure 1: Circuit for Problem 1.

Fig. 1 shows a sinewave oscillator. Determine k so that it just begins to oscillate. All opamps are ideal.

Problem 2

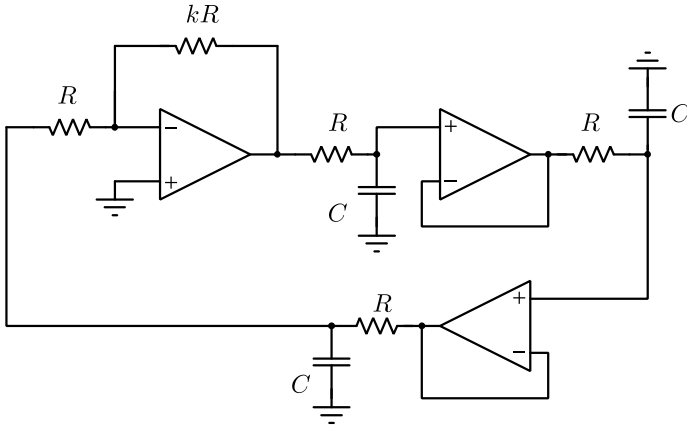


Figure 2: Circuit for Problem 2.

All opamps are ideal in Fig. 2. Determine k so that it just begins to oscillate.

Problem 3

Repeat for the circuit of Fig. 3.

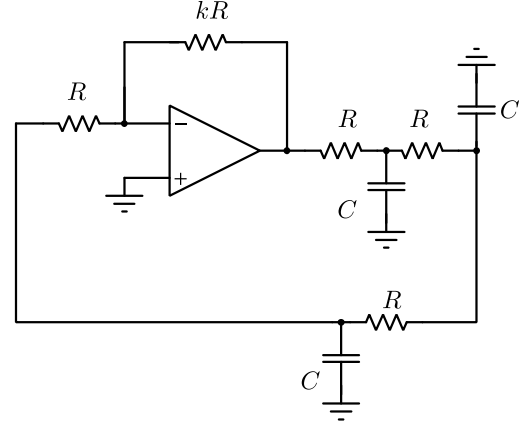


Figure 3: Circuit for Problem 3.

Problem 4

Fig. 4(a) shows an LCR network with a limiting VCCS. The Q of the RLC parallel network can be assumed to be $\gg 1$. The characteristic of the VCCS is shown in Fig. 4(b). The slope of the VCCS is denoted by G_1 and the maximum/minimum current it can source/sink is given by $\pm I_{max}$.

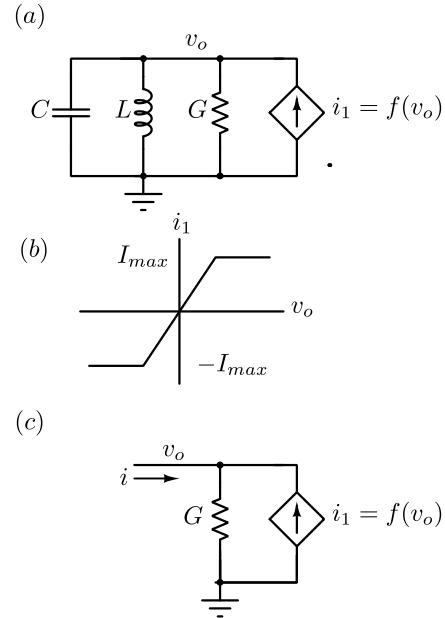


Figure 4: Circuit for Problem 4.

Determine the condition on G_1 for oscillation to start up. Assuming that this condition is satisfied, draw the $i - v_o$ characteristic of the element shown in Fig. 4(c). Assume

that $v_o = A \sin(\omega t)$. Determine and plot the amplitude of the fundamental component of the current i as A is varied from 0 to ∞ . What will be amplitude of oscillation of the circuit in part (a) of the figure, in steady state? You may assume that v_o is a sinusoid at the fundamental frequency.

Problem 1

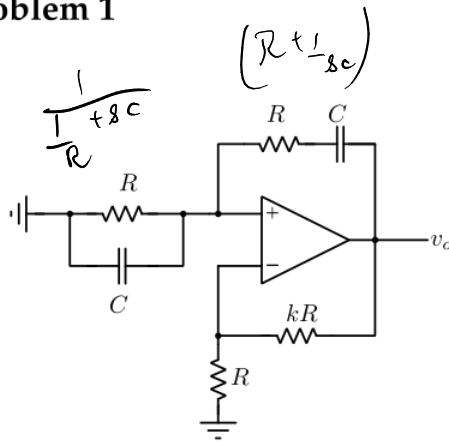


Figure 1: Circuit for Problem 1.

Fig. 1 shows a sinewave oscillator. Determine k so that it just begins to oscillate. All opamps are ideal.

$$\frac{v_o}{k} = V_0 \left[\frac{1}{\left(\frac{1}{R} + sC \right)} \right]$$

$$\frac{1}{k} = \frac{1}{R + \frac{1}{sC}}$$

$$\frac{1}{k} = \frac{1}{1 + \left(R + \frac{1}{sC} \right) \left(\frac{1}{R} + sC \right)}$$

$$\frac{1}{k} = \frac{1}{3 + \frac{1}{sC} + sCR}$$

Use $s = j\omega$

$$\frac{1}{k} = \frac{1}{3 - \frac{j}{\omega RC} + j\omega RC}$$


$$-\frac{j}{\omega RC} + j\omega RC = 0$$

$$\boxed{\omega = \frac{1}{RC}}$$

$$\frac{1}{k} = \frac{1}{3 - 1} = \frac{1}{2}$$

$$\boxed{k = 2}$$

②

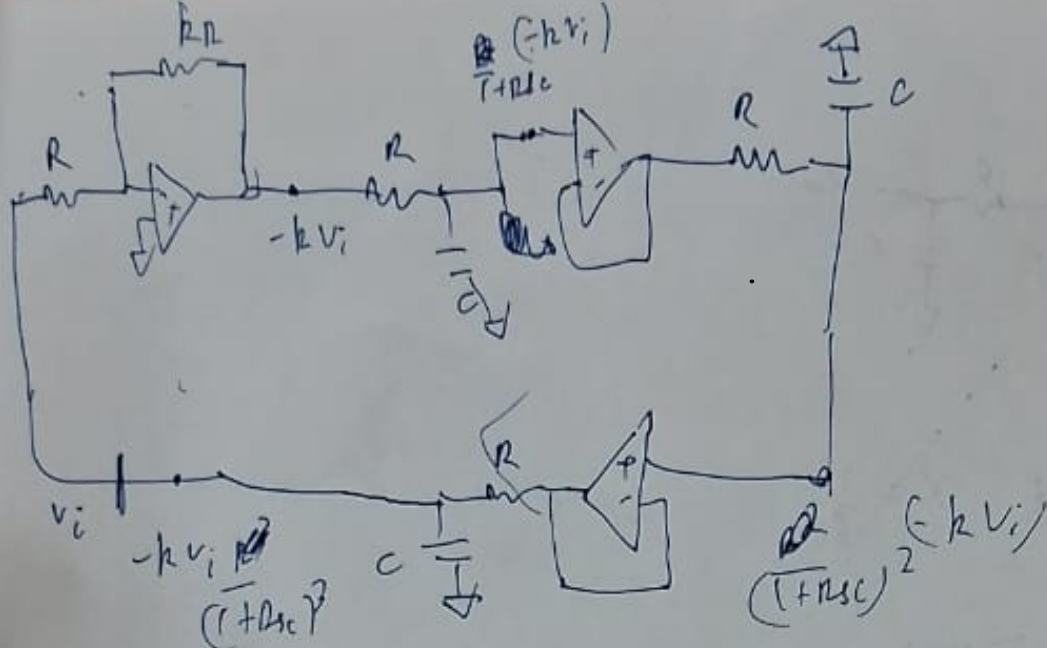

$$LH(s) = \frac{V_{bb}}{v_i} = \frac{-k}{(1 + R s C)^3}$$

$$= -k$$

$$1 + 3 s R C + 3 s^2 R^2 C^2 + s^3 R^3 C^3$$

$$s = j\omega$$

$$= -k$$

$$1 - 3 \omega^2 R^2 C^2 + j [3 \omega R C - \omega^3 R^3 C^3] \approx 0$$


$$3 \omega R C = \omega^3 R^3 C^3$$

$$\boxed{\omega = \sqrt{3/RC}}$$

$$\text{Also, } |LH(s)| = 1$$

$$\frac{-k}{1 - 3 \frac{R^2 C^2}{R^2 C^2}} \approx \frac{-k}{-9} = 1 \Rightarrow k = 9$$

③

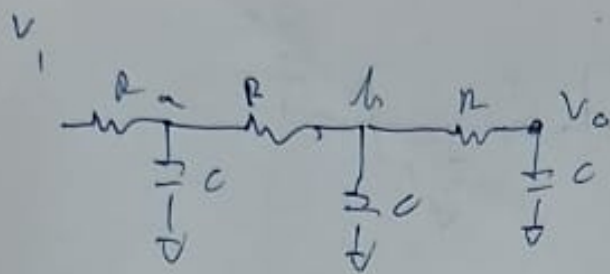

$$\frac{a - V_1}{R} + \frac{a - b}{R} + a s C = 0$$

$$a \frac{b - a}{R} + \frac{b - c}{R} + \frac{b s C}{s R C + 1} = 0$$

$$(b - a) + b s C R + \frac{b s C R}{s R C + 1} = 0$$

$$b = \frac{a}{1 + s C R + \frac{s C R}{s R C + 1}}$$

$$a \left[\frac{2}{R} + s C R \right] = V_1$$

$$b a \left[\frac{1 + s C R + \frac{s C R}{s R C + 1}}{s R C + 1} \right] \left[\frac{2 + s C R}{-b} \right] = V_1$$

$$b = \frac{V_1 (s R C + 1)}{((1 + s C R)^2 + s C R) (2 + s C R) - (s R C + 1)}$$

$$V_0 = \frac{V_1}{((1 + s R C)^2 + s R C) (2 + s R C) - (1 + s R C)}$$



Now, Consider

$$H(s) = \frac{-k}{((1+sRC)^2 + sRC)(2+sRC) - (1+sRC)} = \frac{V_o}{V_{in}}$$

$$\text{Let } sRC = j\omega_x$$

$$= \frac{-k}{(1 - \omega_x^2 + j\omega_x)(2 + j\omega_x) - (1 + j\omega_x)}$$

$$= \frac{-k}{(2 - \omega_x^2 + j\omega_x - j\omega_x^3 - 3\omega_x^2) - (1 + j\omega_x)}$$

$$= \frac{-k}{(1 - \omega_x^2 s + j\omega_x - j\omega_x^3)}$$

$$(1 - \omega_x^2 s + j\omega_x - j\omega_x^3)$$

$$6\omega_x = \omega_x^3 \quad \omega_x = \sqrt{6} = \omega_{ORC}$$

$$\boxed{\omega_{ORC} = \sqrt{6}} \quad \frac{-k}{1 - 5(6)} = 1, \quad \boxed{k=29} \quad \boxed{k=29}$$

(4)

$$\frac{V_0}{\omega L} + \frac{V_0}{\omega L} + \frac{V_0}{\omega L} - \frac{V_0}{\omega L} = 0$$

We want $G_1 = -G_2$, so that $\omega = \frac{1}{\sqrt{LC}}$

$$G_1 = -G_2$$

Now, considering I_{max} ,


if $A < \frac{I_{max}}{\omega}$, then $I = 0$ [As $\omega L = G_1 - G_2 = 0$]



If $A > \frac{I_{max}}{\omega}$

For $V < \frac{I_{max}}{\omega}$, $i = 0$

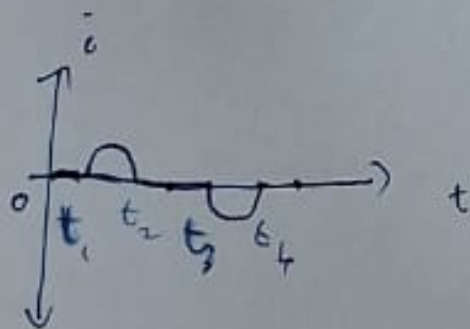$V > \frac{I_{max}}{\omega}$, $i = V\omega - i_{max}$



i starts increasing

at $t = \frac{1}{\omega} \sin^{-1}\left(\frac{i_{max}}{A}\right)$

$$t_1 = \frac{1}{\omega} \sin^{-1} \frac{i_{max}}{A}, \quad t_2 = \frac{T}{2} - t_1, \quad t_3 = \frac{T}{2} + t_1, \quad t_4 = T - t_1$$

Amplitude of first component

$$\epsilon_1 = \frac{1}{\omega} \sin^{-1} \frac{I_{max}}{\omega A}$$

$$= \frac{2 \int_{t_1}^{t_2} (\cancel{\omega A \sin \omega t} - I_{max}) e^{-j\omega t} dt + \int_{t_3}^{t_4} (\cancel{\omega A \sin \omega t} + I_{max}) e^{-j\omega t} dt}{T}$$

$$= \frac{(-I_{max}) (e^{-j\omega t_2} - e^{-j\omega t_1})}{2\omega}$$

$$= \frac{2 I_{max}}{2\omega} \left[2 e^{-j\omega t_1} \right] = \frac{2 I_{max}}{\omega} \cos \left(\sin^{-1} \left(\frac{I_{max}}{\omega A} \right) \right)$$

$$= \frac{2 I_{max}}{\omega} \sqrt{1 - \frac{I_{max}^2}{\omega^2 A^2}}$$

As $A \rightarrow \infty$, Amplitude $\rightarrow \frac{2 I_{max}}{\omega}$

