

EE2019–Analog Systems and Lab: Tutorial 5

Nagendra Krishnapura, Shanthi Pavan

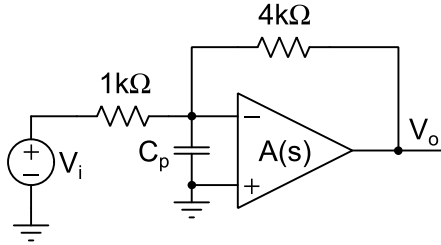


Figure 1: Circuit for problem 1

- Fig. 1 shows an inverting amplifier. The opamp has a gain $A(s) = A_0/(1 + s/p_1)(1 + s/p_2)$ where $A_0 = 20000$, $p_1 = 1 \text{ krad/s}$, $p_2 = 10 \text{ Mrad/s}$. C_p is a parasitic capacitor.

- What is the phase margin of the system with $C_p = 0$?
- What is the closed loop bandwidth of the system? (Calculate this from (a) Unity loop gain frequency, (b) Natural frequency of the second order system, and (c) Exact calculation-computing the frequency at which the gain magnitude drops to $1/\sqrt{2}$ times the dc gain.; Compare the estimates so obtained)
- What is the value of C_p for which the circuit becomes unstable?
- With C_p being the value calculated in the previous part, can you change the circuit so that the phase margin is 60° without changing the opamp or the closed-loop dc gain V_o/V_i ?

- Fig. 2 shows a transimpedance amplifier. The opamp has a frequency independent gain A_0 . The feedback resistor R has a parasitic capacitor C . C is distributed across the length of the resistor and should be modeled as shown in Fig. 2(b) where the infinite number of infinitesimal ΔR and ΔC sum up to R

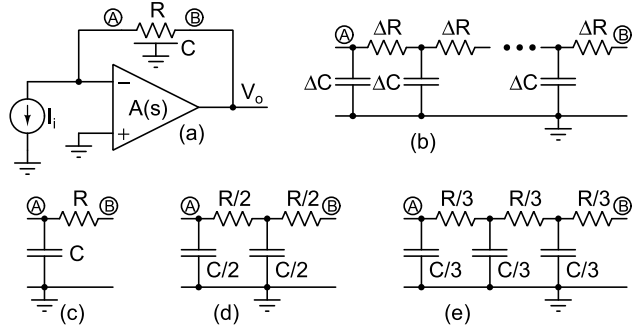


Figure 2: Circuit for problem 2

and C respectively. This cannot be analyzed easily, so we model it as shown in Fig. 2(c), (d), or (e). Analyze each case and comment on the effect of A_0 on stability or damping. (In addition to stability, this problem also tells you something about oversimplified models).

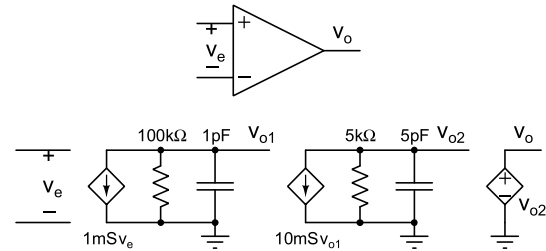


Figure 3: Circuit for problem 3

- Fig. 3 shows the internal schematic of an opamp. This opamp is used to realize a unity gain, non-inverting amplifier.

- What is the phase margin?
- Connect a capacitor across one of the existing capacitors inside the opamp so that the phase margin is 60° .

Repeat the above if the opamp is used to realize an inverting amplifier of gain -4 .

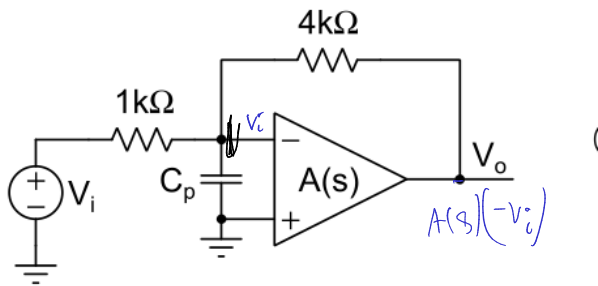


Figure 1: Circuit for problem 1

1. Fig. 1 shows an inverting amplifier. The opamp has a gain $A(s) = A_0 / (1 + s/p_1)(1 + s/p_2)$ where $A_0 = 20000$, $p_1 = 1 \text{ krad/s}$, $p_2 = 10 \text{ Mrad/s}$. C_p is a parasitic capacitor.

- What is the phase margin of the system with $C_p = 0$?

$$\frac{A_0}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$L_h(s) = -\frac{1}{5} A_0$$

$$\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)$$

$$= \left| \frac{-4000}{\left(1 + \frac{s}{10^3}\right) \left(1 + \frac{s}{10^7}\right)} \right| = 1$$

$$4000^2 = \left(1 + \frac{\omega^2}{10^6}\right) \left(1 + \frac{\omega^2}{10^{14}}\right)$$

$$\omega = 4 \times 10^6 \text{ rad/s}$$

$$\left| \frac{-4000}{\left(1 + j 4 \times 10^3\right) \left(1 + j 0.4\right)} \right|$$

$$= 68^\circ$$

- What is the closed loop bandwidth of the system? (Calculate this from (a) Unity loop gain frequency, (b) Natural frequency of the second order system, and (c) Exact calculation - computing the frequency at which the gain magnitude drops to $1/\sqrt{2}$ times the dc gain.; Compare the estimates so obtained)

a) $\omega_{ug} = 4 \times 10^6 \text{ rad/s}$

b) 2nd order system

$-4A(s)$


$(A(s) + 5) = s^2 + 2\gamma s\omega_n + \omega_n^2$

$\left(1 + \frac{1}{p_1}\right) \left(1 + \frac{1}{p_2}\right) 5 + A_0 = 0$

$s = -5 \times 10^6 \pm 3.873 \times 10^6$

$\text{abs}(s) = 6.35 \times 10^6 \text{ rad/s}$

c) Exact

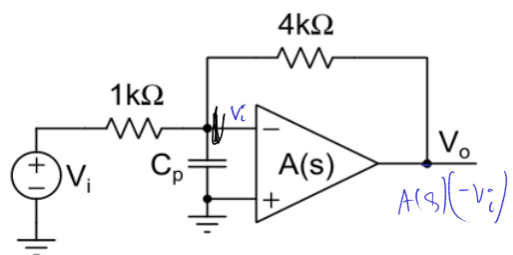

$V_o = A(s)(-V_i)$

$\frac{V_i - V_o}{4k} = \frac{V_i - V_o}{4k}$

$4V_i - 4V_o = V_o - V_o$

$4V_i + V_o = 5V_i = -\frac{V_o 5}{A(s)}$

$$V_i = \frac{-V_o - V_o s}{A(s)}$$

$$\frac{V_i}{V_o} = \frac{-1 - \frac{s}{A(s)}}{4}$$

$$\frac{V_o}{V(s)} = \frac{4}{-1 - \frac{s}{A(s)}}$$

$$= \frac{-4 A(s)}{A(s) + s}$$

$$\left| \frac{V_i(s)}{V_o} \right| = \frac{1}{\sqrt{2}}$$

$$\left| \frac{-4 A_o}{\left(1 + \frac{j\omega}{p_1}\right) \left(1 + \frac{j\omega}{p_2}\right)} \cdot \frac{A_o}{\left(1 + \frac{j\omega}{p_1}\right) \left(1 + \frac{j\omega}{p_2}\right)} + s \right|$$

$$= \frac{4}{\sqrt{2}}$$

$$\left| \frac{4 A_o}{A_o + s \left(1 + \frac{j\omega}{p_1}\right) \left(1 + \frac{j\omega}{p_2}\right)} \right| = \frac{4}{\sqrt{2}}$$

$$\text{abs}\left(4 \cdot \frac{20000}{\left(20000 + 5\left(1 + \frac{iw}{1e3}\right)\left(1 + \frac{iw}{1e7}\right)\right)}\right) = \frac{4}{\text{sqrt}(2)}$$

✕ =

NATURAL LANGUAGE \int_0^x MATH INPUT

★ √ ∂f (::) √ √ aω ...

POPULAR

×

$\frac{\square}{\square}$
 \square^\square
 $\sqrt{\square}$
 $\sqrt[3]{\square}$
 $\sqrt[n]{\square}$
 $\frac{d}{d\square}$
 $\frac{d^2}{d^2\square}$
 $\int \square$
 $\int \square^\square$
 \sum_{\square}^{\square}
 $\lim_{\square \rightarrow \square} \square$
 $[\square, \square, \square]$
 $\begin{pmatrix} \square & \square \\ \square & \square \end{pmatrix}$

Assuming i is the imaginary unit | Use i as a [variable](#) instead

Input interpretation

$$\left| 4 \times \frac{20000}{20000 + 5\left(1 + \frac{iw}{1 \times 10^3}\right)\left(1 + \frac{iw}{1 \times 10^7}\right)} \right| = \frac{4}{\sqrt{2}}$$

|z| is the absolute value of z

i is the imaginary unit

Result

$$\frac{80000}{\left| 5\left(\frac{iw}{10000000} + 1\right)\left(\frac{iw}{1000} + 1\right) + 20000 \right|} = 2\sqrt{2}$$

Real solutions

More digits

Exact forms


☒ Step-by-step solution

$$w \approx -5587607$$

$$w \approx 5587607$$

$$\left(w = 5.587 \times 10^6 \text{ rad/s} \right)$$

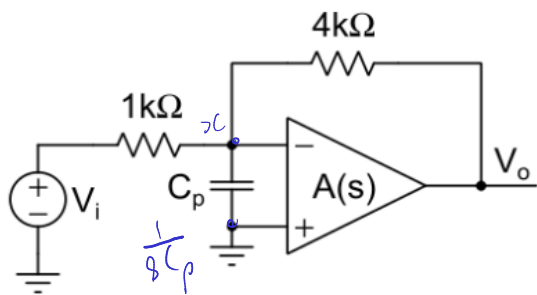- What is the value of C_p for which the circuit becomes unstable?



$$\frac{V_i - x}{1k} + \frac{V_o - x}{4k} + \frac{0 - x}{1/sC_p} = 0$$

$$V_o = -A(s)x$$

$$-V_o \left(\frac{1}{1k} + \frac{1}{4k} + sC_p \right) = \frac{V_i}{1k} + \frac{V_o}{-4k}$$

$$-V_o \left(\frac{1}{A(s)} \left(\frac{1}{1k} + \frac{1}{4k} + sC_p \right) + \frac{1}{4k} \right) = \frac{V_i}{1k}$$

$$V_o = - \frac{1}{1k} \left(\frac{1}{A(s)} \left(\frac{1}{1k} + \frac{1}{4k} + sC_p \right) + \frac{1}{4k} \right)$$

$$= - \frac{1}{1k} \left[\underbrace{\left(1 + \frac{s}{p_1} \right) \left(1 + \frac{s}{p_2} \right)}_{A_o} \left(\frac{1}{800} + sC_p \right) + \frac{1}{4k} \right]$$

$$= -1$$

$$1k \left[\frac{\left(1 + \frac{s}{p_1} \right) \left(1 + \frac{s}{p_2} \right) (1 + 800sC_p)}{800(20000)} + \frac{10000}{(4000)4000} \right]$$

$$= \frac{16000}{\left(\left(1 + \frac{s}{p_1} \right) \left(1 + \frac{s}{p_2} \right) (1 + 800sC_p) + 4000 \right)}$$

$$LH(s) = k \times 10^3$$

$$\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_c}\right)$$

$$p_c = \frac{1}{800} \text{ s}^{-1}$$

Now, set $\phi M = 0^\circ$

Assume $p_1 \ll p_c \ll p_2$

$$0 = 180 - \tan^{-1}\left(\frac{\omega_u}{p_1}\right) - \tan^{-1}\frac{\omega_u}{p_c} - \tan^{-1}\left(\frac{\omega_u}{p_2}\right)$$

Take $\omega_u = 10 p_c$ (by Bode approximation)

set $|LH(s)| = 1$

$$k \times 10^3 = \left| \left(1 + \frac{s}{p_1}\right) \underbrace{\left(1 + \frac{s}{p_2}\right)}_{\approx 1} \left(1 + \frac{s}{p_c}\right) \right|$$

$$k \times 10^3 = \sqrt{1 + \frac{100 p_c^2}{10^6}} \sqrt{1 + 100}$$

$$\frac{k \times 10^3}{\sqrt{101}} = \sqrt{1 + \frac{100 p_c^2}{10^6}}$$

$$\frac{16 \times 10^6}{101} = \frac{100 p_c^2}{10^6}$$

$$p_c = \frac{16 \times 10^{10}}{101}$$

$$= 16 \times 10^8$$

$$p_c = \sqrt[4]{16 \times 10^8} = \frac{1}{800} \text{ s}^{-1}$$

$$C = \frac{1}{800 \times 4 \times 10^4}$$

$$= 31.25 \text{ nF}$$

$$\phi M = 0^\circ$$

becomes unstable:

- With C_p being the value calculated in the previous part, can you change the circuit so that the phase margin is 60° without changing the opamp or the closed-loop dc gain V_o/V_i ?

Decrease R_1 & R_2

Poles are


$$\frac{1}{R_1 C_1}$$

$$\frac{1}{R_2 C_2}$$

Poles move to left

Wash, so

PM \downarrow

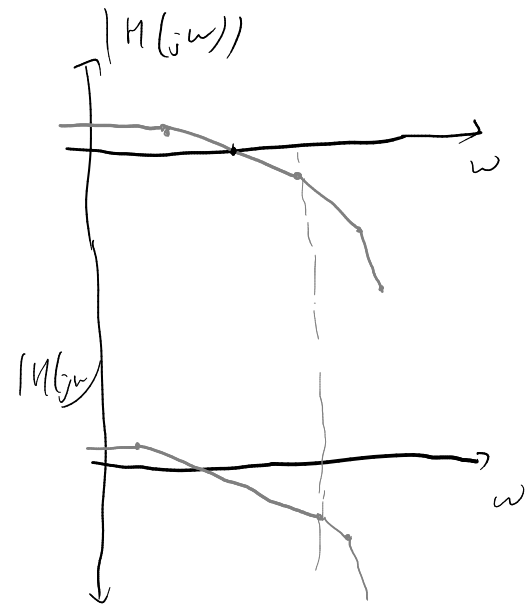

2. Fig. 2 shows a transimpedance amplifier. The opamp has a frequency independent gain A_0 . The feedback resistor R has a parasitic capacitor C . C is distributed across the length of the resistor and should be modeled as shown in Fig. 2(b) where the infinite number of infinitesimal ΔR and ΔC sum up to R


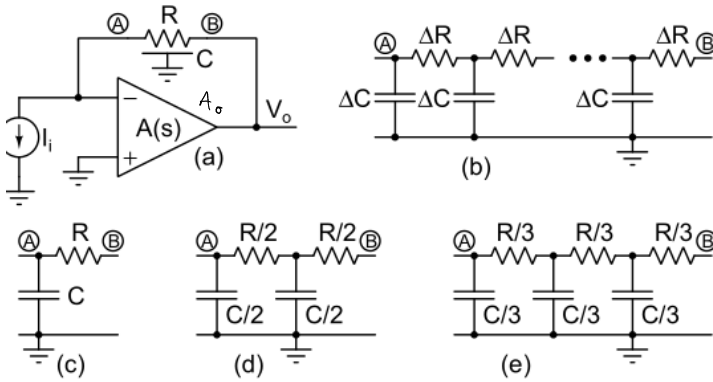


Figure 2: Circuit for problem 2

and C respectively. This cannot be analyzed easily, so we model it as shown in Fig. 2(c), (d), or (e). Analyze each case and comment on the effect of A_0 on stability or damping. (In addition to stability, this problem also tells you something about oversimplified models).

*

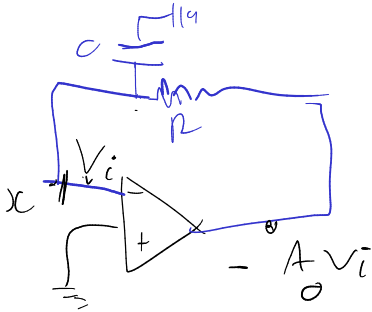

$$\frac{-A_0 V_i - V_o}{R} + \frac{0 - V_o}{\left(\frac{L}{sC}\right)} = 0$$


$$\frac{-A_0 V_i}{R} = V_o \left(\frac{1}{R} + sC \right)$$

$$LL(s) = +A_0 \frac{1}{R \left(\frac{1}{R} + sC \right)}$$

$$- \left(\frac{+A_0}{(1 + R s C)} \right)$$

$$s = -\frac{1}{RC}$$

4

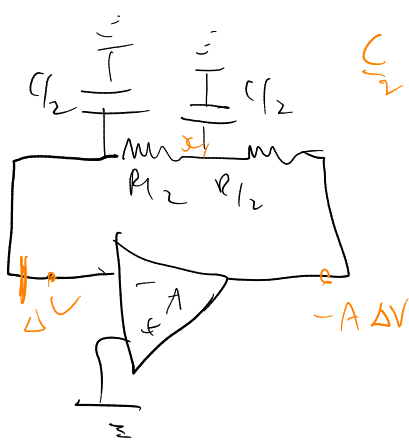

$$C_2 = C', R_2 = R'$$

$$\frac{-A\Delta V - x}{R/2} + \frac{0 - x}{\frac{2}{s}C} + \frac{0 - x}{\frac{R}{2} + \frac{1}{s}C}$$

$$\frac{-A\Delta V}{R/2} = x \left[\frac{2}{R} + \frac{sC}{2} + \frac{1}{\frac{R}{2} + \frac{1}{s}C} \right]$$

$$x = \frac{-A\Delta V}{R/2 \left[\frac{2}{R} + \frac{sC}{2} + \frac{1}{\frac{R}{2} + \frac{1}{s}C} \right]}$$

$$\frac{V_{out}}{\Delta V} = \frac{-A}{R/2} \left[\frac{2}{R} + \frac{sC}{2} + \frac{1}{\frac{R}{2} + \frac{1}{s}C} \right] \frac{\frac{1}{sC}}{\frac{1}{sC} + \frac{R}{2}}$$

$$LH(s) = \left(\frac{A}{1 + \frac{sRC}{4} + \frac{R^2sC}{R^2sC + 4}} \right) \left(\frac{4}{4 + R^2sC} \right)$$

$$\approx 4A$$

$$\left(1 + \frac{sRC}{4} + \frac{R^2sC}{R^2sC + 4} \right) (4 + R^2sC)$$

$$\approx 4A$$

$$4 + R^2sC + \frac{s^2R^2C^2}{4} + R^2sC$$

$$\approx 16A$$

$$(16 + 12R^2sC + s^2R^2C^2)$$

144
62


$$2RC = \frac{-12 \pm \sqrt{144 - 4(16)}}{2}$$

$$= \frac{-12 \pm \sqrt{80}}{2}$$

$$= -6 \pm 2\sqrt{5}$$

$$8 \left(\frac{-6 \pm 2\sqrt{5}}{RC} \right)$$
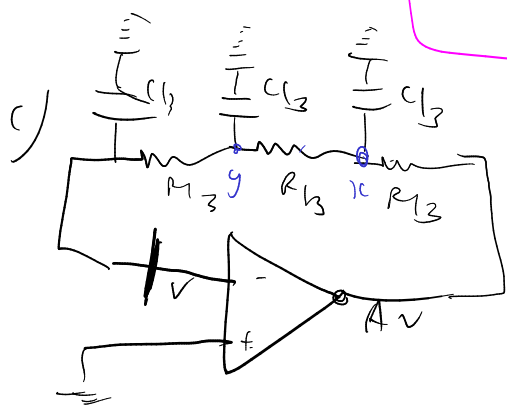
$$\approx \frac{-1.527}{RC}, \quad \frac{-10.4}{RC}$$



$$A_v \frac{x-y}{R_1} + \frac{y-x}{R_2} + \frac{0-x}{\frac{1}{s}C_3} = 0$$

$$\frac{0-y}{\frac{1}{s}C_1} + \frac{x-y}{R_1} + \frac{0-y}{\frac{R_2}{s} + \frac{1}{s}C_2} = 0$$

$$x = \frac{R_2}{3} y \left[\frac{sC_1}{3} + \frac{3}{R_2} + \frac{1}{\frac{R_2}{3} + \frac{1}{s}C_2} \right]$$

$$\frac{y}{R_1} = -\frac{A_v}{3} + y \left[\frac{3}{R_2} + \frac{3}{R_2} + \frac{sC_1}{3} \right] \frac{R_2}{3} \left[\frac{sC_1}{3} + \frac{3}{R_2} + \frac{1}{\frac{R_2}{3} + \frac{1}{s}C_2} \right]$$

$$-\frac{A_v}{3} = y \left[\frac{3}{R_2} - \frac{R_2}{3} \left(\frac{6}{R_2} + \frac{sC_1}{3} \right) \left(\frac{sC_1}{3} + \frac{3}{R_2} + \frac{1}{\frac{R_2}{3} + \frac{1}{s}C_2} \right) \right]$$

$$V_O = -A_v \frac{3}{R_2}$$

$$\frac{3}{R_2} - \frac{R_2}{3} \left(\frac{6}{R_2} + \frac{sC_1}{3} \right) \left(\frac{sC_1}{3} + \frac{3}{R_2} + \frac{1}{\frac{R_2}{3} + \frac{1}{s}C_2} \right) \left(\frac{3}{R_2} + \frac{1}{s}C_2 \right)$$

$$= \frac{-A}{\left(\frac{3}{R} - \frac{R}{3} \left(\frac{6}{R} + \frac{8C}{3} \right) \left(\frac{8C}{3} + \frac{3}{R} + \frac{38C}{R \cdot 8C + 9} \right) \right) (9 + R \cdot 8C)}$$

$$= \frac{-A}{\left(\frac{3(9+8CR)}{R} - \frac{R}{3} \left(\frac{6}{R} + \frac{8C}{3} \right) \left(\frac{38C + R \cdot \frac{8C^2}{3} + \frac{27}{R} + 38C + 38C}{3} \right) \right)}$$

$$= \frac{-A}{\left(\frac{3(9+8CR)}{R} - \frac{1}{3} \left(\frac{18 + R \cdot 8C}{3} \right) \left(\frac{R \cdot \frac{8C^2}{3} + \frac{27}{R} + 98C \right) \right)}$$

$$= \frac{A}{\left(\frac{81(9+8CR)}{27R} - \left(\frac{18 + R \cdot 8C}{27R} \right) \left(\frac{R^2 \cdot 8C^2 + 81 + 27 \cdot 8CR}{27R} \right) \right)}$$

$$= \frac{A(27R)}{729 + 818CR - (18 + R \cdot 8C)(R^2 \cdot 8C^2 + 81 + 27 \cdot 8CR)}$$

$$= \frac{27AR}{27}$$

$$729 + 818CR - (R^3 \cdot 8C^3 + 81R \cdot 8C + 27 \cdot 8C^2 R^2 + 18 \cdot 8C^2 R^2 + (18)81 + (18)27 \cdot 8CR)$$

$$= -27AR$$

$$729 + 4868CR + 4512C^2R^2 + R^3 \cdot 8C^3$$

$$s = \frac{-29 \cdot 2}{RC} \quad \frac{-13 \cdot 9}{RC} \quad \frac{-1 \cdot 78}{RC}$$

We can see that, as more R & C are added, poles become larger & larger.

DC gain increases by large value, but AC gain is lesser, so

P.M. \downarrow

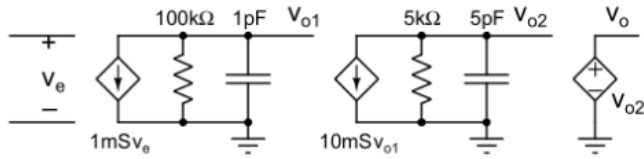
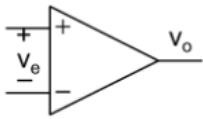


Figure 3: Circuit for problem 3

3. Fig. 3 shows the internal schematic of an opamp. This opamp is used to realize a unity gain, non-inverting amplifier.

- What is the phase margin?
- Connect a capacitor across one of the existing capacitors inside the opamp so that the phase margin is 60° .

$$V_o = V_{o2} = (10 \text{ mS } V_{o1}) \left(\frac{8C_2 + 1}{R_2} \right)$$

$$A(s) = 10 \text{ mS } (s)$$

$$\left(8C_1 + \frac{1}{R_1} \right) \left(8C_2 + \frac{1}{R_2} \right)$$

$$= \frac{10^{-7} \times R_1 R_2}{(R_1 C_1 s + 1) (R_2 C_2 s + 1)}$$

$$= 5000$$

$$\left(\frac{8}{10^{-7}} + 1 \right) \left(1 + \frac{8}{4 \times 10^{-7}} \right)$$

$$5000 = \sqrt{\frac{\omega^2}{10^{14}} + 1} \sqrt{\frac{\omega^2}{16 \times 10^{14}} + 1}$$

$$25 \times 10^6 = \left(\frac{\omega}{10^{14}} + 1 \right) \left(\frac{\omega}{16 \times 10^{14}} + 1 \right)$$

$$\omega_{ug} = 1.4 \times 10^9$$

$$|A(s)| = \left(\frac{50}{\left(1 + \frac{s}{10^7}\right) \left(1 + \frac{s}{1.4 \times 10^7}\right)} \right)$$

$$= 180^\circ = \left(\tan^{-1} \left(\frac{\omega_{ug}}{p_1} \right) + \tan^{-1} \left(\frac{\omega_{ug}}{p_2} \right) \right)$$

$$= 2^\circ$$

- Connect a capacitor across one of the existing capacitors inside the opamp so that the phase margin is 60° .

Let us connect across first capacitor

let C be new capacitance

$$| = \left(\frac{50}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)} \right)$$

$$[p_1 \cdot L \cdot L \cdot p_2]$$

$$W_{avg} = 50 \times P_1$$

$$= 5000 \times \frac{1}{(10^5)} C$$

$$= \boxed{\frac{1}{200 C}}$$

$$60 = 180 - \tan^{-1} \left(\frac{1}{200 C} \right)$$

$$= \tan^{-1} \left(\frac{1}{200 C} \right)$$

$$L \times 10^5 \times 200 C = \sqrt{3}$$

$$C = \frac{\sqrt{3} \cdot 10^{-7}}{80} = \boxed{1.25 \times 10^{-9} \sqrt{3} \text{ nF}}$$

$$C_{eq} = C_1 + C_2, \quad C_1 = \boxed{1.25 \times 10^{-9} \sqrt{3} \text{ nF}}$$

2nd Q


$$P_1 \gg P_2$$

$$I = 50 \mu A$$

$$\left(1 + \frac{I}{P_1}\right) \left(1 + \frac{I}{P_2}\right)$$

$$\omega_{ag} = \frac{5 \times 10^3}{5 \times 10^3} \times$$

(C)

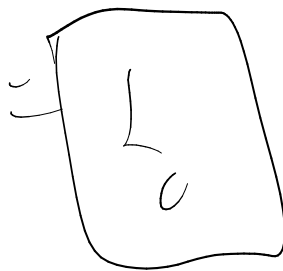

$$\phi = 180 - \tan^{-1}\left(\frac{\omega_{ag}}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right) \approx 90^\circ$$

$$\frac{\omega_{ag}}{P_1} = \frac{1}{\sqrt{3}}$$


$$\frac{1}{C} = \frac{1}{\sqrt{3} \times 10^{-7}}$$

$$C = 3 \times 10^{-7}$$

$$= 173.2 \text{ nF}$$

$$C' \approx 17.32 \text{ nF}$$

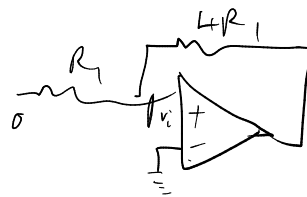- c) Repeat the above if the opamp is used to realize an inverting amplifier of gain -4 .



$$L_h = -\beta A(s) = \boxed{-\frac{1}{5} A(s)}$$

$$|L_h(s)| = \frac{1000}{\left(1 + \frac{s}{10^7}\right) \left(1 + \frac{s}{10^7}\right)}$$

$$\omega_{hg} = \boxed{6.31 \times 10^8 \text{ rad/s}}$$

$$PM = 180 - \tan^{-1} \left(\frac{\omega_{hg}}{P_1} \right) - \tan^{-1} \left(\frac{\omega_{hg}}{P_2} \right)$$

$$\boxed{4.44^\circ}$$

* Connect across 1st capacitor

Let C be effective capacitance

Assume

$$\boxed{P_1 \ll P_2}$$

$$\boxed{P_1 = \frac{1}{RC}}$$

$$1 = \frac{1000}{\left(1 + \frac{s}{P_1}\right) \left(1 + \frac{s}{P_2}\right)} \approx \frac{1000}{\left(1 + \frac{s}{P_1}\right)}$$

$$\omega_{hg} = 1000 \quad P_1 = \frac{1000}{10^5 C} = \boxed{\frac{1}{100 C}}$$

$$PM = 60^\circ = 180 - \tan^{-1} \left(\frac{W_{us}}{P_1} \right) - \tan^{-1} \left(\frac{W_{us}}{P_2} \right)$$

90°

$$W_{us} = \frac{1}{\sqrt{3}} P_2$$

$$\frac{1}{100 \text{ C}} = \frac{1}{\sqrt{3}} \cdot 4 \times 10^7$$

$$C = \frac{\sqrt{3}}{4 \times 10^9}$$

$$= \frac{\sqrt{3}}{4} \mu\text{F}$$

$$C_{\text{actual}} \approx \frac{\sqrt{3}}{4} \mu\text{F}$$

$$= 143.2 \mu\text{F}$$