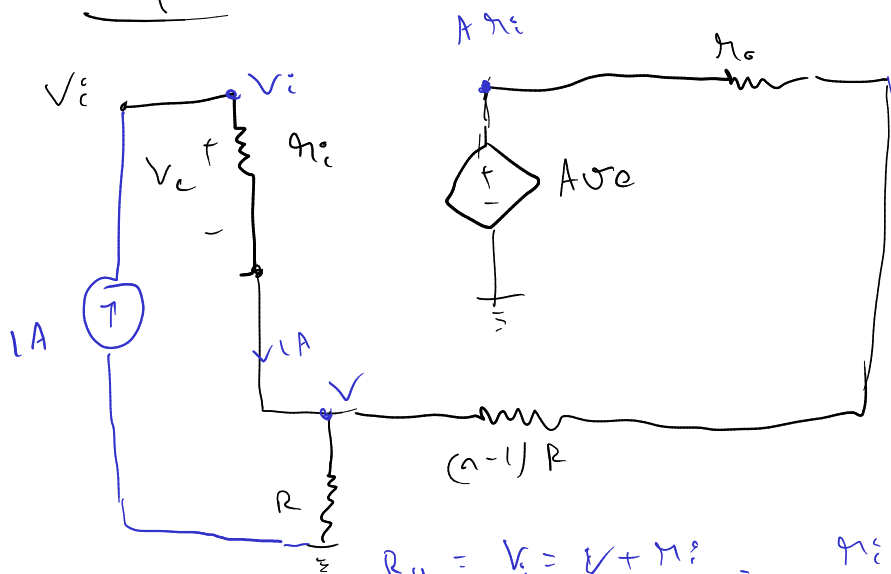


12

Input Resistance



Assume 1A input source


$$1A = \frac{V}{R} = \frac{V - A r_i}{r_o + (n-1)R}$$

$$1 + \frac{A r_i}{r_o + (n-1)R} = V \left[\frac{1}{R} + \frac{1}{r_o + (n-1)R} \right]$$

$$R_{in} = \frac{V_i}{1A} = \frac{V + I R}{1A} = r_i + \frac{A r_i + 1}{\frac{1}{R} + \frac{1}{r_o + (n-1)R}}$$

$$= r_i + R \left[\frac{r_o + (n-1)R + A r_i}{R + r_o + (n-1)R} \right] = \underline{\underline{r_i + R \left[\frac{A r_i + r_o + (n-1)R}{r_o + nR} \right]}}$$

Output Resistance

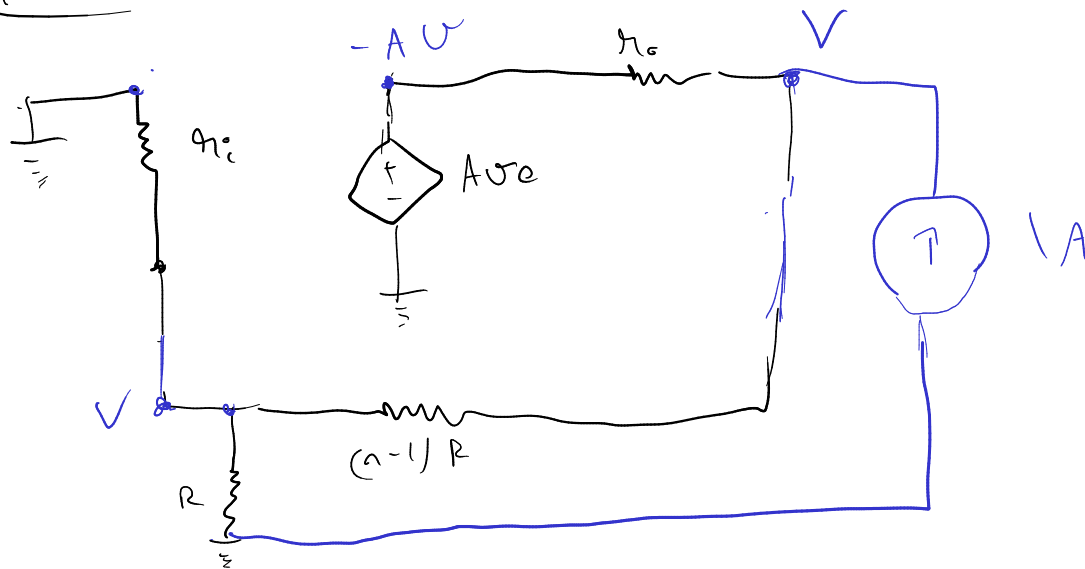

Assume 1A input,

$$1 = \frac{V}{(n-1)R + \frac{R r_i}{R + r_i}} + \frac{V + A V}{r_o} \left[\frac{\frac{r_i R}{R + r_i} + R}{\frac{r_i R}{R + r_i} + (n-1)R} \right]$$

$$V = \frac{1}{(n-1)R + \frac{Rr_i}{R+r_i} + 1 + A \frac{r_i R}{r_i + R} + \frac{\frac{r_i R}{r_i + R} + (n-1)R}{r_0}}$$


$$= \frac{1}{(n-1)R + \frac{Rr_i}{R+r_i} + 1 + \frac{A r_i R}{r_i R + (n-1)R(r_i + R)}}$$

$$= \frac{1}{\frac{R+r_i}{(R+r_i)(n-1)R + Rr_i} + \frac{1}{r_0} + \frac{r_i R + (n-1)R(r_i + R) + A r_i R}{r_i R + (n-1)R(r_i + R)}}$$

$$= \frac{[(R+r_i)(n-1)R + Rr_i] r_0}{Rr_0 + r_i r_0 + r_i R + (n-1)R(r_i + R) + A r_i R}$$

$$= \frac{((R+r_i)(n-1)R + Rr_i) r_0}{r_i r_0 + Rr_0 + (n-1)R(r_i + R) + (A+1)r_i R}$$

Gain

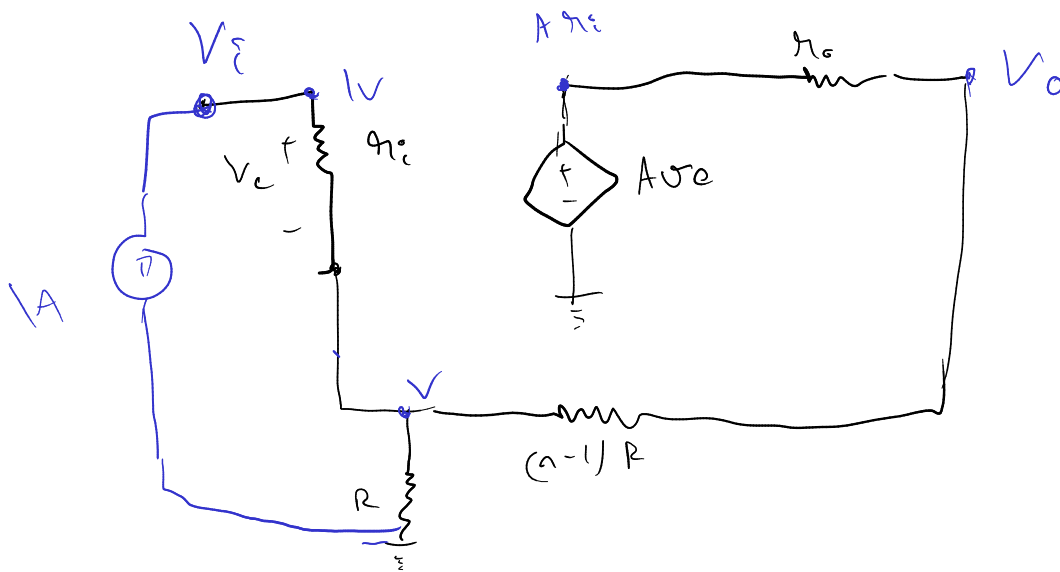

Consider 1A input. we have to find V_o & V_i

$$1A = \frac{V}{R} = \frac{V - A v_i}{r_o + (n-1)R}$$

$$\left(1 + \frac{A r_i}{r_o + (n-1)R}\right) = V \left[\frac{1}{R} + \frac{1}{r_o + (n-1)R} \right] \Rightarrow V = \frac{R \left[\frac{A r_i + r_o + (n-1)R}{r_o + nR} \right]}$$

$$V_f = V + n v_i = \frac{r_i + \frac{A r_i + 1}{r_o + (n-1)R}}{\frac{1}{R} + \frac{1}{r_o + (n-1)R}}$$

$$= r_i + R \left[\frac{r_o + (n-1)R + A r_i}{R + r_o + (n-1)R} \right] = r_i + R \left[\frac{A r_i + r_o + (n-1)R}{r_o + nR} \right] = V_i$$

$$V_o = V - \left(1 - \frac{V}{R}\right) (n-1)R$$

$$= V - (R - V)(n-1) = V - nR + R + nV - V$$

$$= nV - (n-1)R$$

$$V_o = n R \left[\frac{A n_i + g_o + (p-1) R}{n_o + n R} \right] - (n-1) R$$

$$= \frac{A n R n_i + n R n_o + \cancel{n R^2 (p-1)} - (n-1) R g_o + \cancel{n (n-1) R^2}}{n_o + n R}$$

$$\approx \frac{A n R n_i + R n_o}{n_o + n R}$$

$$\frac{V_i}{V_o} = \frac{n_o + R \left[\frac{A n_i + g_o + (p-1) R}{n_o + n R} \right]}{A n R n_i + R n_o} = \frac{g_i g_o + n R g_i + R A n_i + g_o R + (p-1) R^2}{A n R n_i + R n_o}$$

$$= \frac{n_i g_o + A R n_i + n R g_i + g_o R + (p-1) R^2}{A n R n_i + R n_o}$$

$$\frac{V_o}{V_i} = \text{gain} =$$

$$\boxed{\frac{A n R n_i + R n_o}{n_i g_o + A R n_i + n R g_i + g_o R + (p-1) R^2}}$$

Input Resistance

$$r_i + R \left[\frac{A r_i + r_o + (1-\beta)R}{r_o + \beta R} \right]$$

$$r_i + \frac{[A r_i + (1-\beta)R]}{\beta}$$

$$\infty$$

$$\infty$$

Output Resistance

$$\frac{(R + r_i)(1-\beta)R + R r_i}{r_o}$$

$$r_i r_o + R r_o + (1-\beta)R(r_i + R) + (1+\beta)r_i R$$

Gain

$$\frac{A \beta r_i + R r_o}{r_i r_o + A \beta r_i + \beta R r_i + r_o R + (1-\beta)R^2}$$

$$\frac{\beta A r_i}{r_i A + \beta r_i + (1-\beta)R}$$

$$r_o [1-\beta]$$



$$\frac{r_o + (1-\beta)R + (1+\beta)R}{r_o + \beta R + A R}$$

$$0$$


$$\frac{A \beta R}{r_o + A R + \beta R}$$

$$\beta$$


2.

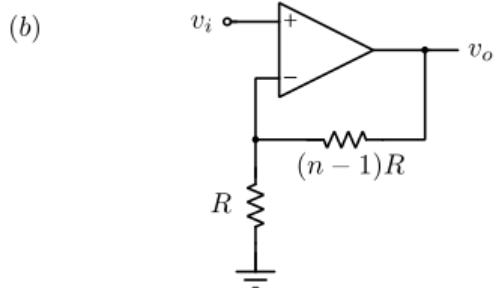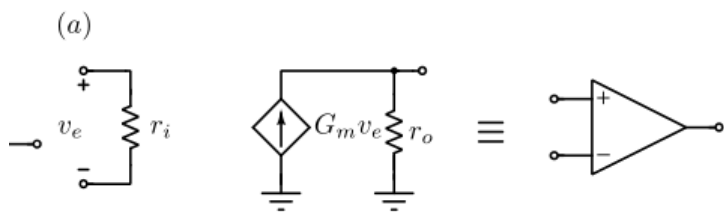


Note that

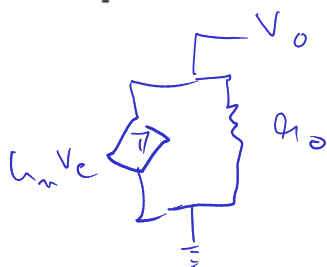

Source Transform

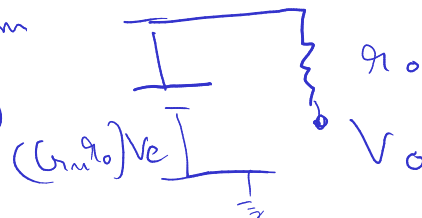

Input Resistance

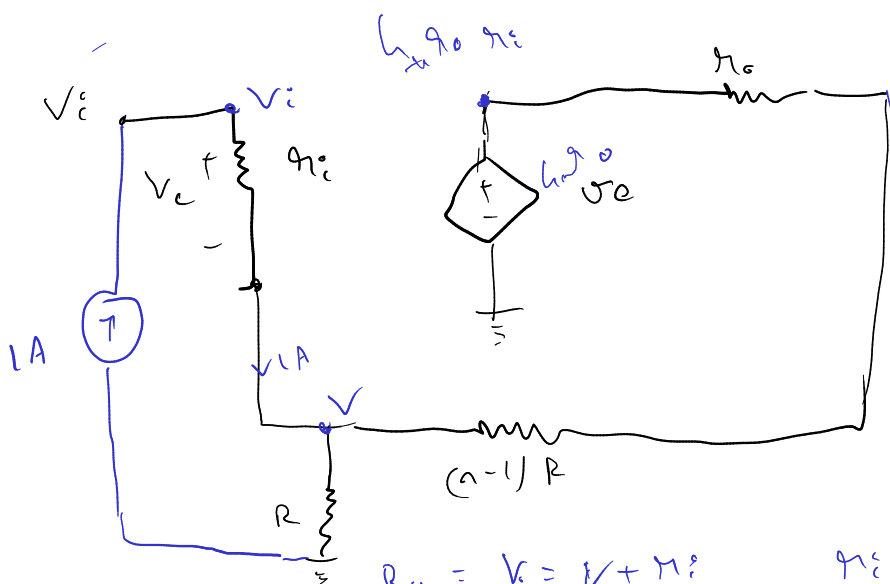

Assume 1A input source

$$I = \frac{V}{R} = \frac{V - \frac{g_i g_o v_o}{g_o + (n-1)R}}{R}$$


$$\left(1 + \frac{g_i g_o v_o}{g_o + (n-1)R}\right) = V \left[\frac{1}{R} + \frac{1}{g_o + (n-1)R} \right]$$

$$R_{in} = \frac{V_i}{1A} = \frac{V + I R}{1A} = \frac{g_i + \frac{g_m g_o g_i + 1}{g_o + (n-1)R}}{\frac{1}{R} + \frac{1}{g_o + (n-1)R}}$$

$$= g_i + R \left[\frac{g_o + (n-1)R + g_i g_o}{R + g_o + (n-1)R} \right] =$$

$$g_i + R \left[\frac{g_o g_i + g_o + (n-1)R}{g_o + nR} \right]$$

Output Resistance

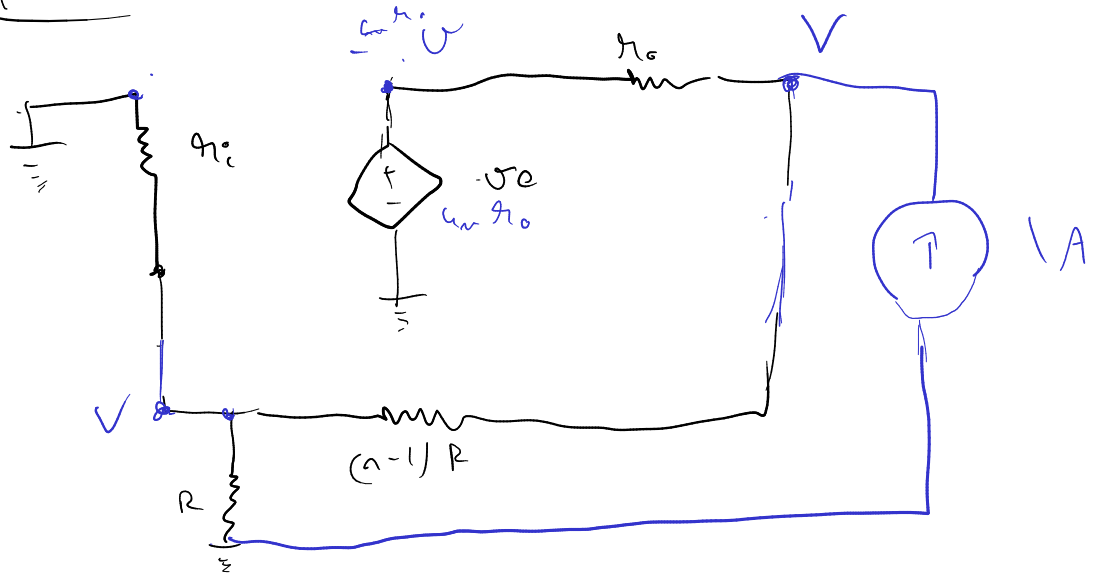

Assume 1A input,

$$I = \frac{V}{(n-1)R + \frac{R r_i}{R + r_i}} + \frac{V + h_m h_o V \left[\frac{\frac{r_i R}{r_i + R}}{\frac{r_i R}{r_i + R} + (n-1)R} \right]}{r_o}$$

$V =$

$$\frac{1}{\frac{(n-1)R + \frac{R r_i}{R + r_i}}{1 + h_m h_o \frac{r_i R}{r_i + R}} + \frac{\frac{r_i R}{r_i + R} + (n-1)R}{r_o}}$$

$=$

$$\frac{1}{\frac{(n-1)R + \frac{R r_i}{R + r_i}}{1 + \frac{h_m h_o r_i R}{r_i R + (n-1)R (r_i + R)}} + \frac{r_o}{r_i R + (n-1)R (r_i + R)}}$$


$=$

$$\frac{1}{\frac{(R + r_i)(n-1)R + R r_i}{(R + r_i)(n-1)R + R r_i} + \frac{r_o}{r_i R + (n-1)R (r_i + R)}}$$

$$= \frac{(R+r_i)(n-1)R + Rr_i}{Rr_0 + r_i r_0 + r_i R + (n-1)R(r_i + R) + \dots + r_i R} n_0$$

$$= \frac{(R+r_i)(n-1)R + Rr_i}{r_i r_0 + Rr_0 + (n-1)R(r_i + R) + (r_0 + 1)r_i R} n_0$$

Gain

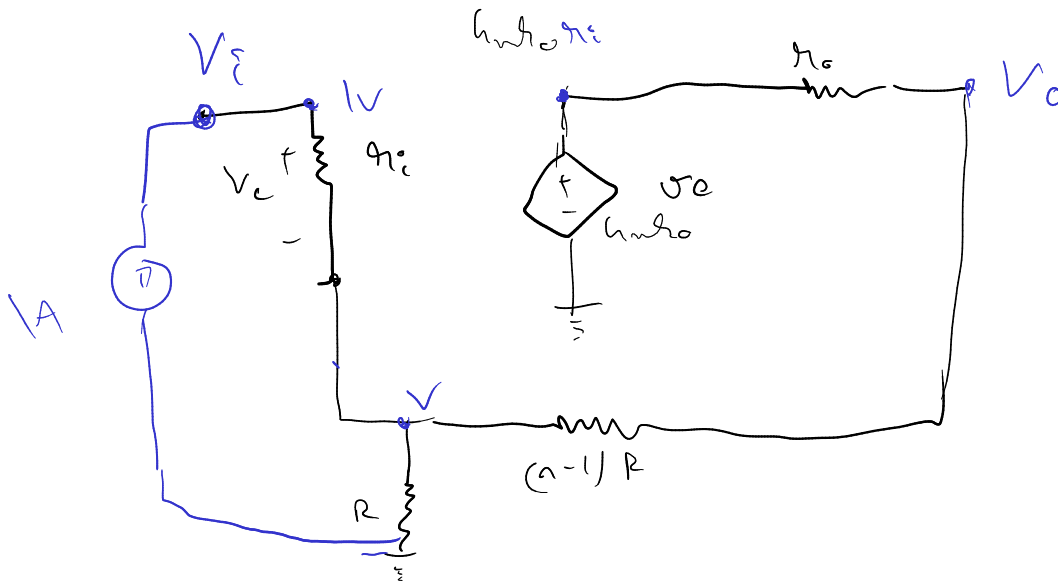

Consider 1A input. We have to find V_o & V_i

$$1A = \frac{V}{R} + \frac{V - \frac{g_i h_o}{g_o + (n-1)R}}{g_o + (n-1)R}$$

$$\left(1 + \frac{g_i h_o}{g_o + (n-1)R}\right) = V \left[\frac{1}{R} + \frac{1}{g_o + (n-1)R} \right] \Rightarrow V = \frac{R \left[\frac{g_i + h_o + (n-1)R}{h_o} \right]}{g_o + nR}$$

$$V_i = V + nV = \frac{g_i + \frac{h_o h_o g_i + 1}{g_o + (n-1)R}}{\frac{1}{R} + \frac{1}{g_o + (n-1)R}}$$

$$= g_i + R \left[\frac{g_o + (n-1)R + h_o g_i}{R + g_o + (n-1)R} \right] = \boxed{g_i + R \left[\frac{g_o + h_o + (n-1)R}{g_o + nR} \right]} = V_i$$

$$V_o = V - \left(1 - \frac{V}{R}\right) (n-1)R$$

$$= V - (R - V)(n-1) = V - nR + R + nV - V$$

$$= nV - (n-1)R$$

$$V_o = n R \left[\frac{h_i h_o + h_o + (n-1)R}{h_o + nR} \right] - (n-1)R$$

$$= \frac{h_i h_o n R + n R h_o + \cancel{n R^2} - (n-1) R h_o + \cancel{n(n-1)R^2}}{h_o + nR}$$

$$= \frac{h_i h_o n R + R h_o}{h_o + nR}$$

$$\frac{V_i}{V_o} = \frac{h_i + R \left[\frac{h_o h_i + h_o + (n-1)R}{h_o + nR} \right]}{h_i h_o + n R h_i + R h_o} = \frac{h_i h_o + n R h_i + R h_o h_i + h_o R + (n-1)R^2}{h_i h_o + n R h_i + R h_o}$$

$$h_i h_o + n R h_i + R h_o$$

$$h_o + nR$$

$$= \frac{h_i h_o + h_i h_o n R + n R h_i + h_o R + (n-1)R^2}{h_i h_o + n R h_i + R h_o}$$

$$\frac{V_o}{V_i} = h_i n =$$

$$\frac{h_i h_o n R h_i + R h_o}{h_i h_o + h_i h_o n R h_i + n R h_i + h_o R + (n-1)R^2}$$

Input Resistance

$$r_i + R \left[\frac{h_{ie} r_o + r_o + (n-1)R}{r_o + nR} \right]$$

$$r_o \rightarrow 0$$

$$r_i + \frac{[h_{ie} r_i + (n-1)R]}{n}$$

$$r_i \rightarrow \infty$$

$$\infty$$

$$A \rightarrow \infty$$

$$\infty$$

Output Resistance

$$\frac{(R + h_{ie})(n-1)R + R h_{ie}}{r_o}$$

$$0$$

$$r_o [nR]$$

$$\frac{r_o + (n-1)R + (h_{ie} r_o + 1)R}{r_o + nR + R h_{ie} r_o}$$

$$0$$

$$h_{ie} r_o + R h_{ie} + (n-1)R (h_{ie} + R) + (h_{ie} r_o + 1)R$$

$$= \frac{r_o n R}{r_o + nR + R h_{ie} r_o}$$

G_{min}

$$\frac{h_{ie} r_o n R h_{ie} + R h_{ie}}{r_i r_o + h_{ie} R h_{ie} r_o + n R h_{ie} + r_o R + (n-1) R^2}$$

$$R h_{ie}$$

$$\frac{n R h_{ie} + (n-1) R^2}{r_i}$$

$$= \frac{r_i}{n h_{ie} + (n-1) R}$$

$$h_{ie} r_o n R$$

$$\frac{h_{ie} r_o n R}{r_o + h_{ie} R + n R}$$

$$n$$


2. contd -

Rather than use a VCVS with a large (but uncertain) gain, this problem attempts to use a VCCS with a large (but uncertain) transconductance G_m . Further, the imprecise VCCS, shown in Fig. 2(a), is not all that ideal – its input and output resistances are finite. For simplicity, we use the same symbol for the imprecise VCCS as in Fig. 1(a). It is realized to make the VCVS shown in Fig. 2(b). What is v_o/v_i when $G_m = \infty$?

→ When $G_m = \infty$,


$$\frac{v_o}{v_i} = n$$

Question 3a

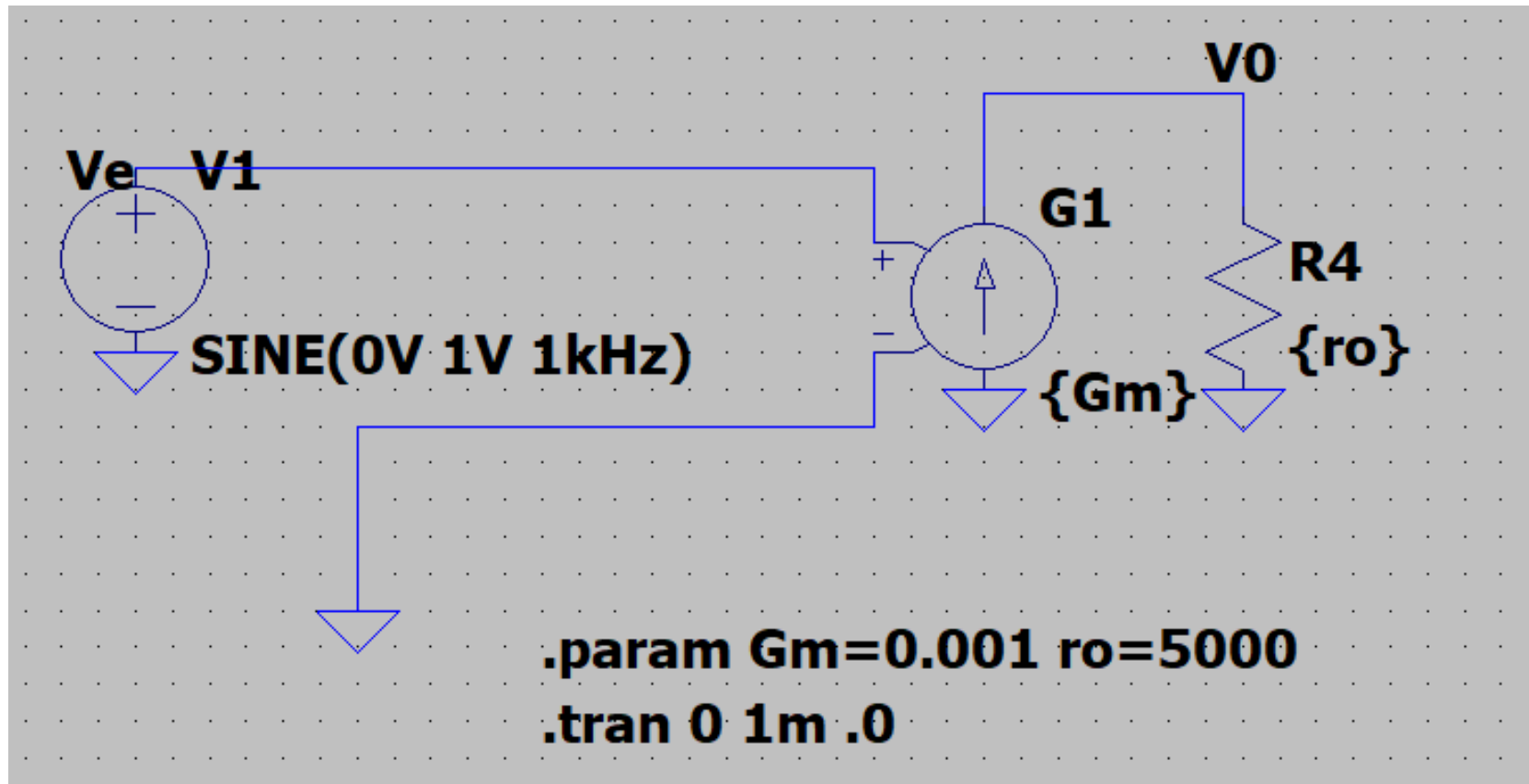


Theoretical Calculation of Gain = $G_m * r_o$

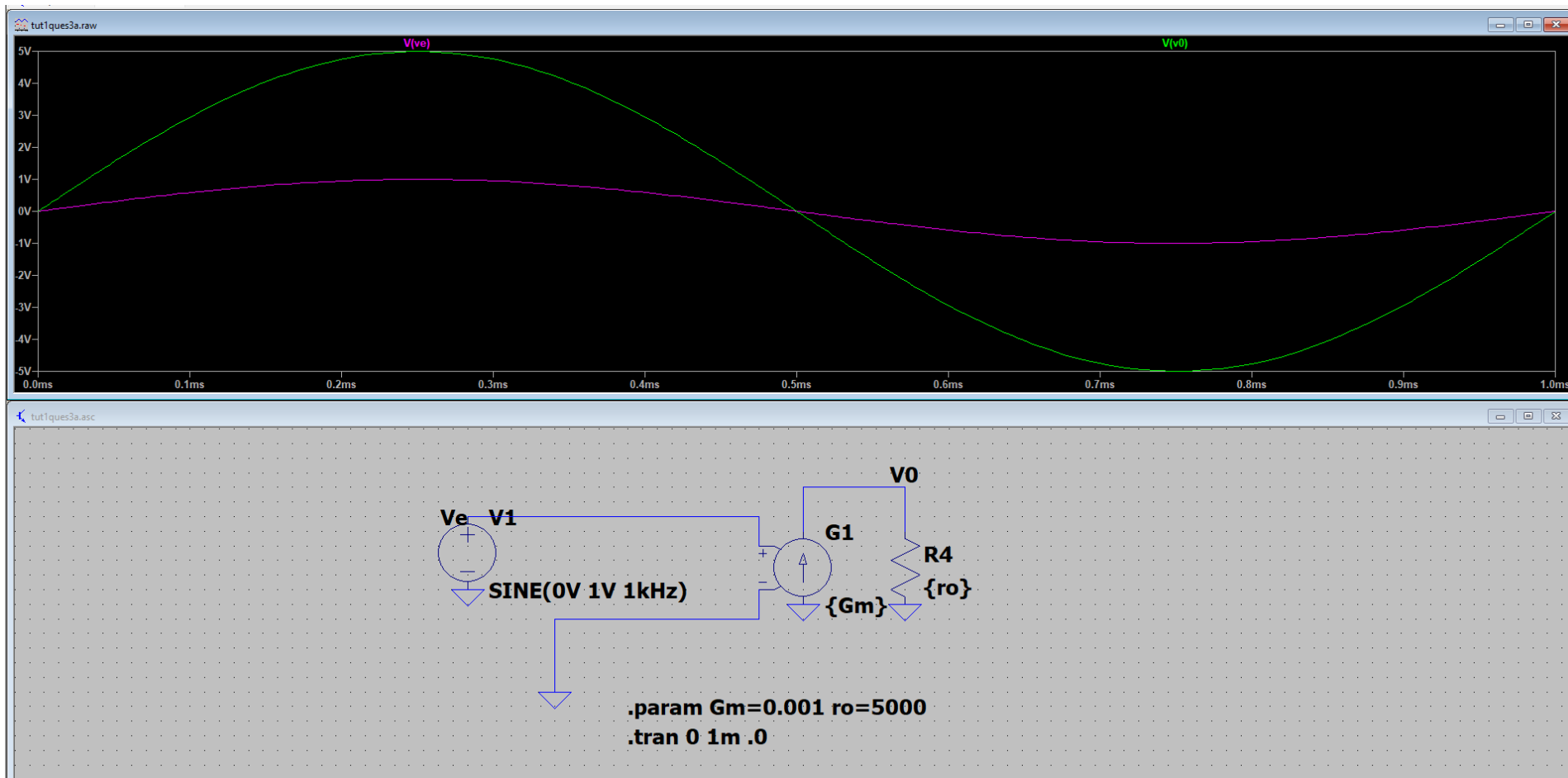- $A_0 = 1\text{mS} * 5\text{k} = 5$ can be observed from plot




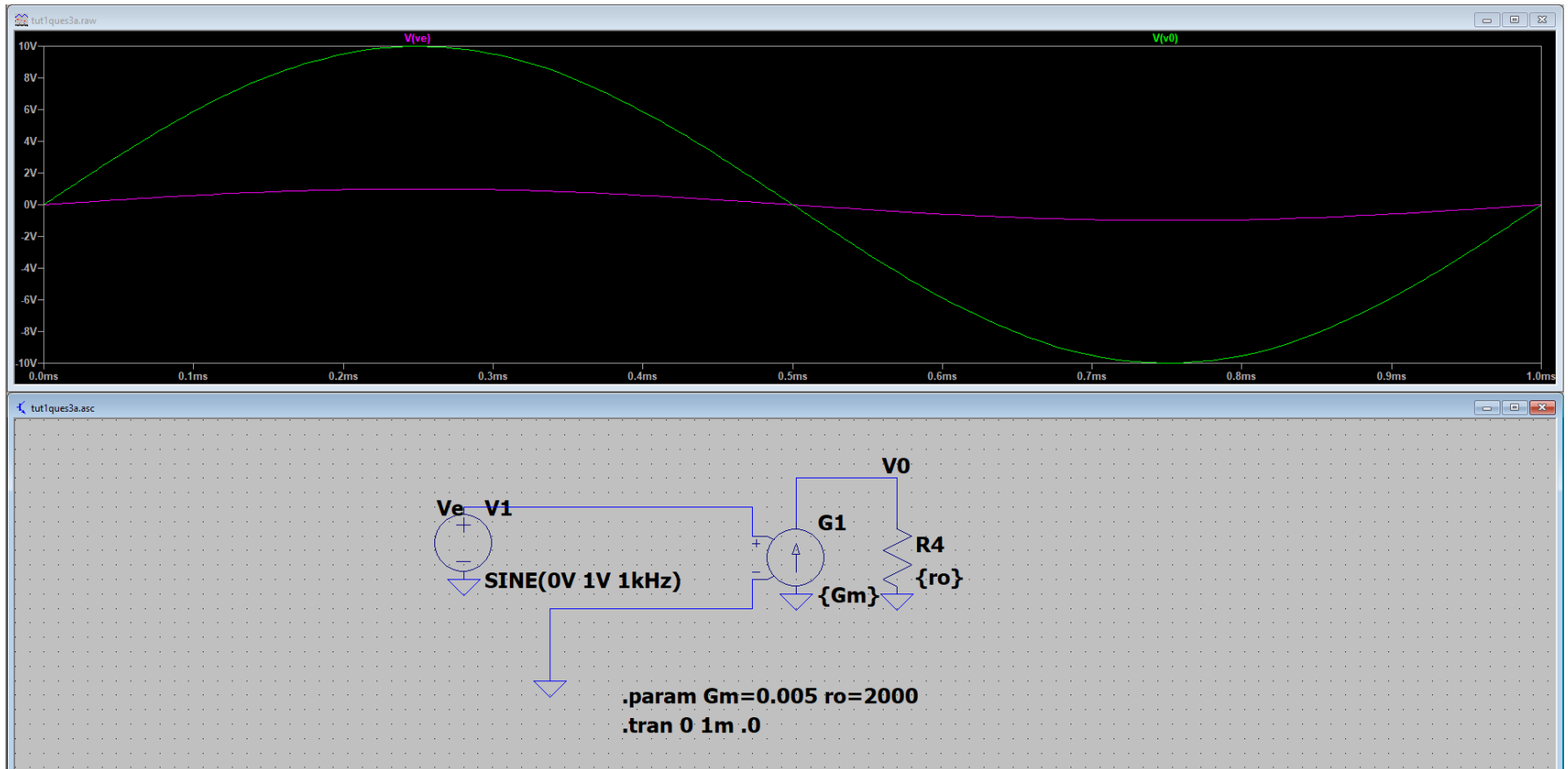- $A_0 = 5S * 2k = 10$ can be observed from plot




Explanation: Using LTSpice, it is verified that the gain graphically = $G_m * r_o$, which is the theoretically expected value.

Question 3b

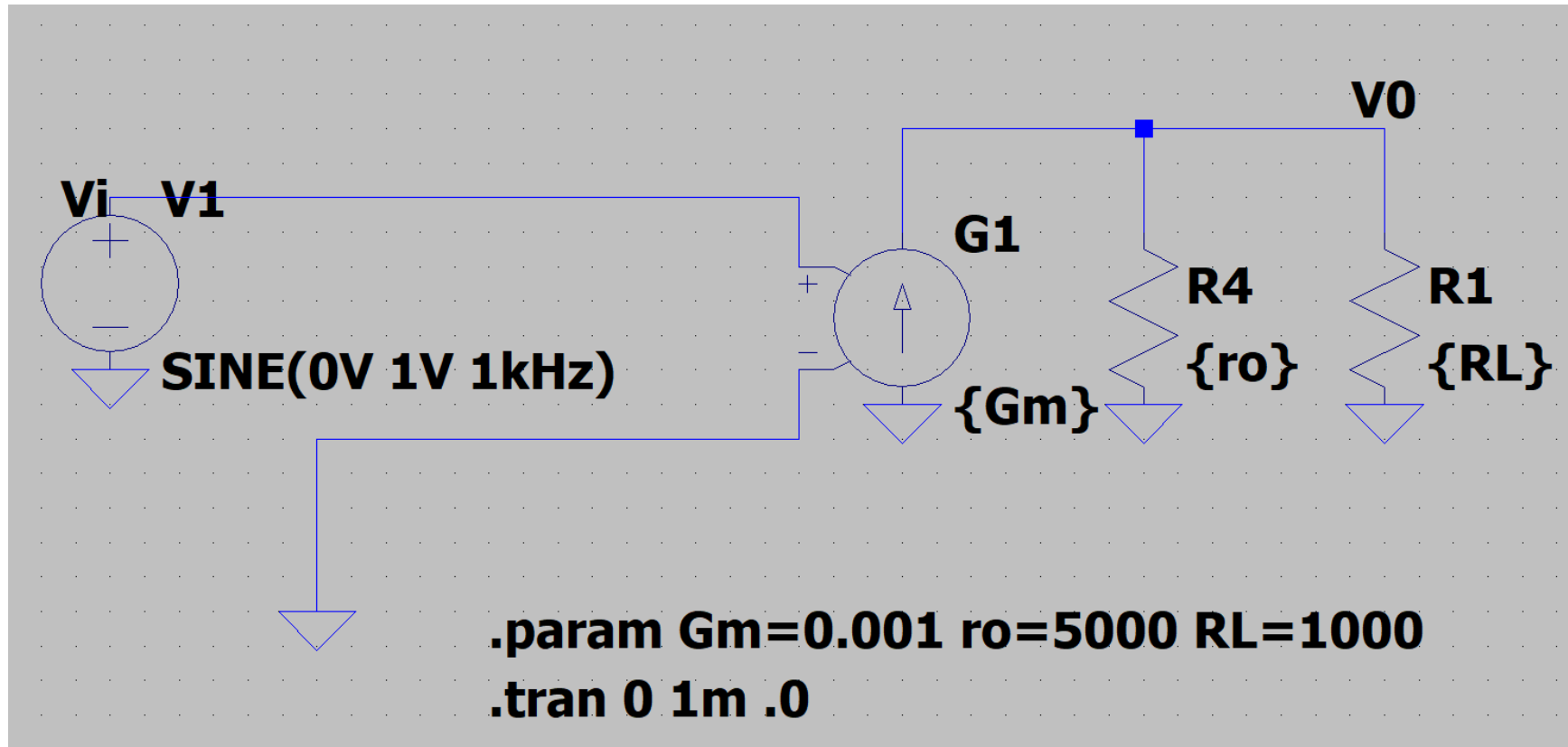


Theoretical Calculation of Gain = $G_m * ((r_o * R_L)/(r_o + R_L))$

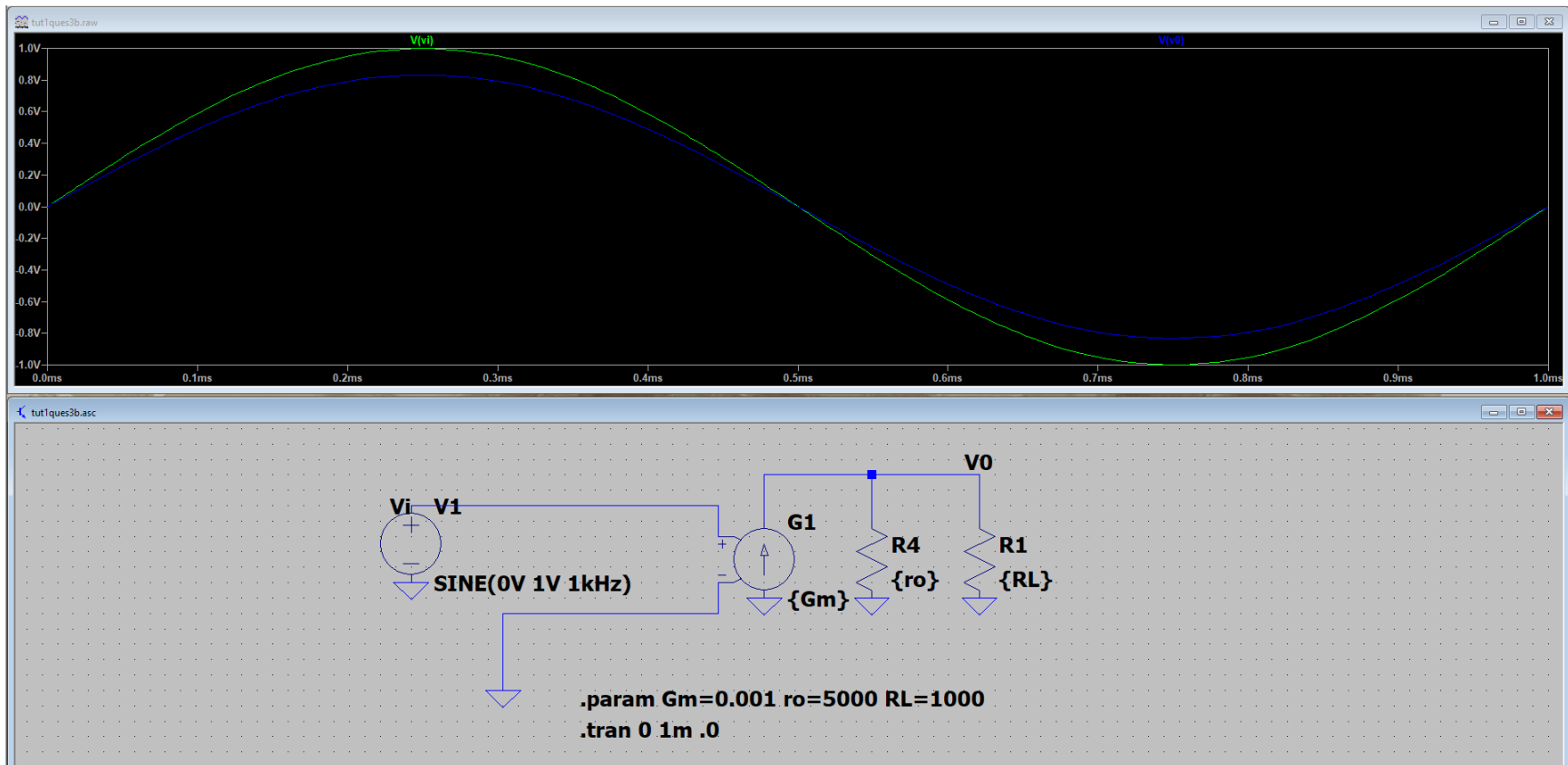- Theoretical gain $A_0 = 1\text{mS} * ((5000 * 1000)/(5000 + 1000)) = 0.83$ can be observed from plot. Here, gain < 1, so amplification is not achieved.



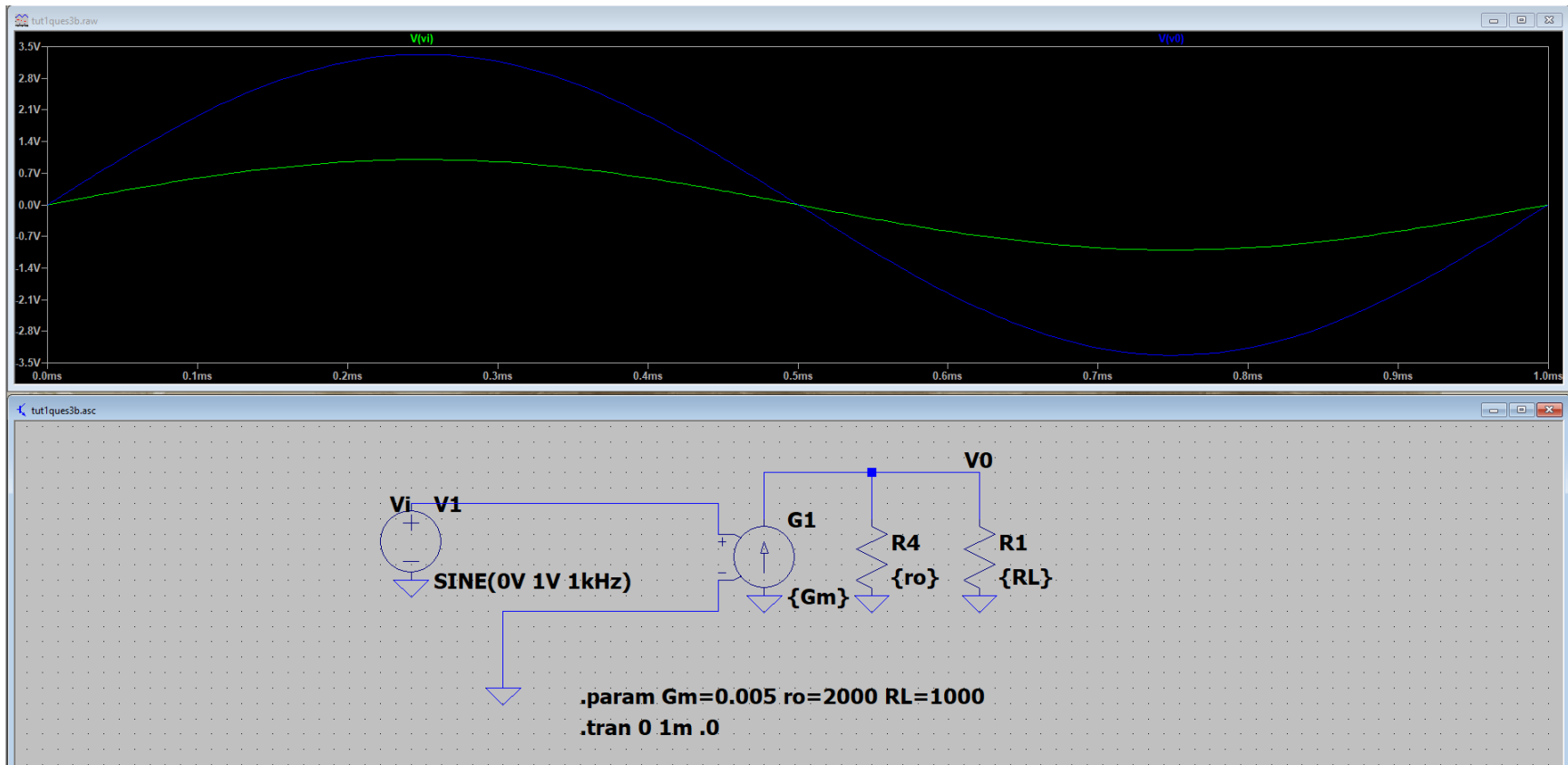- Theoretical gain $A_0 = 5\text{mS} * ((2000 * 1000)/(2000 + 1000)) = 3.33$ can be observed from plot




Explanation: Using LTSpice, it is verified that the gain graphically = $G_m * (r_o * R_L)/(r_o + R_L)$

Effect of R_L = R_L is a load resistance connected in parallel, so it effectively decreases the value of Output resistance r_o . So, clearly, the **Gain decreases**.


Ques 3c

WITHOUT LOAD RESISTANCE

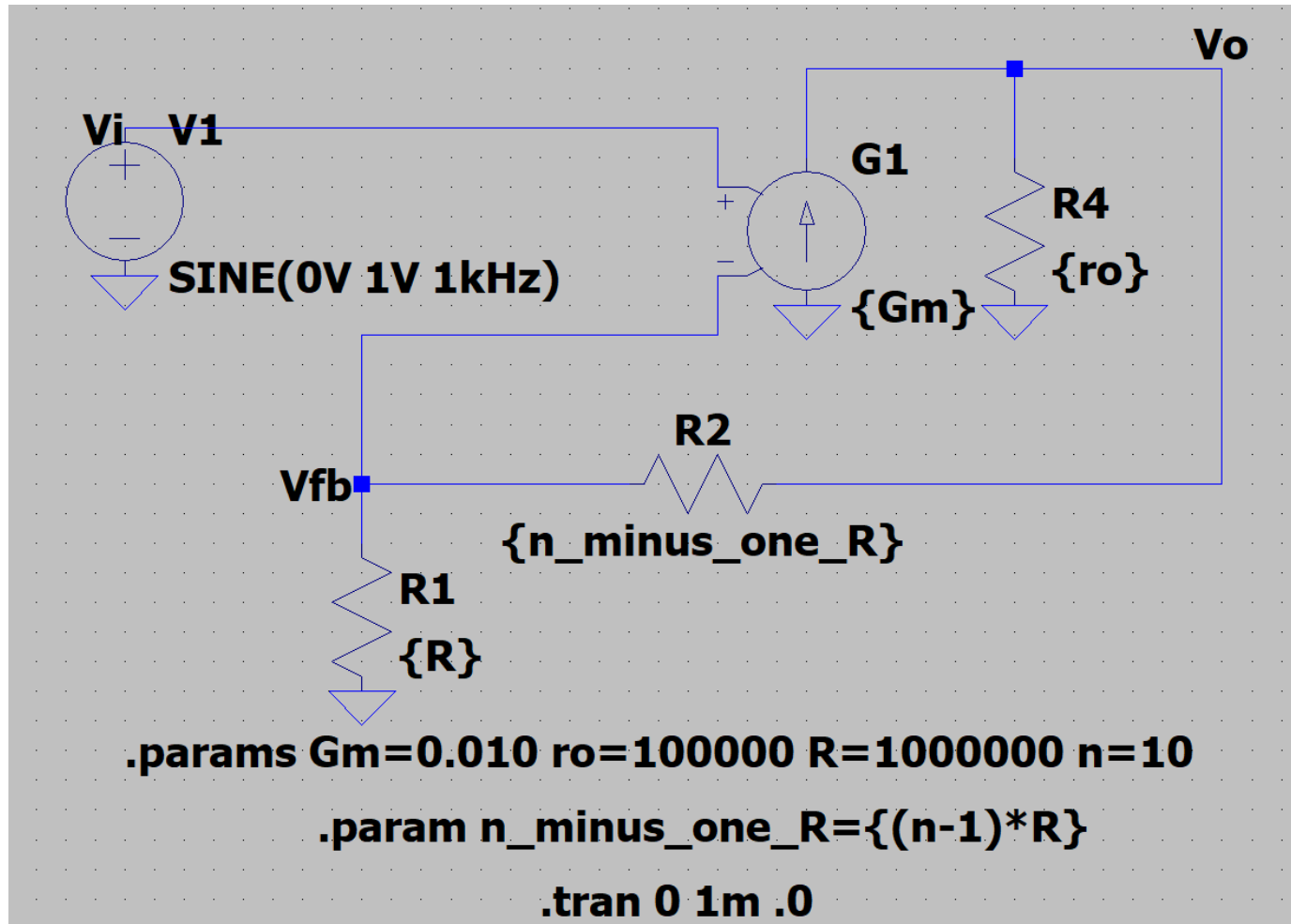


By theoretical calculation, closed loop gain of circuit would be $1/(1/n + 1/A0) = 1/(1/n + 1/(Gm * ro))$

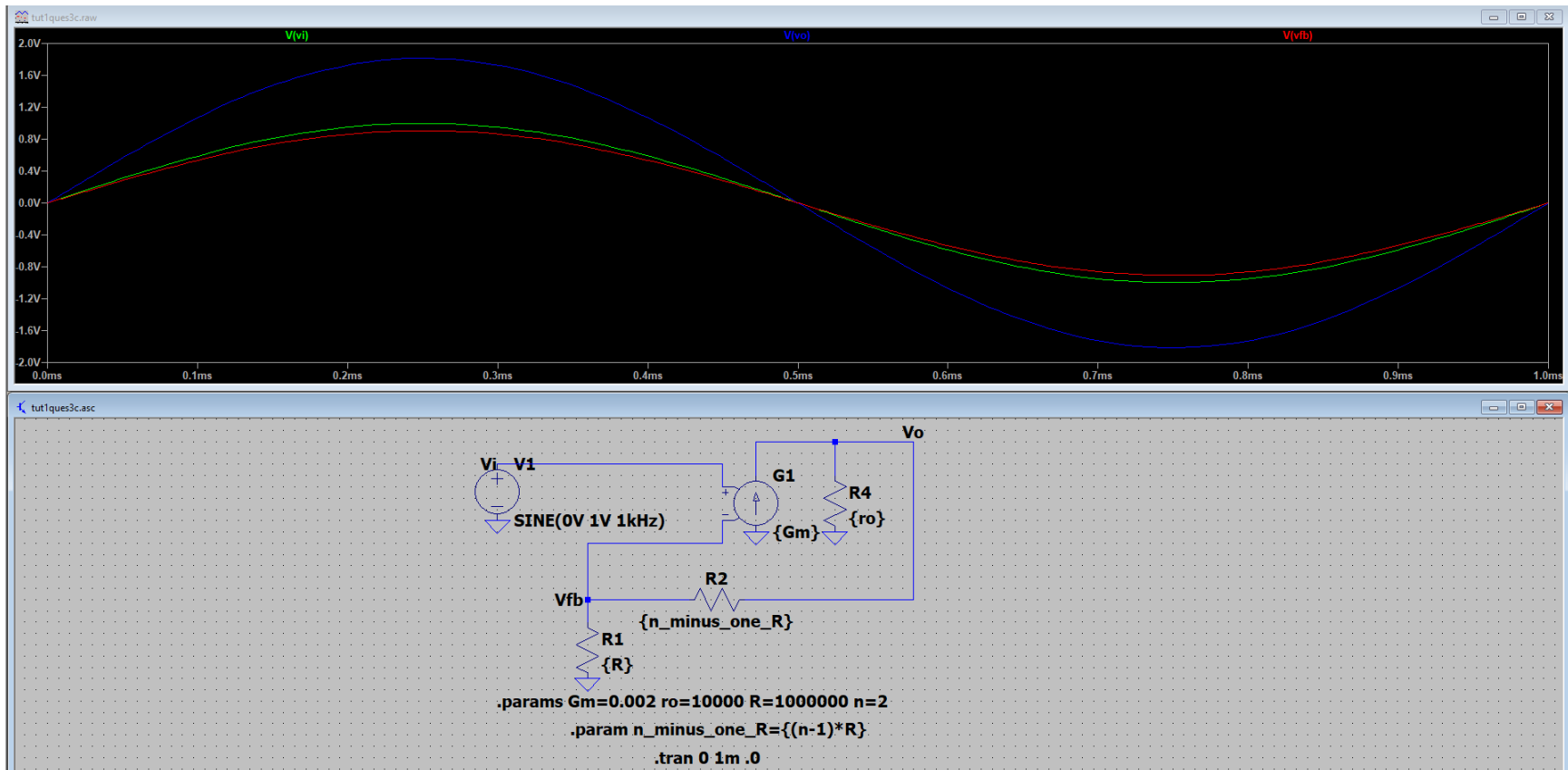
i) Closed Loop Gain = $1/(1/2 + 1/(2\text{mS} * 10\text{k})) = 1/(\frac{1}{2} + \frac{1}{20}) = 1.81$ by calculation, which can be verified graphically



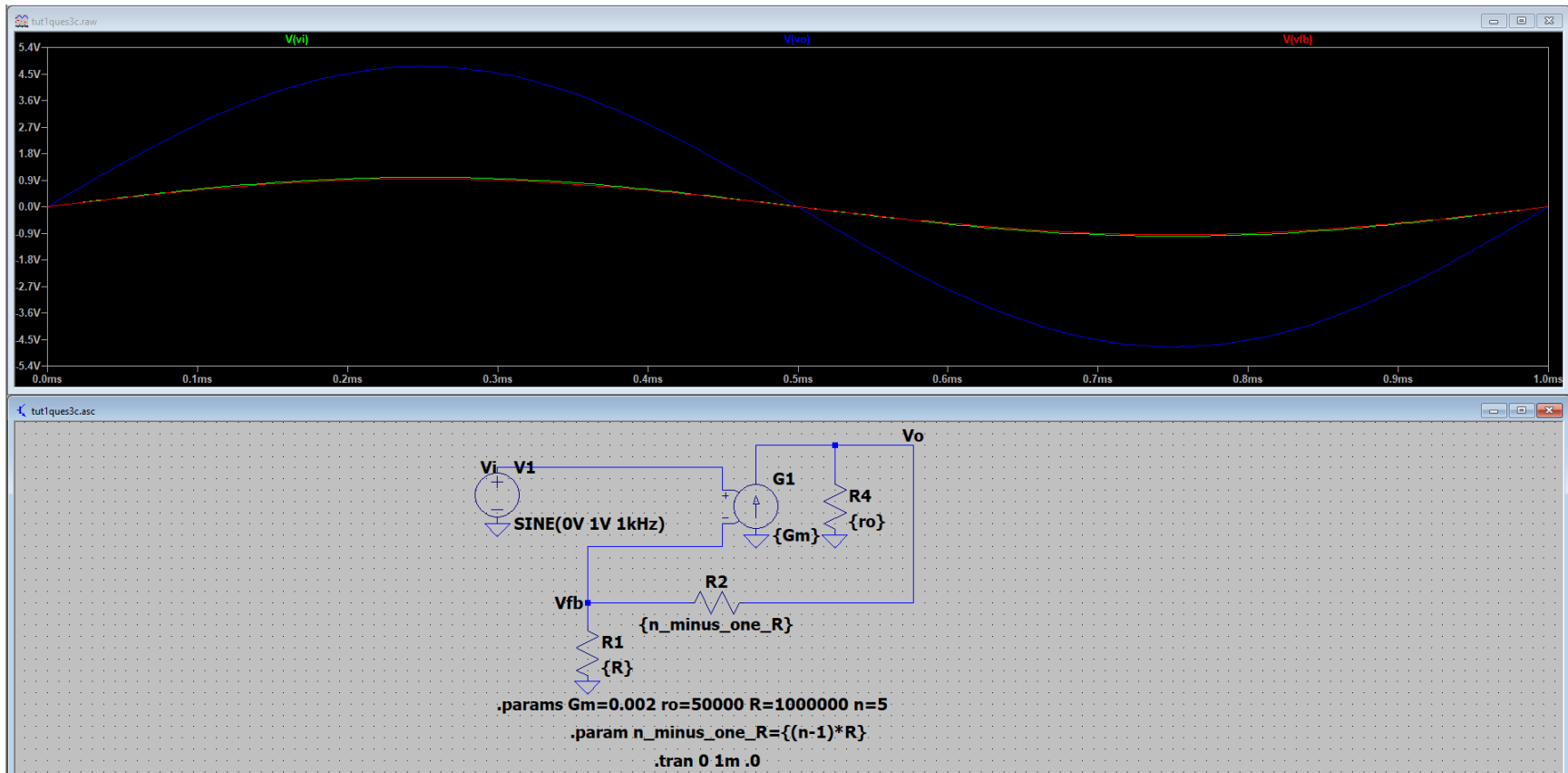
ii) Closed Loop Gain = $1/(1/5 + 1/(2\text{mS} * 50\text{k})) = 1/(1/5 + 1/100) = 4.76$ by calculation, which can be verified graphically



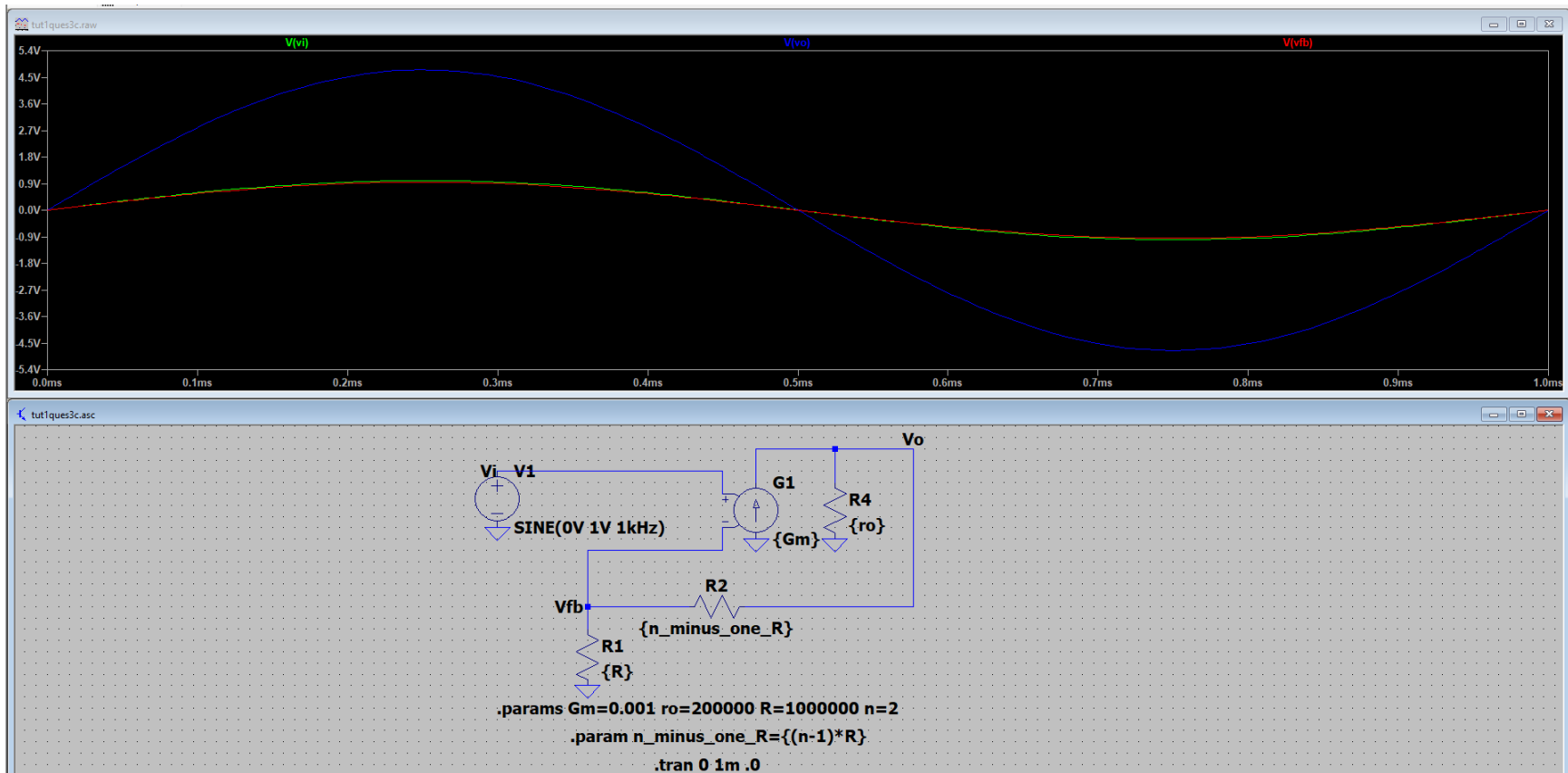
iii) Closed Loop Gain = $1/(1/2 + 1/(1\text{mS} * 200\text{k})) = 1/(1/2 + 1/200) = 1.98$ by calculation, which can be verified graphically



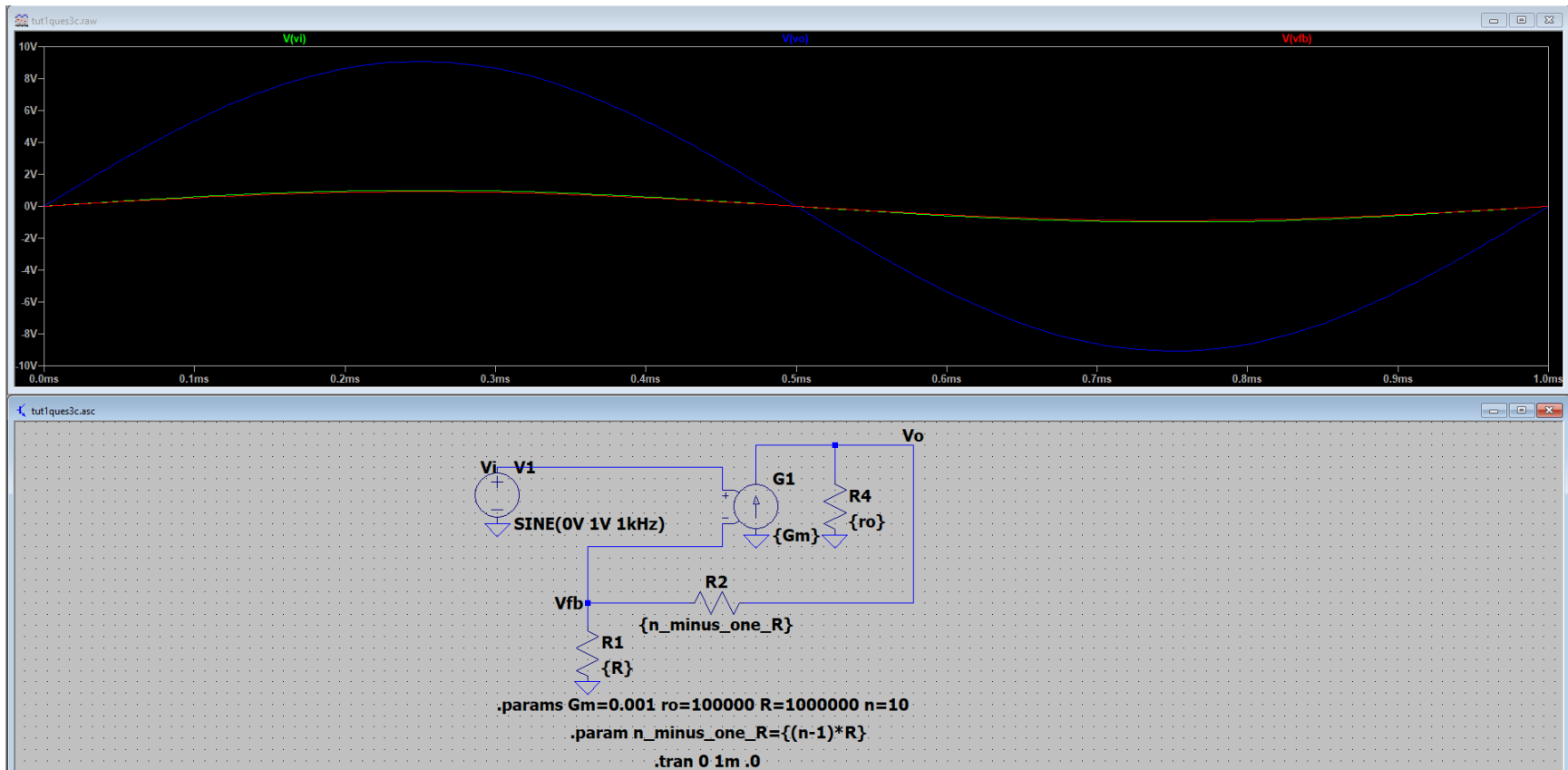
iv) Closed Loop Gain = $1/(1/10 + 1/(1\text{mS} * 100\text{k})) = 1/(1/10 + 1/100) = 9.09$ by calculation, which can be verified graphically



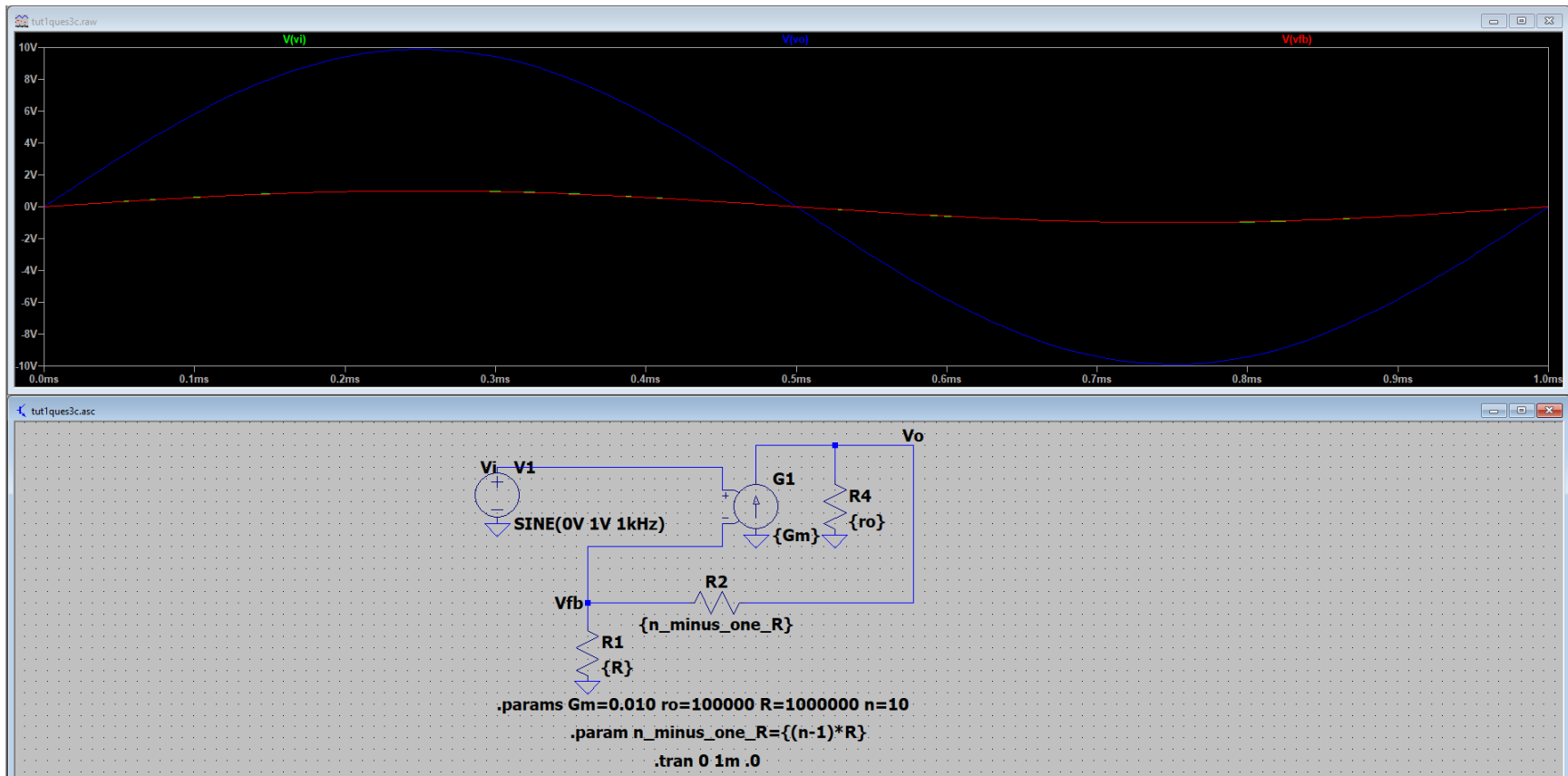v) Closed Loop Gain = $1/(1/10 + 1/(10\text{mS} * 100\text{k})) = 1/(1/10 + 1/100) = 9.90$ by calculation, which can be verified graphically




WITH LOAD RESISTANCE

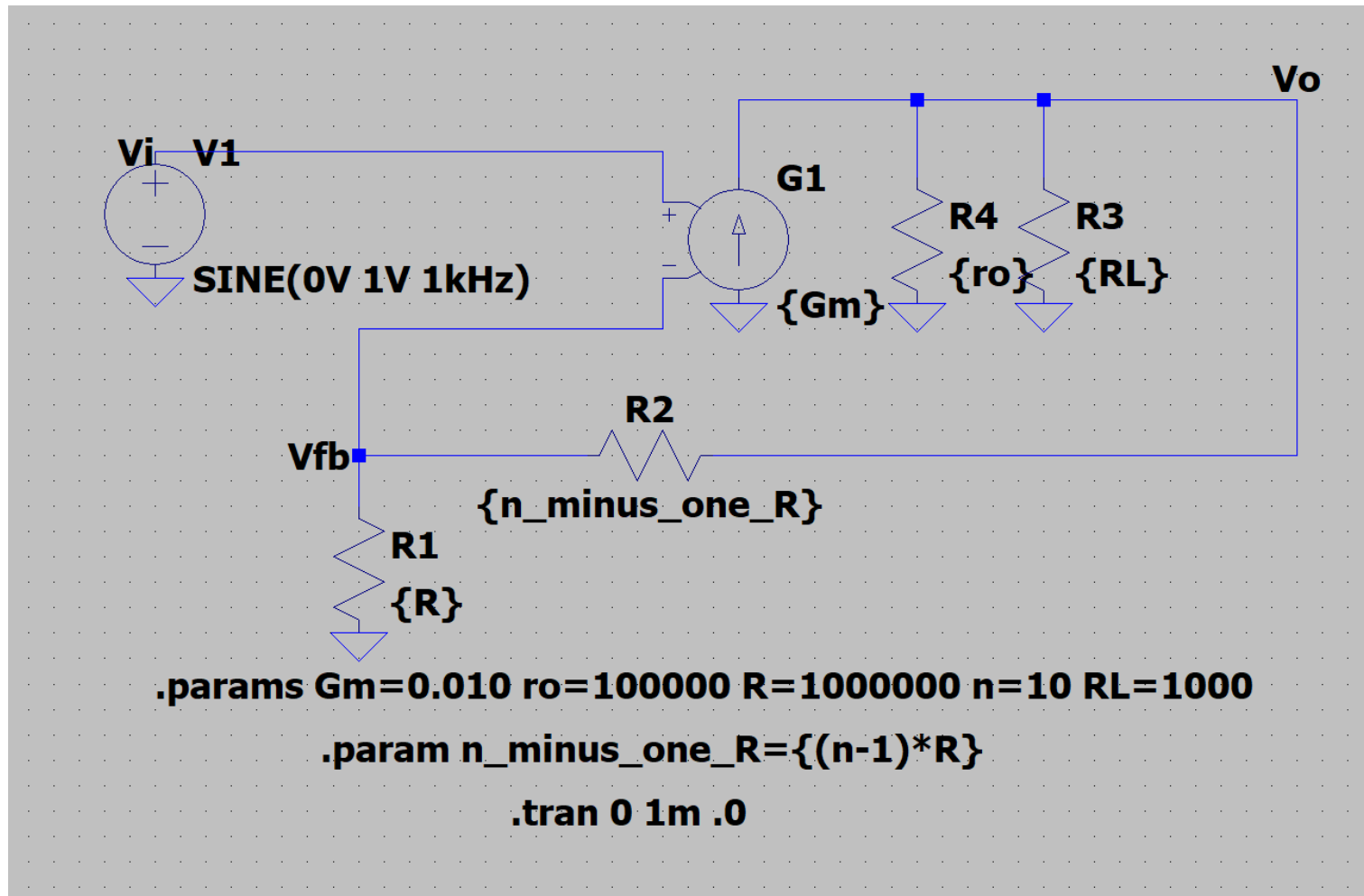


By theoretical calculation, closed loop gain of circuit would be $1/(1/n + 1/(Gm * (ro * RL/(ro + RL))))$

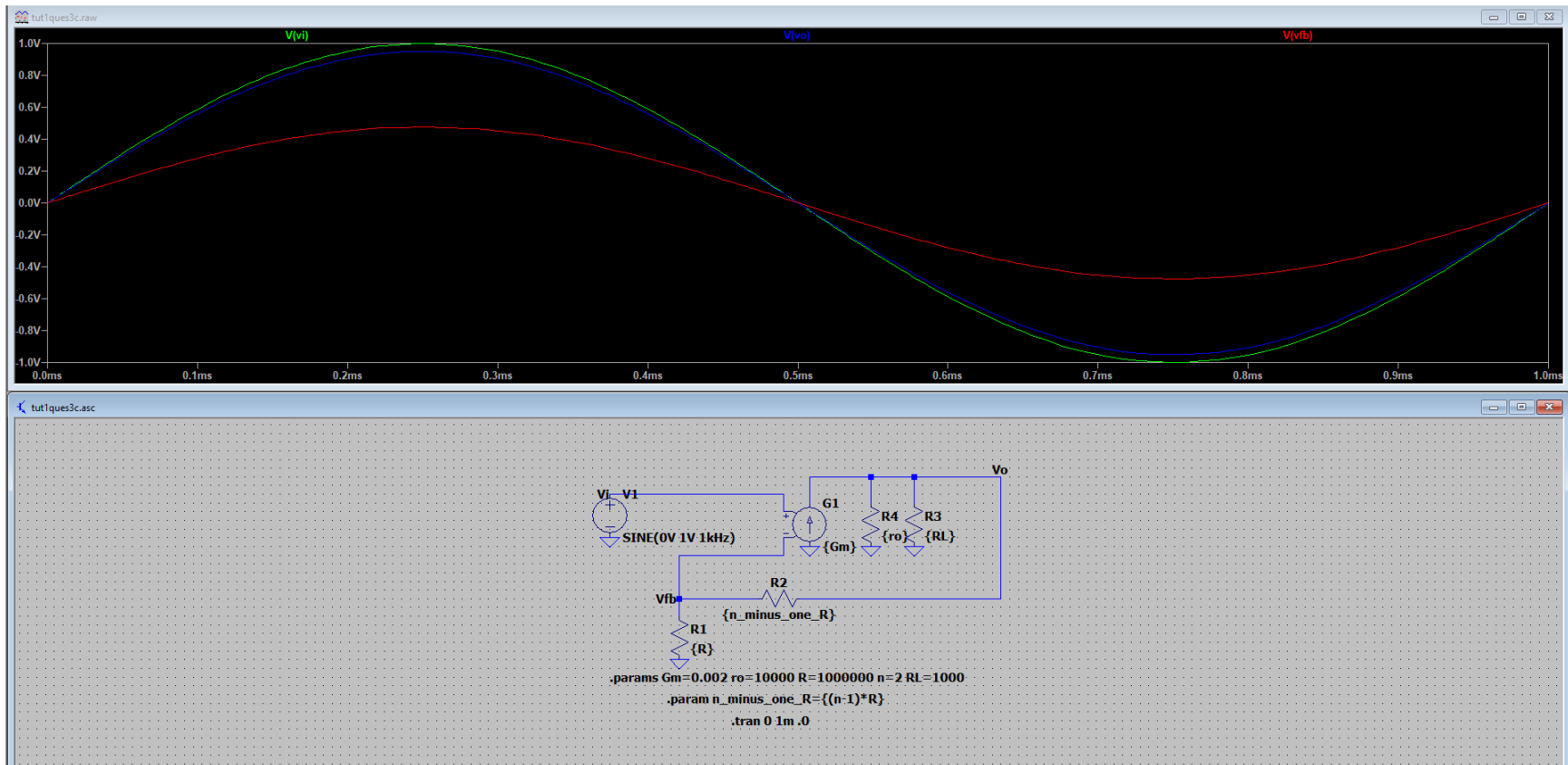
i) Gain 0.95 by theoretical calculation, which matches with simulated values



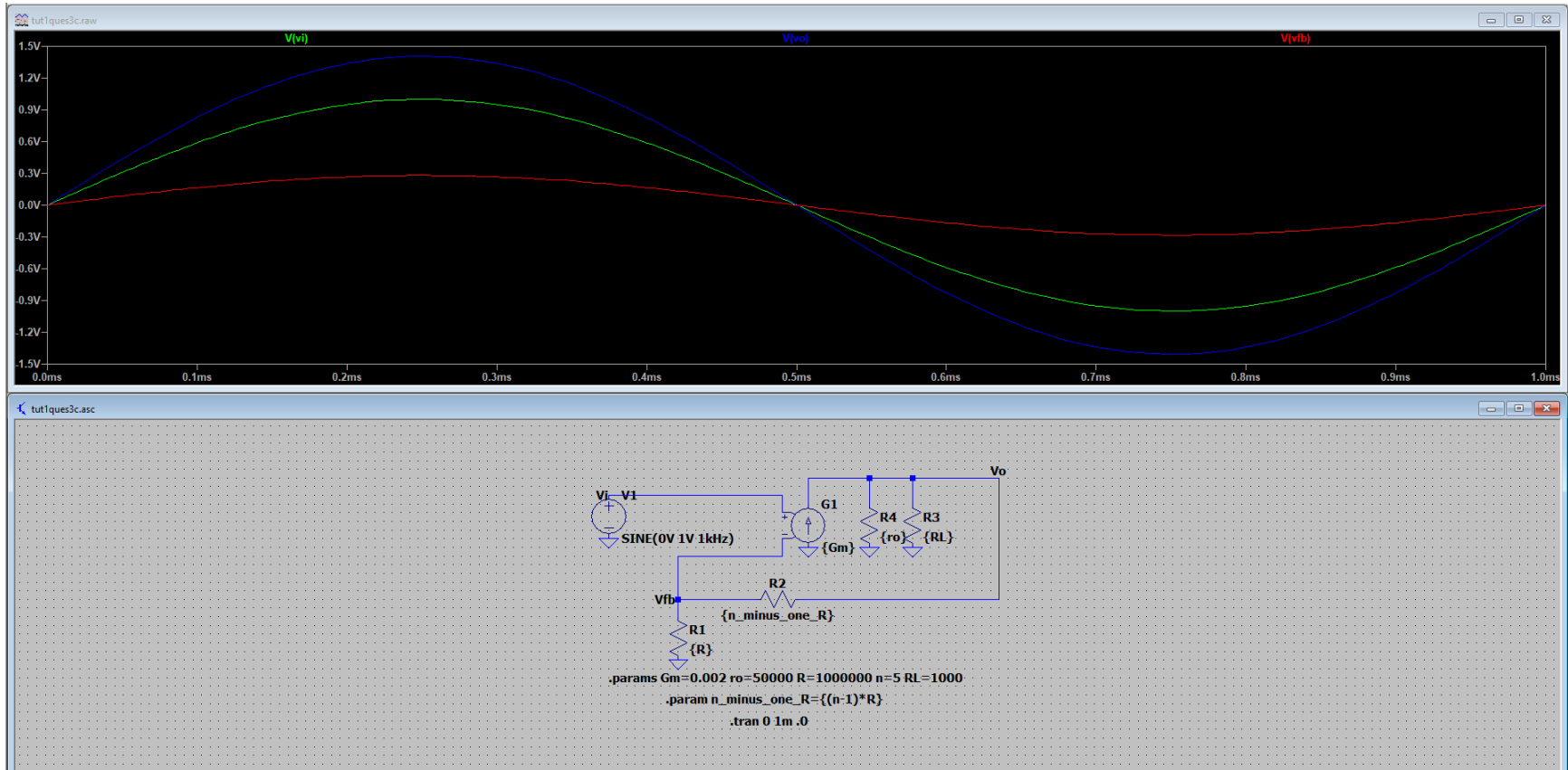
ii) Gain 1.408 by theoretical calculation, which matches with simulated values



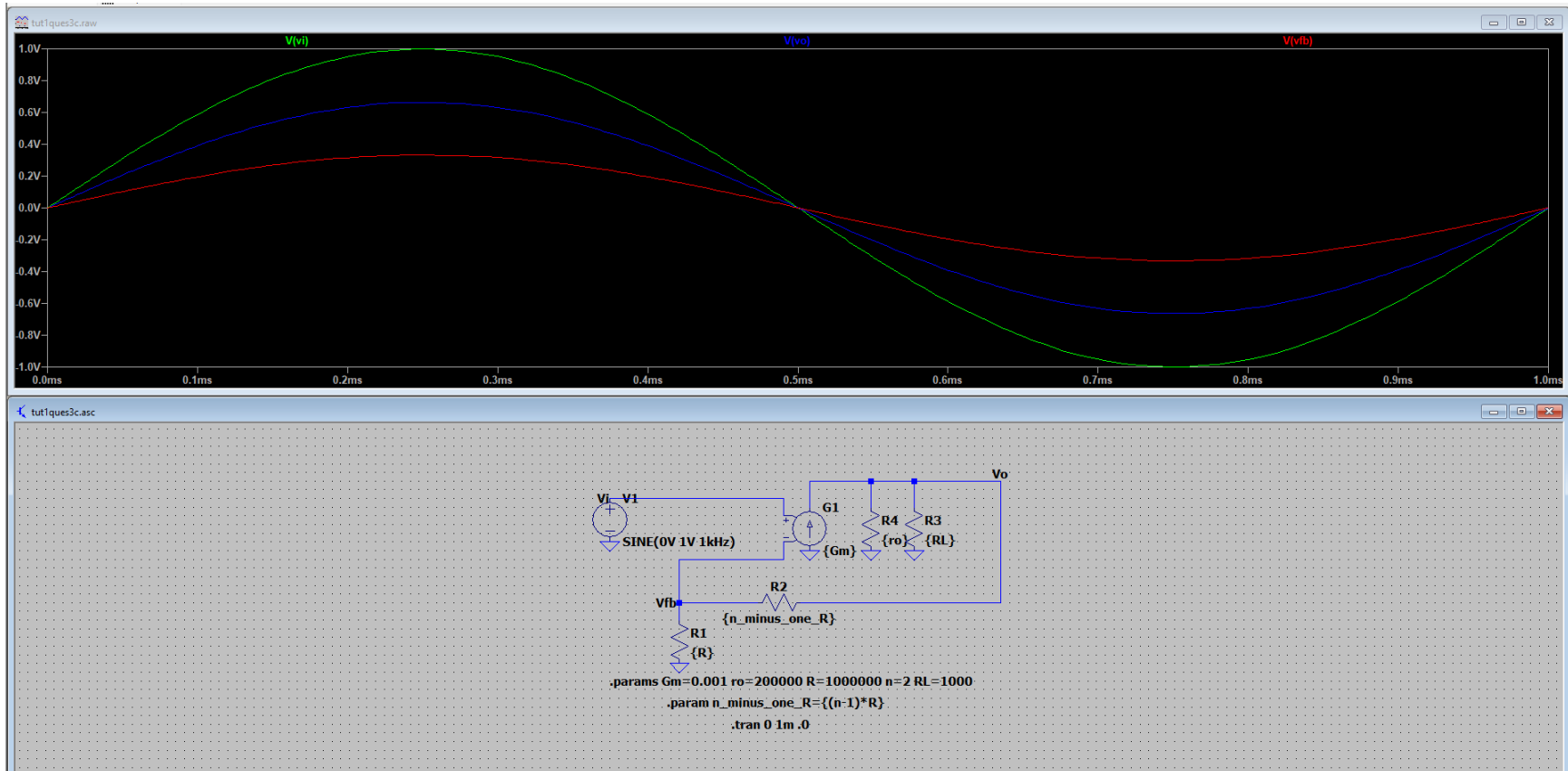
iii) Gain 0.66 by theoretical calculation, which matches with simulated values



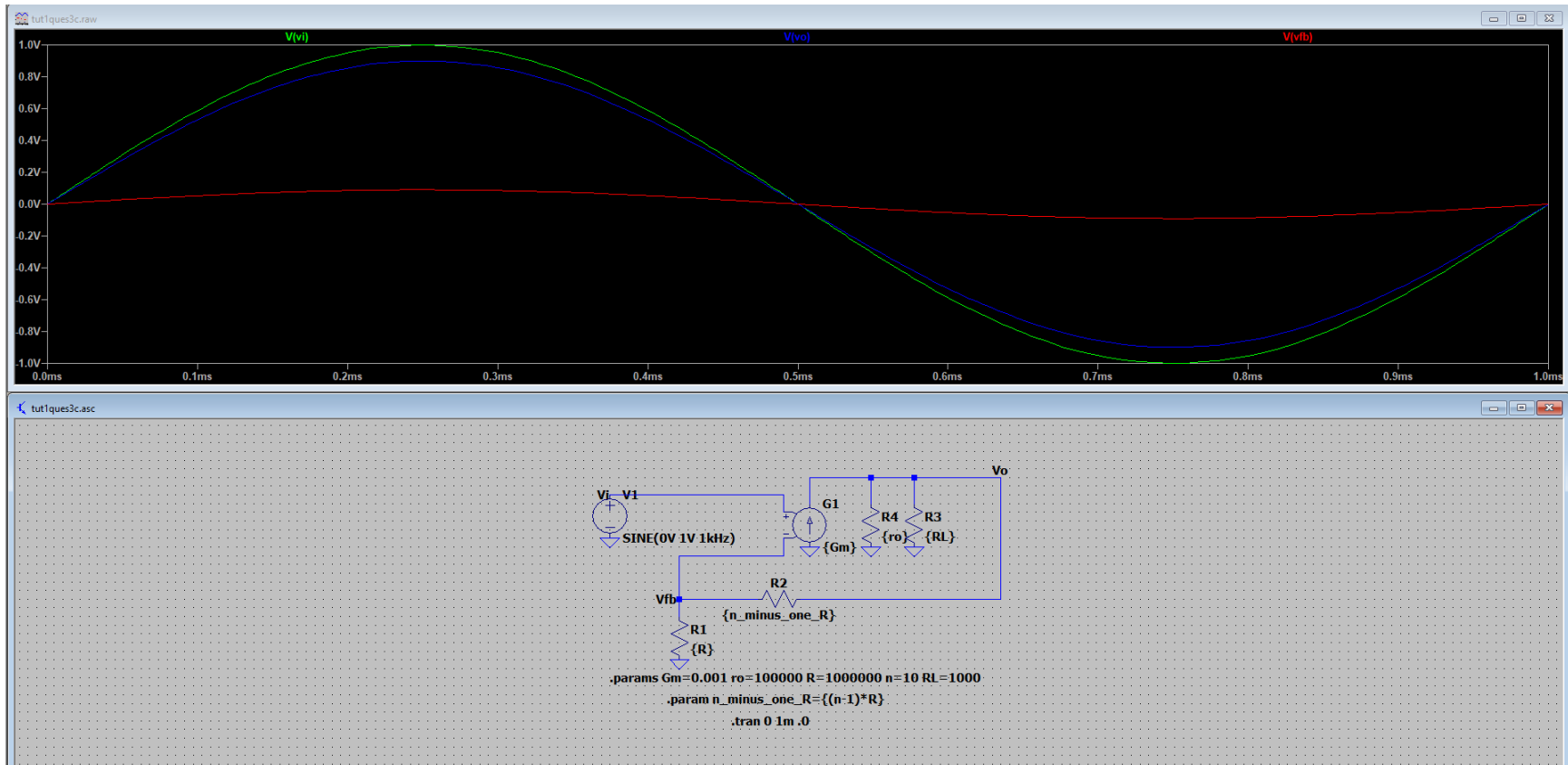iv) Gain 0.90 by theoretical calculation, which matches with simulated values



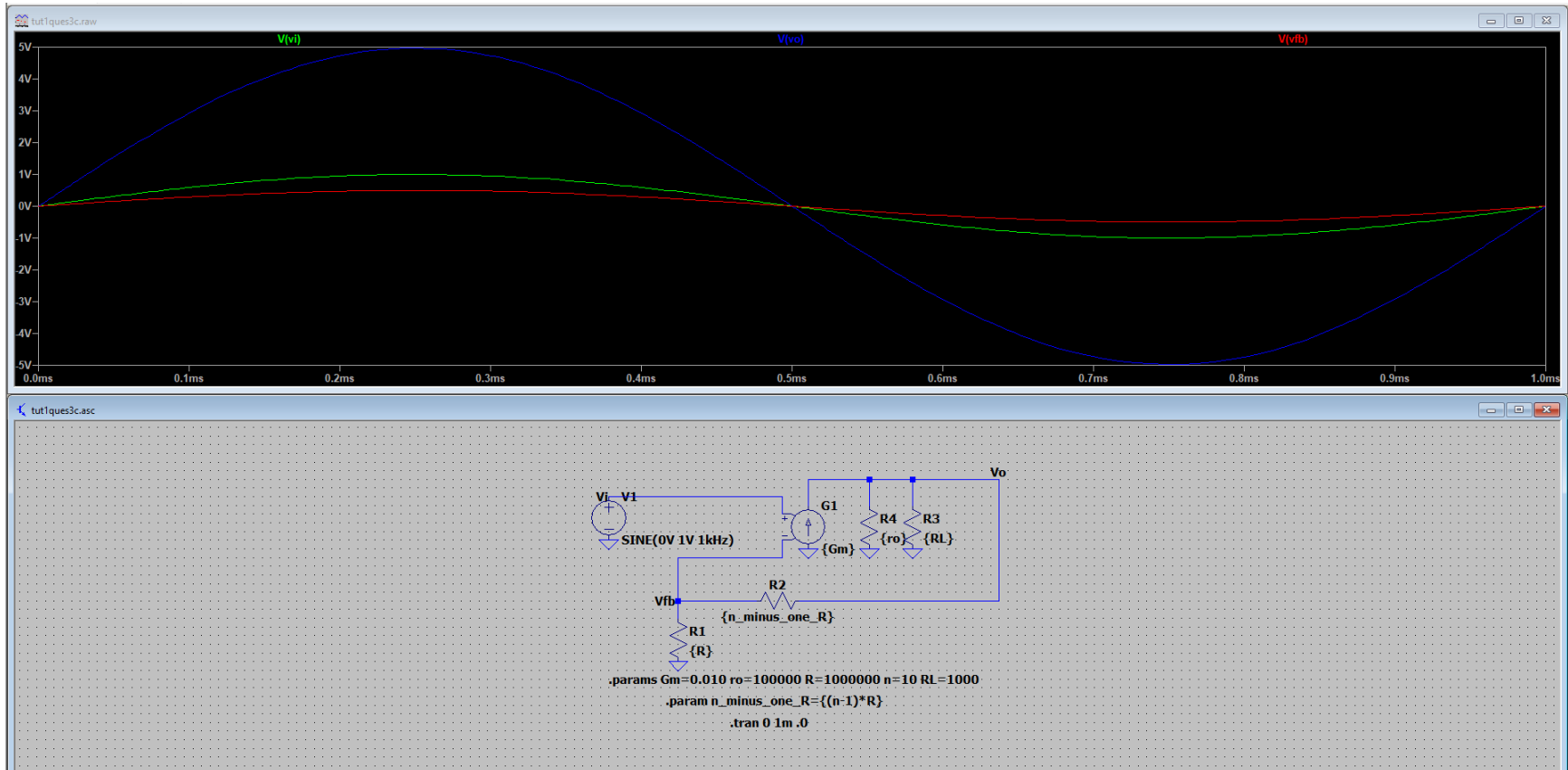v) Gain 4.97 by theoretical calculation, which matches with simulated values



Explanation: Compared to a and b, we see that the closed loop gain value is not the same as open loop gain, but depends on the value of n also.

It is verified using LTSpice that the gain is $1/(1/n + 1/(G_m * r_o))$ graphically. Now,

- As the value of VCVS gain ($G_m * r_o$) increases, the closed loop gain tends to n. In the limit as VCVS gain becomes infinite, the closed loop gain = n
- As the value of n increases, the closed loop gain also increases