

ANALOG SYSTEMS : PROBLEM SET 8

Problem 1

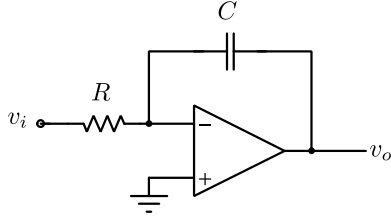


Figure 1: Circuit for Problem 1.

Fig. 1 shows an integrator. The opamp is ideal. The capacitor is initially uncharged. $v_i = \sin(\omega_o t)u(t)$, where $\omega_o = 1/RC$ and $u(t)$ is the unit step function. Draw to scale, on the same graph, v_i and v_o . Repeat with $v_i = \cos(\omega_o t)u(t)$.

Problem 2

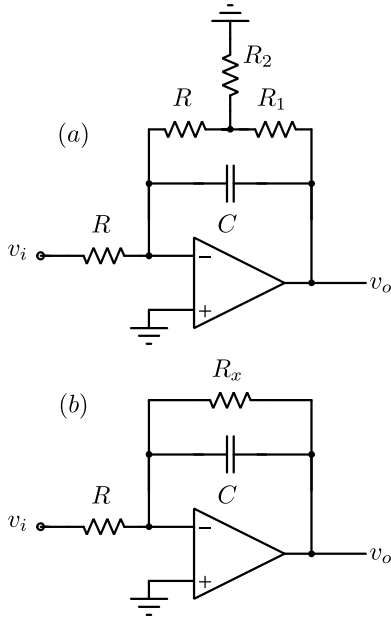


Figure 2: Circuit for Problem 2.

All opamps are ideal in Fig. 2. Determine the dc gain and 3-dB bandwidth of the circuit of Fig. 2(a). What R_x should be chosen in the circuit of Fig. 2(b) to obtain the same transfer function?

Evaluate R_x in the limiting case when $R_1, R_2 \ll R$. What might be the utility of the T-network in Fig. 2(a)?

Problem 3

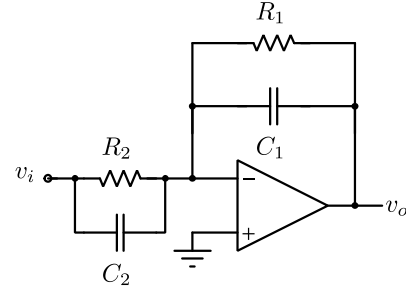


Figure 3: Circuit for Problem 3.

Determine the transfer function of the circuit of Fig. 3. Sketch a Bode plot.

Problem 4

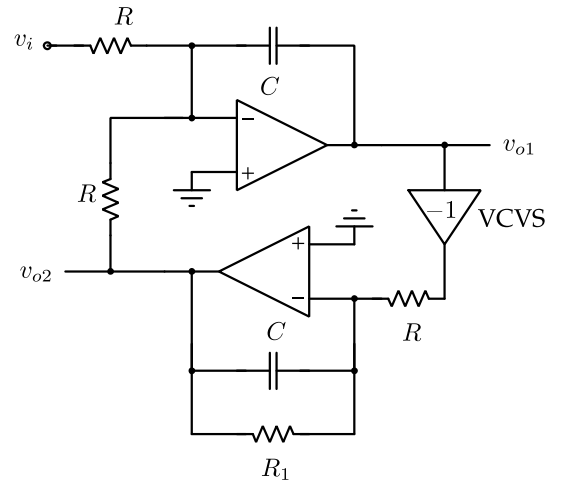


Figure 4: Circuit for Problem 4.

The opamps are ideal. Determine the transfer functions from the v_i to v_{o1} and v_{o2} .

Problem 5

The opamps are ideal. The initial conditions are marked. Plot the waveforms v_{o1} and v_{o2} .

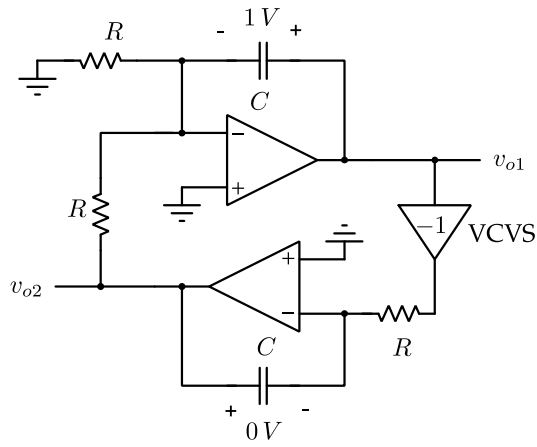


Figure 5: Circuit for Problem 5.

Problem 6

Consider the integrator of Fig. 1. The opamp is not ideal, but has a frequency dependent gain determined by GB/s , where GB denotes its gain-bandwidth product. Determine the integrator's transfer function, when a nonideal opamp is used.

Problem 7

Use the results of Problem 6 to evaluate the transfer function of the circuit of Fig. 4 when the opamps have a finite gain-bandwidth product. The VCVS can be assumed to be ideal.

Problem 1

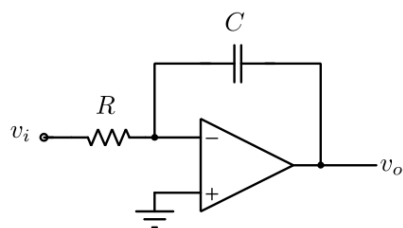


Figure 1: Circuit for Problem 1.

Fig. 1 shows an integrator. The opamp is ideal. The capacitor is initially uncharged. $v_i = \sin(\omega_o t)u(t)$, where $\omega_o = 1/RC$ and $u(t)$ is the unit step function. Draw to scale, on the same graph, v_i and v_o . Repeat with $v_i = \cos(\omega_o t)u(t)$.

$$V_i = \sin \omega_o t u(t)$$

$$V_i(\omega) = \frac{\omega_o}{s^2 + \omega_o^2}$$


$$V_o = -\frac{1}{sRC} \frac{\omega_o}{s^2 + \omega_o^2}$$

$$= \left(\frac{\omega_o}{RC} \right) \frac{1}{s(s^2 + \omega_o^2)}$$

$$= \left(\frac{\omega_o}{RC} \right) \left[\frac{1}{s} - \frac{s}{s^2 + \omega_o^2} \right] \frac{1}{\omega_o^2}$$

$$= -\frac{j}{\omega_o RC} \left[u(t) - \cos \omega_o t u(t) \right]$$
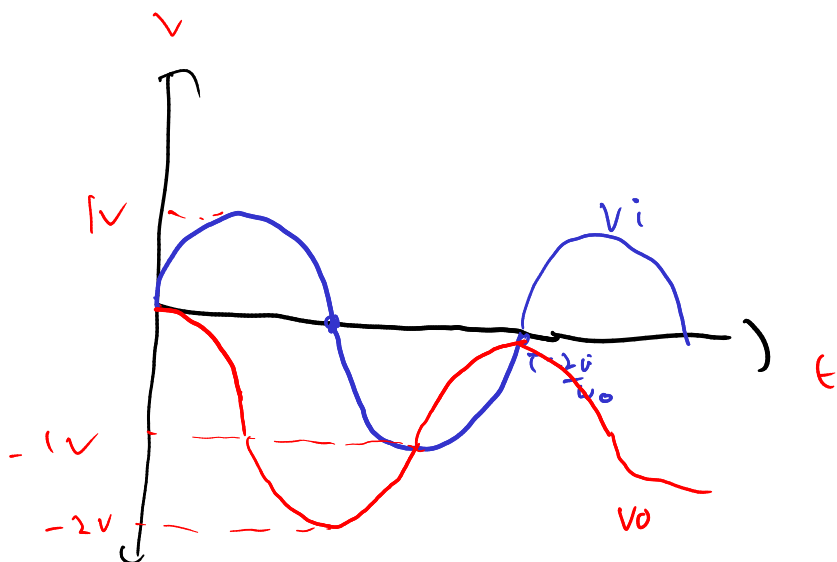
$$= \frac{1}{\omega_o RC} \left[\cos \omega_o t - 1 \right] u(t)$$



$$V_o RC = v_i$$

$$\frac{V_o}{V_i} = -\frac{1}{sRC}$$

Rough

$$\cos \omega_o t \rightarrow \frac{e^{j\omega} + e^{-j\omega}}{2}$$

$$\frac{1}{2} \left(\frac{1}{s-j\omega_o} + \frac{1}{s+j\omega_o} \right)$$

$$\frac{1}{2} \left(\frac{2s}{s^2 + \omega_o^2} \right) = \left(\frac{s}{s^2 + \omega_o^2} \right)$$

$$\sin \omega_o t \rightarrow \frac{\omega_o}{s^2 + \omega_o^2}$$


$$v_i = (\cos \omega_0 t) u(t)$$

$$\mathcal{I} \int v_i = \frac{1}{s^2 + \omega_0^2}$$

$$v_o \mathcal{I} \left\{ \left(\frac{1}{RC} \right) \frac{1}{s^2 + \omega_0^2} \right\} = \frac{1}{s} (-1)$$

$$= \left(-\frac{1}{RC} \right) \frac{1}{s^2 + \omega_0^2} \mathcal{I}^{-1}$$

$$v_o(t) = \left(-\frac{1}{RC} \right) \frac{\sin \omega_0 t}{\omega_0} = -\sin \omega_0 t$$

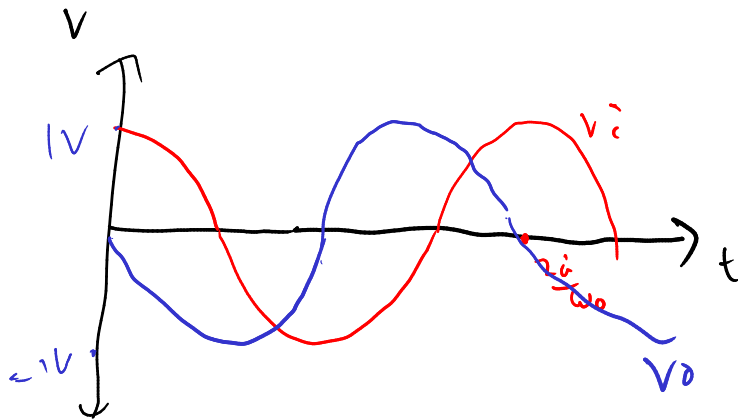

Problem 2

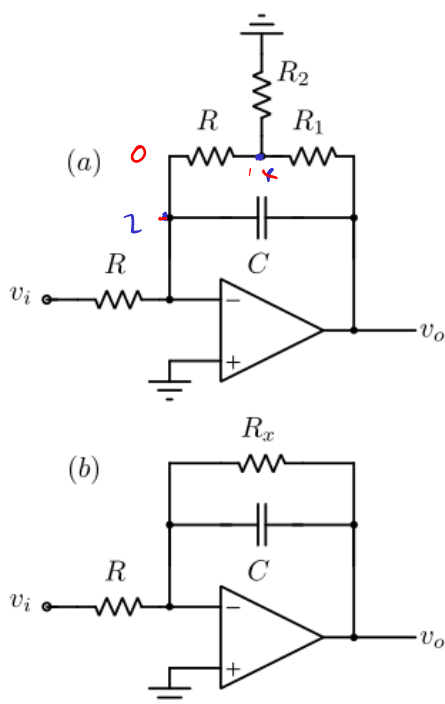


Figure 2: Circuit for Problem 2.

All opamps are ideal in Fig. 2. Determine the dc gain and 3-dB bandwidth of the circuit of Fig. 2(a). What R_x should be chosen in the circuit of Fig. 2(b) to obtain the same transfer function?

Evaluate R_x in the limiting case when $R_1, R_2 \ll R$. What might be the utility of the T-network in Fig. 2(a)?

a) At node 1,

$$\frac{x}{R_2} + \frac{x - v_o}{R_1} + \frac{x}{R} = 0$$

$$0 - \frac{v_i}{R} + (0 - v_o) \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R} \right) = 0$$

$$-\left(\frac{v_i}{R} + v_o \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R} \right) \right) = \frac{x}{R}$$

$$= \left(\frac{v_o}{R R_1} \right)$$

$$\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2}$$

$$-\frac{v_i}{R} = v_o \left(\frac{1}{R R_1} \right) + v_o \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$v_i = -v_o \left[\frac{1}{R R_1} + \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) \right] R$$

$$\frac{v_o}{v_i} = - \frac{1}{R} \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right) \bigg/ \left(\frac{1}{R R_1} + \frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$b) \quad v_o \left(\frac{1}{R R_1} \right) = -v_i \left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{v_o}{v_i} = - \left(\frac{1}{R} \right) \left(\frac{1}{\left(\frac{1}{R R_1} + \frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)} \right)$$

$$\frac{1}{R_x} = \frac{1}{R R_1} \left(\frac{1}{\left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2} \right)} \right)$$

$$A(\text{gain}) = -R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\omega_{-3dB} = \left(\frac{1}{C R_x} \right) = \frac{1}{C R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2} \right)}$$

Limiting Case

$$R_x = R R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2} \right) \approx R \left(1 + \frac{R_1}{R_2} \right)$$

Same as inverting amplifier, so if $R_2 \ll R_1$,
 R_x effective can be very large.

Problem 3

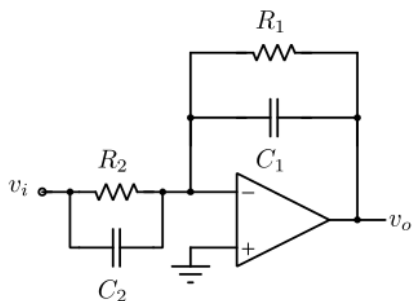


Figure 3: Circuit for Problem 3.

Determine the transfer function of the circuit of Fig. 3.
Sketch a Bode plot.

$$Z_1 = \frac{1}{\frac{1}{R_1} + sC_1} = \frac{R_1}{1 + sCR_1}$$



$$Z_2 = \frac{R_2}{1 + sCR_2}$$

$$\frac{V_i}{Z_2} = -\frac{V_o}{Z_1}$$

$$V_o = -Z_1 \frac{V_i}{Z_2}$$


$$H(s) = \frac{-\frac{R_1}{1 + sCR_1}}{\frac{R_2}{1 + sCR_2}} = -\frac{R_1}{R_2} \left(\frac{1 + sCR_2}{1 + sCR_1} \right)$$

Bode plot $R_1, C_1, 1/R_2 C_2$

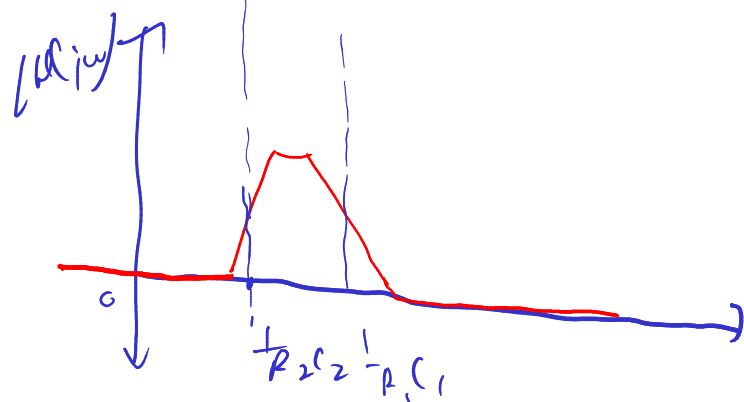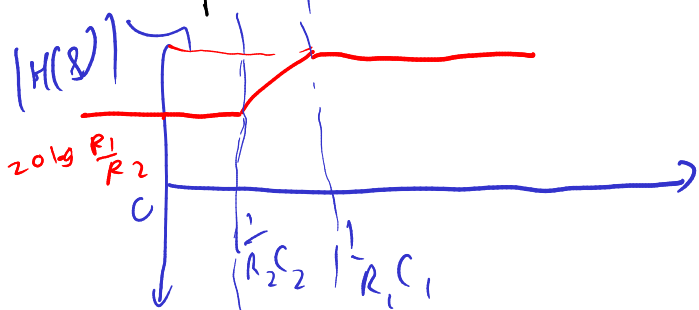

Bode plot

$$R_1 C_1 \gg R_2 C_2$$

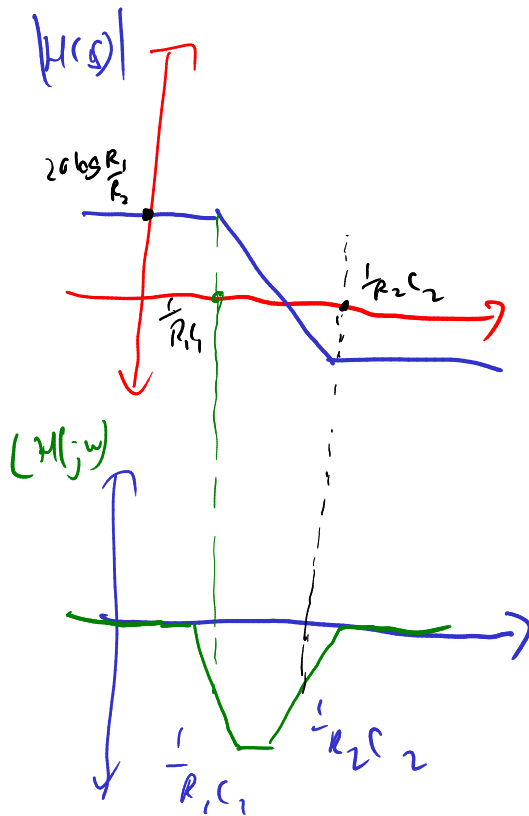

Problem 4

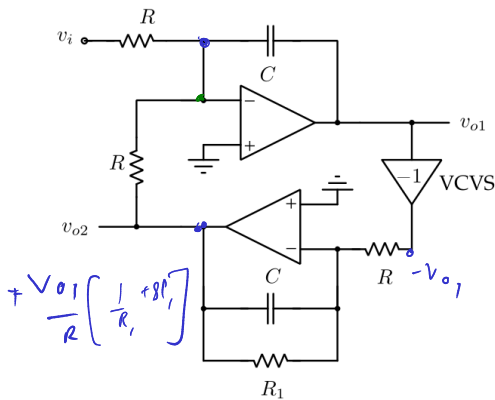


Figure 4: Circuit for Problem 4.

The opamps are ideal. Determine the transfer functions from the v_i to v_{o1} and v_{o2} .

$$\frac{v_{o1}}{-R_0} = + \frac{v_i}{R} \left[\frac{1}{R_1} + sC \right]$$

$$\frac{v_i}{R} + \frac{v_{o2}}{R} + (v_{o1})sC = 0$$

$$\frac{v_i}{R} + \frac{v_{o1}}{R} \left[\frac{1}{R_1} + sC \right] + \frac{R v_{o1} (sC)}{R} = 0$$

$$v_i = -v_{o1} \left[\frac{1}{R \left(\frac{1}{R_1} + sC \right)} + R sC \right]$$

$$= -v_{o1} \left[\frac{1}{\frac{R}{R_1} + R sC} + R sC \right]$$

$$v_i = -v_{o1} \frac{R sC}{\frac{R}{R_1} + R sC} \left[1 + (R sC) \left(\frac{R}{R_1} + R sC \right) \right]$$

$$\frac{v_{o1}}{v_i} = \frac{-\left(R_f + R_{sc}\right)}{1 + (R_{sc})\left(\frac{R_f}{R_i} + R_{sc}\right)}$$


$$v_{o2} = v_{o1} \frac{v_{ef}}{v_i} = \frac{1}{-R_f} \left(\frac{R_f}{R_i} + R_{sc} \right)$$

$$= \frac{-\left(R_f + R_{sc}\right)}{1 + (R_{sc})\left(\frac{R_f}{R_i} + R_{sc}\right)}$$

$$= \frac{-1}{1 + R_{sc} \left(\frac{R_f}{R_i} + R_{sc} \right)}$$

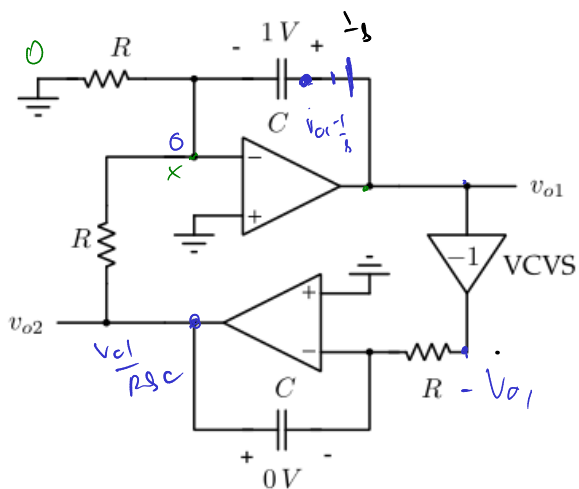Problem 5

The opamps are ideal. The initial conditions are marked. Plot the waveforms v_{o1} and v_{o2} .



$$\left(v_{o1} - \frac{1}{s}\right) \left(1 + \frac{v_{o2}}{R}\right) = 0$$

$$sC v_{o1} - C + \frac{v_{o2}}{R} = 0$$

$$sC v_{o1} - C + \frac{v_{o1}}{R^2 sC} = 0$$

$$v_{o1} \left[sC + \frac{1}{R^2 sC} \right] = C$$



$$v_{o1} = \frac{C}{sC + \frac{1}{R^2 sC}} = \frac{C R^2 sC}{R^2 s^2 C^2 + 1}$$

$$= RC \frac{R sC}{R^2 s^2 C^2 + 1}$$

$$v_{o1}(t) = \left[1 + \cos\left(\frac{t}{RC}\right) \right]$$


$$v_{o2} = \left[\sin\left(\frac{t}{RC}\right) \right]$$

$$v_{o2} = v_{o1} \frac{v_{ef}}{v_i} = \frac{RC}{R^2 s^2 C^2 + 1}$$

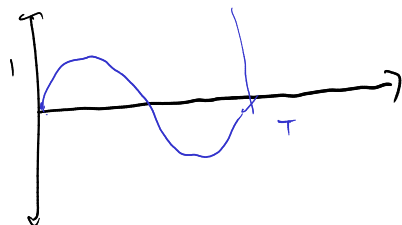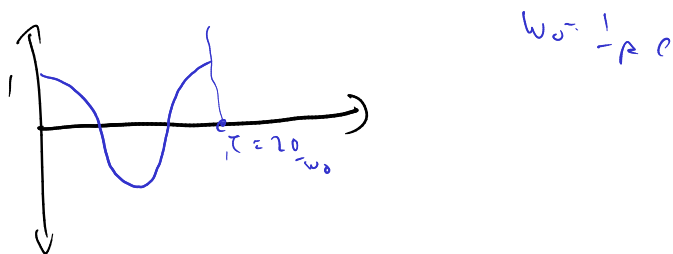

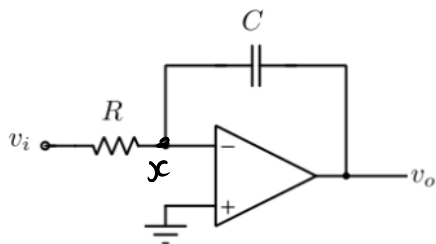Problem 6

Consider the integrator of Fig. 1. The opamp is not ideal, but has a frequency dependent gain determined by GB/s , where GB denotes its gain-bandwidth product. Determine the integrator's transfer function, when a nonideal opamp is used.



$$V_o = -A x$$

$$x - V_i + \frac{(x - V_o)}{R} = 0$$

$$x - V_i + (x - V_o) R s C = 0$$

$$x(1 + R s C) - V_i - V_o R s C = 0$$

$$-\frac{V_o}{A}(1 + R s C) - R s C V_o = V_i$$

$$\frac{V_o}{V_i} = \frac{-1}{\left(\frac{1 + R s C}{A}\right) + R s C}$$


$$\approx \frac{-1}{\underbrace{(1 + R s C)}_{GB} (s) + R s C}$$

$$= -GB$$

$$(1 + R s C) s + R s C (GB)$$

$$= \frac{-A}{(1 + R s C) + A R s C}$$

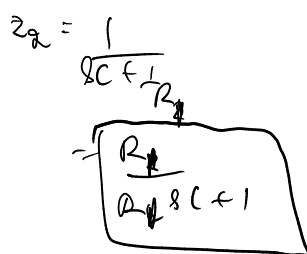Use the results of Problem 6 to evaluate the transfer function of the circuit of Fig. 4 when the opamps have a finite gain-bandwidth product. The VCVS can be assumed to be ideal.



$$V_{02} = +1 \quad V_{01}$$


$$R \left[\frac{R_i g(t)}{R_i} + \frac{1}{A} \left[\frac{1}{R} + \frac{R_i g(t)}{R_i} \right] \right]$$

$$V_{O2} - x + r_i - x + (V_{O1} - x)RSC = 0$$

$$V_{o2} + V_i + V_{o1} R_{sc} = X \left[1 + R_{sc} \right] = - \frac{V_{o1}}{\lambda} \left[2 + R_{sc} \right]$$

$$\left[R \left[\frac{R_i s + 1}{R_i} + \frac{1}{A} \left[\frac{1}{R} + \frac{R_i s + 1}{R_i} \right] \right] + R s C \right] V_{o1} + v_i = - \frac{V_{o1}}{A} \left[\lambda + R s C \right]$$
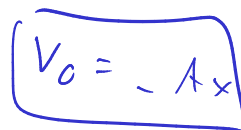
$$V_{o1} = \frac{-A}{R} \left(\frac{Z}{R} + \text{sc}((1+A)) \right) - \frac{A^2 R^2}{\frac{1}{R^2} + (1+A) (\text{sc} + \text{sc}_c)}$$



$$\frac{V_1 - x}{z_1} + \frac{fV_0 - x}{z_2} = 0$$

$$V_i = -\frac{V_0}{z_v} + x \left[\frac{1}{z_1} + \frac{1}{z_v} \right]$$

$$z = \frac{V_0}{z_v} = \frac{V_0}{-A} \left[\frac{1}{z_1} + \frac{1}{z_v} \right]$$

$$V_{\frac{z}{2}} = -V_0 \left[\frac{1}{z_2} + \frac{1}{A} \left(-\frac{1}{z_1} + \frac{1}{z_w} \right) \right]$$

$$\frac{V_0}{V_L} = \frac{1}{2} \left(\frac{1}{z_2} + \frac{1}{z_1} \left(\frac{1}{z_1} + \frac{1}{z_2} \right) \right)$$

$$\frac{V_{02} - x}{R} + \frac{V_{01} - x}{R} + (V_{01} - x) \cdot 80 = 0$$

Voic-Ax

$$V_{O1} = \frac{-A}{R}$$

$$A \approx \frac{4B}{8}$$

$$V_{02} = \frac{A^2 R^2}{\left[2R + 8(1+A) \right] \left(\frac{1}{R} + (1+A) \left(\frac{1}{R_1} \right) \right)} - \frac{A^2}{R}$$

$$A = \frac{4R}{\delta}$$