

EE2019–Analog Systems and Lab: Tutorial 6

Nagendra Krishnapura, Shanthi Pavan

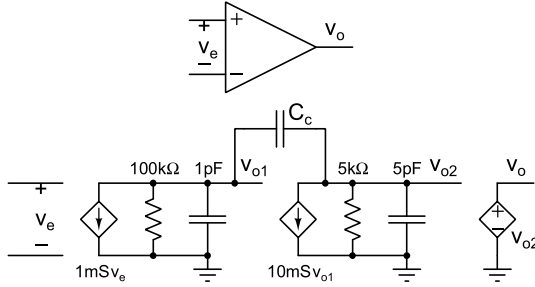


Figure 1: Circuit for problem 1


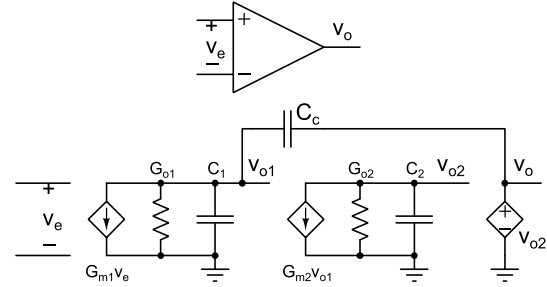
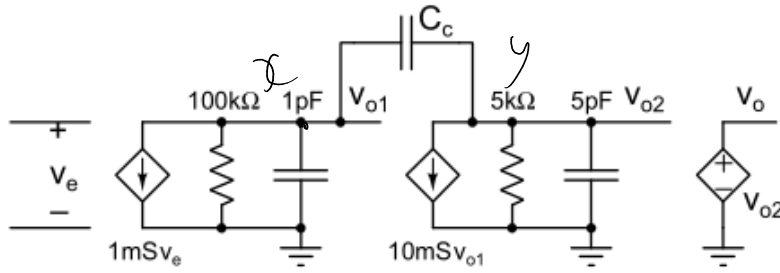


Figure 2: Circuit for problem 2

- Fig. 1 shows the internal schematic of a Miller-compensated opamp. This opamp is used to realize a unity gain, non-inverting amplifier.
 - What is the phase margin?
 - Determine C_c so that the phase margin is 60° .
 - If the same opamp is used without any change to realize an inverting amplifier of gain -4 , what are the phase margin and the closed loop bandwidth?
 - Re-design the opamp (value of C_c) so that when an inverting amplifier of gain -4 is realized using it, the phase margin is 60° . Compare the three cases wrt the following aspects: (a) Closed loop bandwidth, (b) phase margin, (c) phase lag contributed by the right-half-plane zero at the unity loop gain frequency.
 - Compare the bandwidths you obtain to the ones in the previous tutorial in which you simply increased C_1 .
- Determine the transfer function of the opamp in Fig. 2. How does it differ from the conventional Miller compensated opamp in the previous problem?
- It is common to approximate the unity loop gain frequency as $\omega_{u,loop} \approx L_0 p_1$ where L_0 is the dc loop gain and p_1 is the dominant pole. If the loop gain is a second order function $L(s) = L_0 / (1 + s/p_1)(1 + s/p_2)$, determine the exact unity loop gain frequency and the phase margin for the following cases: (a) $p_2 = 4L_0 p_1$, (b) $p_2 = 2L_0 p_1$, and (c) $p_2 = L_0 p_1$. Compare them to the values obtained using the approximation above. $L_0 \gg 1$.

(This approximation is very commonly used for hand calculations, but you should know how much error you end up with while doing so.)

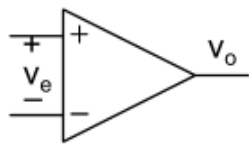While determining the unity loop gain frequency, phase margin, and C_c , do the calculations with and without the approximation $C_c \gg C_{1,2}$.



$$h_{m1} = 10^{-3}$$

$$h_{m2} = 10^{-2}$$

$$R_1 = 10^5$$

$$C_1 = 10^{-12}$$

$$R_2 = 5 \times 10^3$$

$$C_2 = 5 \times 10^{-12}$$

• What is the phase margin?

$$\frac{x}{R_1} + x \delta C_1 + h_{m1} v_e + (x-y) \delta C_c = 0$$

$$x \left(\frac{1}{R_1} + \delta C_1 + \delta C_c \right) = y \delta C_c - h_{m1} v_e$$

$$\left(\frac{y-x}{R_2} \right) \delta C_c + \frac{y}{R_2} + y \delta C_2 - h_{m2} x = 0$$

$$y \left[\delta C_c + \frac{1}{R_2} + \delta C_2 \right] = x \left[\delta C_c - h_{m2} \right]$$

$$y = \frac{x (\delta C_c - h_{m2})}{\left[\delta C_c + \frac{1}{R_2} + \delta C_2 \right]}$$

$$y = \frac{(\delta C_c - h_{m2})}{\left(\delta C_c + \frac{1}{R_2} + \delta C_2 \right)} \left(y \delta C_c - h_{m1} v_e \right) \left[\frac{1}{R_1} + \delta C_1 + \delta C_c \right]$$

$$= (g_{m1} g_{m2}) \left(1 - \frac{s C_c}{g_{m2}} \right)$$

$$s^2 [C_1 C_2 + C_c C_1 + C_c C_2] + s \left[\frac{C_1}{r_{\pi 2}} + \frac{C_2}{r_{\pi 1}} + C_c \left(\frac{1}{r_{\pi 1}} + \frac{1}{r_{\pi 2}} + g_{m2} \right) \right] + \frac{1}{r_{\pi 1} r_{\pi 2}}$$

Dominant pole

$$\frac{1}{s_1} = \frac{\left[\frac{C_1}{r_{\pi 2}} + \frac{C_2}{r_{\pi 1}} + \left(\frac{1}{r_{\pi 1}} + \frac{1}{r_{\pi 2}} + g_{m2} \right) C_c \right]}{\frac{1}{r_{\pi 1} r_{\pi 2}}}$$

Approx

$$\frac{1}{C s^2 + b s + a}$$

Dominant pole
 $= \frac{C}{b}$

$$\left. \begin{aligned} g_{m1} &= 10^{-3} \\ g_{m2} &= 10^{-2} \\ R_1 &= 10^5 \\ C_1 &= 10^{-12} \\ R_2 &= 5 \times 10^3 \\ C_2 &= 5 \times 10^{-12} \end{aligned} \right\}$$

$$= \frac{g_{m2} C_c}{r_{\pi 1} r_{\pi 2}}$$

$$s_1 = \frac{1}{g_{m2} C_c r_{\pi 1} r_{\pi 2}} = \frac{1}{5 \times 10^8 \times 10^{-2} \times C_c}$$

$$= \frac{10}{5 \times 10^8 \times C_c} = \frac{2 \times 10^{-7}}{C_c}$$

Other pole

$$P_2 = \frac{b}{a}$$

$$= \frac{g_{m2} C_c}{C_c [C_1 + C_2] + C_1 C_2}$$

$$= \frac{C_c 10^{-2}}{C_c (6 \times 10^{-12}) + 5 \times 10^{-24}}$$

$$\begin{aligned} \omega_{ng} &= g_m g_{m2} R_1 R_2 P_1 \\ &= 5 \times 10^3 \times 2 \times 10^{-7} = \boxed{\frac{1}{10^3 C_c}} \end{aligned}$$

$$\begin{aligned} PM &= 180 - \tan^{-1} \frac{1}{10^3 C_c} - \tan^{-1} \frac{C_c 10^{-2}}{C_c (6 \times 10^{-12}) + 5 \times 10^{-24}} \\ &\quad - \tan^{-1} \frac{\omega_{ng} C_c}{g_{m2}} \end{aligned}$$

$$= 84.2^\circ - \tan^{-1} \frac{1}{10^3 C_c} - \tan^{-1} \frac{C_c 10^{-2}}{C_c (6 \times 10^{-12}) + 5 \times 10^{-24}}$$

$$= 84.2^\circ - \tan^{-1} \frac{6 \times 10^{-12} C_c + 5 \times 10^{-24}}{C_c^2 10}$$

- Determine C_c so that the phase margin is 60° .

$$80 = 84.2^\circ - \tan^{-1} \frac{6 \times 10^{-12} C_c + 5 \times 10^{-24}}{C_c^2 \cdot 10}$$


$$24^\circ = \tan^{-1} \frac{6 \times 10^{-12} C_c + 5 \times 10^{-24}}{C_c^2 \cdot 10}$$

$$0.44 = \frac{6 \times 10^{-12} C_c + 5 \times 10^{-24}}{C_c^2 \cdot 10}$$

$$C_c \approx 1.9 \times 10^{-12} \text{ F} = \boxed{1.9 \text{ pF}}$$

$$\text{B-W} = 5.26 \times 10^8 \text{ rad/s}^{-1}$$

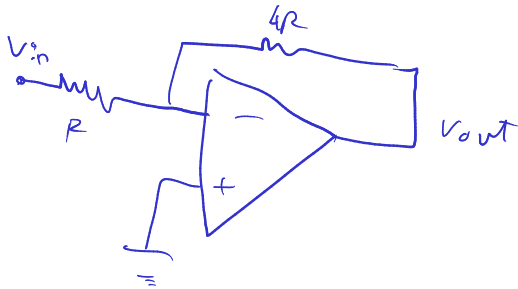- If the same opamp is used without any change to realize an inverting amplifier of gain -4 , what are the phase margin and the closed loop bandwidth?



$$a + bs + cs^2$$

$$\omega_{cg} = A_0 p_1$$

$$= \left(\frac{1}{5 \times 10^3} \right) = \frac{1}{5} \times 10^3 \times 1.9 \times 10^{-12}$$

$$= \boxed{1.05 \times 10^8 \text{ rad/s}}$$

$$LH(s) = -\beta A(s)$$

$$= \left| \frac{-A(s)}{s} \right|$$

$$\text{P.M.} = (80 - \tan^{-1} \frac{\omega_{cg}}{p_1} - \tan^{-1} \frac{\omega_{cg}}{p_2} - \tan^{-1} \frac{\omega_{cg} C_c}{s_{r2}})$$

$$p_1 = \frac{2 \times 10^7}{C_c} = \boxed{1.05 \times 10^8}$$

$$p_2 = \frac{C_c \cdot 10^{-2}}{C_c (6 \times 10^{-12}) + 5 \times 10^{-24}}$$

$$= \boxed{1.05 \times 10^8}$$

$$PM = 180 - 90^\circ - 5.45 - 1.14 = \boxed{83^\circ}$$

$$B.W = \omega_{wg} = \boxed{(0.5 \times 10^8 \text{ rad s}^{-1})}$$

- Re-design the opamp (value of C_c) so that when an inverting amplifier of gain -4 is realized using it, the phase margin is 60° . Compare the three cases wrt the following aspects:
 (a) Closed loop bandwidth, (b) phase margin, (c) phase lag contributed by the right-half-plane zero at the unity loop gain frequency.

$$60 = 180 - \left(90 + 1.14 + \tan^{-1} \frac{\omega_{wg}}{p_2} \right)$$

$$\frac{\omega_{wg}}{p_2} = 0.55$$

$$p_2 = \frac{\omega_{wg}}{0.55} = \frac{1}{5000 C_c \times 0.55}$$

$$= \frac{E_c 10^{-2}}{C_c (6 \times 10^{-12}) + 5 \times 10^{-24}}$$

solve for x $1/(5000x \cdot 0.55) = x \cdot 1e-2/(x \cdot 6e-12 + 5e-24)$

NATURAL LANGUAGE MATH INPUT

EXTENDED KEYBOARD EXAMPLES UPLOAD RANDOM

Input interpretation

solve	$\frac{1}{5000x \cdot 0.55} = x \cdot \frac{1 \times 10^{-2}}{x \cdot 6 \times 10^{-12} + 5 \times 10^{-24}}$	for	x
-------	---	-----	-----

Results

☒ Step-by-step solution

$$x = -3.31044 \times 10^{-13}$$

$$x = 5.49226 \times 10^{-13}$$

$$C_c = 0.54 \text{ pF}$$

$$P.M = 60^\circ$$

$$B.W = \omega_{B.S} =$$

$$3.7 \times 10^8 \text{ rad/s}$$

Comparison

CLBW

$$b \rightarrow 5.2 \times 10^8 \text{ rad/s}$$

$$c \rightarrow 1 \times 10^8 \text{ rad/s}$$

$$d \rightarrow 3.7 \times 10^8 \text{ rad/s}$$

BW

$$b \rightarrow 60$$

$$c \rightarrow 83$$

$$d \rightarrow 60$$

Phase Lag

$$= \tan^{-1} \frac{\omega_{B.S} C_1}{g_2}$$

$$b) 5.6^\circ$$

$$c) 1^\circ$$

$$d) 1^\circ$$

- Compare the bandwidths you obtain to the ones in the previous tutorial in which you simply increased C_1 .

B.W is greater in this case

2)

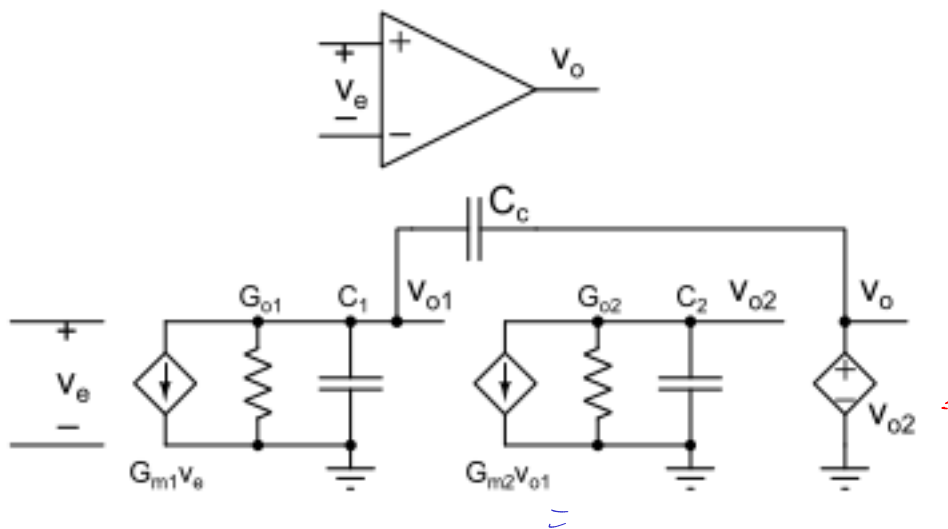


Figure 2: Circuit for problem 2

2. Determine the transfer function of the opamp in Fig. 2. How does it differ from the conventional Miller compensated opamp in the previous problem?

$$G_{m1}v_e + (v_{o1} - 0)G_{o1} + v_{o1}sC_1 + (v_{o1} - v_{o2})sC_c = 0$$

$$G_{m1}v_e + v_{o1}[G_{o1} + sC_1 + sC_c] - v_{o2}sC_c = 0$$

$$G_{m1}v_e - \frac{v_{o2}}{G_{m2}}[G_{o2} + sC_2][G_{o1} + sC_1 + sC_c] - v_{o2}sC_c = 0$$

$$\frac{v_{o2}}{v_e} = \frac{G_{m1}}{sC_c + \frac{(G_{o2} + sC_2)(G_{o1} + s(C_1 + C_c))}{G_{m2}}}$$

$$= L_{m1} L_{m2}$$

$$s L_c L_{m2} + (L_{m2} + s L_c) (L_{m1} + s (C_1 + C_c))$$

$$= \frac{L_{m1} L_{m2}}{L_{m2} L_{m1} + s [L_c L_{m2} + C_2 L_{m1} + L_{m2} (C_1 + C_c)] + s^2 (C_1 + C_c) L_c}$$

No zeroes, unlike miller capacitor

3. It is common to approximate the unity loop gain frequency as $\omega_{u,loop} \approx L_0 p_1$ where L_0 is the dc loop gain and p_1 is the dominant pole. If the loop gain is a second order function $L(s) = L_0 / (1 + s/p_1)(1 + s/p_2)$, determine the exact unity loop gain frequency and the phase margin for the following cases: (a) $p_2 = 4L_0 p_1$, (b) $p_2 = 2L_0 p_1$, and (c) $p_2 = L_0 p_1$. Compare them to the values obtained using the approximation above. $L_0 \gg 1$.

(This approximation is very commonly used for hand calculations, but you should know how much error you end up with while doing so.)

$$a) \frac{L_0}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$L_0^2 = \left(1 + \frac{\omega_u^2}{p_1^2}\right) \left(1 + \frac{\omega_u^2}{p_2^2}\right)$$

$$1 - L_0^2 + \omega_u^2 \left[\frac{1}{p_1^2} + \frac{1}{p_2^2} \right] + \frac{\omega_u^4}{p_1^2 p_2^2} = 0$$

$$1 - L_0^2 + \omega_u^2 \left[\frac{1}{p_1^2} + \frac{1}{L_0^2 p_1^2} \right] + \frac{\omega_u^4}{p_1^2 L_0^2 p_1^2} = 0$$

$$(1-L_0^2) + \left(\frac{\omega \omega^2}{P_1^2}\right) \left[1 + \frac{1}{16L_0^2}\right] + \frac{\omega_0^4}{P_1^4} \left[\frac{1}{16L_0^2}\right] = 0$$

$$\frac{\omega \omega^2}{P_1^2} = - \left(1 + \frac{1}{16L_0^2}\right) \pm \sqrt{1 + \frac{1}{16L_0^4} + \frac{1}{8L_0^2} - \frac{4}{(16L_0^2)}(1-L_0^2)}$$

$$(2) \frac{1}{16L_0^2}$$

$$\frac{\omega \omega}{P_1} = \frac{1}{\sqrt{2}} \sqrt{8\sqrt{5}L_0^2 \sqrt{1 - \frac{1}{16L_0^2}} - 1 - 16L_0^2}$$

$$= \sqrt{4L_0^2(\sqrt{5}-2)}$$

$$\approx 0.97 L_0 P_1$$

$$P.M. (\text{assume } \tan^{-1} L_0 \approx 90^\circ) = \tan^{-1}\left(\frac{4}{0.97}\right) =$$

$$76.3^\circ$$

b)

$$P_2 = 2L_0 P_1$$

$$0 = (1-L_0^2) + \frac{\omega \omega^2}{P_1^2} \left[1 + \frac{1}{4L_0^2}\right] + \frac{\omega \omega^4}{P_1^4 4L_0^2}$$

$$\frac{\omega \omega^2}{P_1^2} = -1 - \frac{1}{4L_0^2} + \sqrt{1 + \frac{1}{(16L_0^4)} + \frac{1}{2L_0^2} - \frac{(1-L_0^2)}{L_0^2}}$$

$$= \frac{\sqrt{1 + \frac{1}{16L_0^4} + \frac{1}{L_0^2} - \frac{1}{L_0^2} + 1}}{\frac{1}{2}L_0^2} - 1 - \frac{1}{4L_0^2}$$

$$= \left[\sqrt{2L_0^2 + \cancel{\frac{1}{16L_0^2}} - \frac{1}{2}} \quad -L_0^2 - \frac{1}{4} \right]^2 (x-y)^{1/2}$$

$$= 2L_0^2 \left(\sqrt{2 - \frac{1}{2L_0^2}} - 1 - \frac{1}{4L_0^2} \right)$$

$$\omega \quad \bar{P} = \sqrt{2} L_0 \sqrt{\sqrt{2} \left(1 - \frac{1}{4L_0^2} \right)^{1/2} - 1 - \frac{1}{4L_0^2}}$$

$$= \sqrt{2} L_0 \sqrt{\sqrt{2} \left[1 - \frac{1}{8L_0^2} \right] - 1 - \frac{1}{4L_0^2}}$$

$$= L_0 \sqrt{2(\sqrt{2}-1)} = 0.904 L_0$$

$$P.M. \approx 65^\circ$$

$$c) \quad P_2 = L_0 P_1$$

$$0 = 1 - L_0^2 + \frac{\omega_y^2}{P_1^2} \left[1 + \frac{1}{L_0^2} \right] + \frac{\omega_y^4}{P_1^4 L_0^2}$$

$$0 = L_0^2 - L_0^4 + \frac{\omega_y^2}{P_1^2} (L_0^2 + 1) + \frac{\omega_y^4}{P_1^4}$$

$$\frac{\omega_y^2}{P_1^2} = -L_0^2 - 1 + \sqrt{L_0^4 + 2L_0^2 + 1 - 4L_0^2 + 4L_0^4}$$

$$= L_0^2 \left[\frac{-1 - \frac{1}{L_0^2} + \sqrt{5 - \frac{2}{L_0^2}}}{2} \right]$$

$$\frac{\omega_y}{P_1} = L_0 \sqrt{\frac{\sqrt{5}-1}{2}}$$

$$= 0.78 L_0 \quad P.M. \approx 52^\circ$$